

LECTURE NOTES
PHYSICS
ELECTROSTATS,
CURRENT ELECTRICITY,
ELECTRICAL INSTRUMENT,
CAPACITANCE

BY

D.J. SIR

BOOK - I

ELECTURE NOTES

PHYSICS

ELECTROSTATS

CURRENT ELECTRICITY

ELECTRIC INSTRUMENT

CAPACITANCE

BY

SHREE NATH JI BOOK 7014774207

D.L.SIR

1977

⊕ Fundamental Forces of Nature :-

Force	Relative strength.
① gravitational.	1
② Electromagnetic.	10^{36}
③ Nuclear.	10^{39}
④ weak	10^{14}

**For Proton-Proton only.

Ques > what is relative strength of Electromagnetic force w.r.t

- ① Nuclear force
- ② weak force
- ③ gravitational force.

Ans >

$$① \quad \text{Nuclear force} = \frac{10^{36}}{10^{39}} = 10^{-3}$$

$$② \quad \text{weak force} = \frac{10^{36}}{10^{14}} = 10^{22}$$

$$③ \quad \text{gravit. force} = \frac{10^{36}}{1} = 10^{36}$$

⊕ ⇒ charge :-

→ It is the excess or deficiency of electrons.



 Neutral. ⊖ve charge ⊕ve charge

→ Charge = current × time.

$$q = I \times t$$

→ scalar quantity.

→ Unit $\left\{ \begin{array}{l} \rightarrow \text{MKS; coulomb (C), Amp} \times \text{sec} \\ \rightarrow \text{cgs} \left\{ \begin{array}{l} \rightarrow \text{ESU; static 'c', Frankln.} \\ \rightarrow \text{EMU; Absolute 'c' (Abc)} \end{array} \right. \end{array} \right.$

$$= 1 \text{ C} = 3 \times 10^9 \text{ stat 'c'}$$

$$= 1 \text{ C} = \frac{1}{10} \text{ Abc.}$$

^{special unit}

$$1 \text{ F} = 96500 \text{ C.}$$

$$= (NA) (e)$$

1 Faraday is a charge required to shift 1-gram equivalent mass from one electrode to another in electrolysis.

Dimension:- A.T

Ques) 10 Amp current is passed through a wire upto 10 min, then calculate charge?

Ans)


$$q = A \times t$$

$$= 10 \times (10 \times 60) \text{ sec.}$$

$$= 6000 \text{ C.}$$

* \Rightarrow Property of charge :-

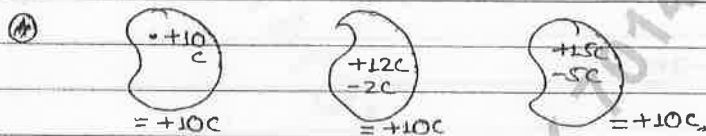- ① charge is additive in nature.
- ② charge is invariant. (it means it's speed value doesn't depends on its speed.)
- ③ Total charge of isolated system is always 'conserved'.



Total charge is conserved but Total Positive 'or' Negative charge may change.

④ Quantisation of charged :-

(i) Minimum possible charge = $(e) = 1.6 \times 10^{-19} \text{ C}$
(Quanta of charge)

(ii) Any other charge

$$q = ne$$

where; $n = \pm 1, \pm 2, \pm 3, \dots$

(iii) Exception of Quantisation :-

"Quark" $\begin{cases} \rightarrow \text{Up (U)} (+2e/3) \\ \rightarrow \text{Down (D)} (-e/3) \end{cases}$

eg:- $\odot 2\text{U} \oplus 1\text{D} \rightarrow 1 \text{ proton}$

$$2 \times \left(\frac{+2e}{3}\right) + 1 \times \left(-\frac{e}{3}\right) = +e$$

② $1U + 2D \longrightarrow 1 \text{ Neutron}$

$$1\left(\frac{+2e}{3}\right) + 2\left(\frac{-e}{3}\right) = 3e \times 0$$

Ques > which of the following charges are possible:-

✓① $+5e$

✓② $-3e$

✗③ $+5.2e$

✗④ $+7/3e$

✓⑤ $\frac{-57e}{19} = -3e$

✓⑥ $3.2 \times 10^{-19} e = \frac{q}{e} = \frac{3.2 \times 10^{-19}}{1.6 \times 10^{-19}} = 2e$

✗⑦ $6.4 \times 10^{-20} C = \frac{q}{e} = \frac{6.4 \times 10^{-20}}{1.6 \times 10^{-19}} = 0.4e$

✓⑧ $1.6 \times 10^{-18} e = \frac{q}{e} = \frac{1.6 \times 10^{-18}}{1.6 \times 10^{-19}} = 10e$

⑤ charge produces:-

At Rest \Rightarrow only 'E'

$v = \text{const} \Rightarrow$ 'E' and 'B'






$v \neq \text{const} \Rightarrow$ "E", "B" & "E.M.W"

*⑥ charge cannot exist without mass.

⑦ In conductor's charge is distributed at outer-surface only, while in non-conductor charge is distributed in inside volume.

⇒ conducting

Non-conducting

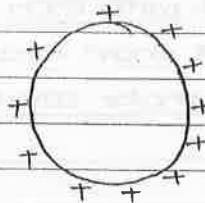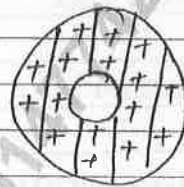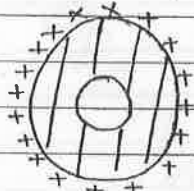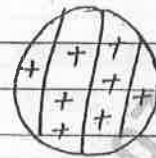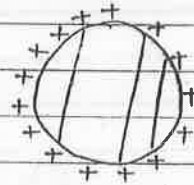

⇒ Electrical Behaviour of charged object is decided by charge distribution only.

⊛ ⇒ Methods of charging :-

① Friction :-



$q_A = +ne$ } ⇒ same magnitude and opposite nature of charges are produced in friction.
 $q_B = -ne$ }

eg:- ⊕ ve ⊖ ve.

- | | |
|--------------|----------|
| ① Dry-Hair | comb. |
| ② cat skin. | Ebonite. |
| ③ wool. | Amber. |
| ④ glass Rod. | silk. |




② CONDUCTION :-

when two conductors are touched with each other "or" connected using conducting wire then total charge of system is redistributed to make same potentials.

$$\therefore V = \frac{Q}{R}$$

$$Q \propto R \quad \text{Here; } R = \text{Radius.}$$

Ques> Two metal spheres:-

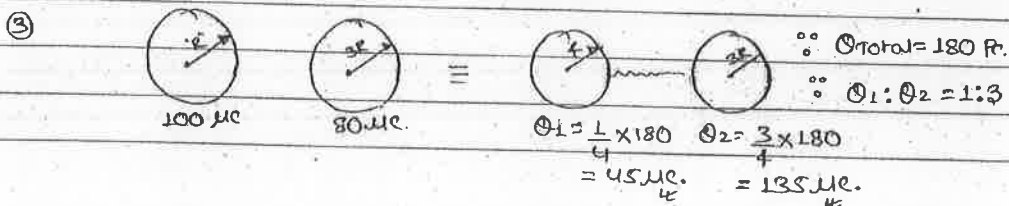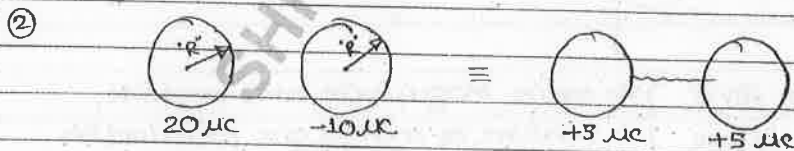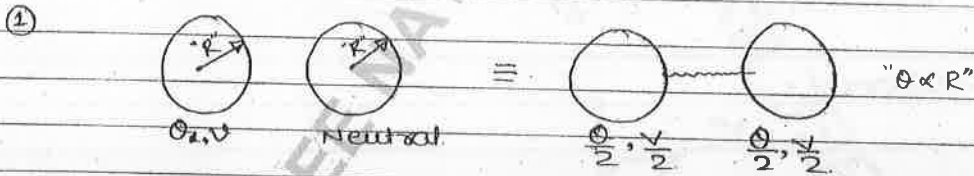

→* After conduction potential definitely become same, while charges may be different.

Ques) Three Identical conducting sphere :-

"TOUCH"	A ^Q	B ⁰	C ^{-Q}
"A & B"	$Q/2$	$Q/2$	$-Q$
"B & C"	$Q/2$	$-Q/4$	$-Q/4$
A & C	$+Q/8$	$-Q/4$	$+Q/8$

☆ ⇒ CHARGE DENSITY :-

① Linear charge density (λ) = $\frac{\text{charge}}{\text{Length}}$ $\frac{C}{m}$

② Surface charge density (σ) = $\frac{\text{charge}}{\text{surface Area}}$ $\frac{C}{m^2}$

③ Volume charge density (ρ) = $\frac{\text{charge}}{\text{Volume}}$ $\frac{C}{m^3}$

** Ques) Two metal sphere ;



If these are touched by each other than find charge density of each other?

- $\Rightarrow \oplus$ charged :- Move from high Potential to low Potential.
 $\Rightarrow \ominus$ charged :- Move from Low Potential to High Potential.

Date _____ Page _____

$$\text{Ans} \rightarrow Q_{\text{Total}} = \sigma(4\pi R^2) + \sigma[4\pi(2R)^2]$$

$$= 20\sigma\pi R^2$$

$$Q_1 : Q_2 = 1 : 2 \quad (R_1 : R_2)$$

$$Q_1 = \frac{1}{3} \times 20\sigma\pi R^2$$

$$Q_2 = \frac{2}{3} \times 20\sigma\pi R^2$$


$$\sigma_1 = \frac{Q_1}{4\pi R^2} = \frac{1/3 \times 20\sigma\pi R^2}{4\pi R^2} = \frac{5\sigma}{3}$$

$$\sigma_2 = \frac{Q_2}{16\pi R^2} = \frac{2/3 \times 20\sigma\pi R^2}{16\pi R^2} = \frac{10\sigma}{12} = \frac{5\sigma}{6}$$

$$\frac{\sigma_1}{\sigma_2} = 2 : 1$$

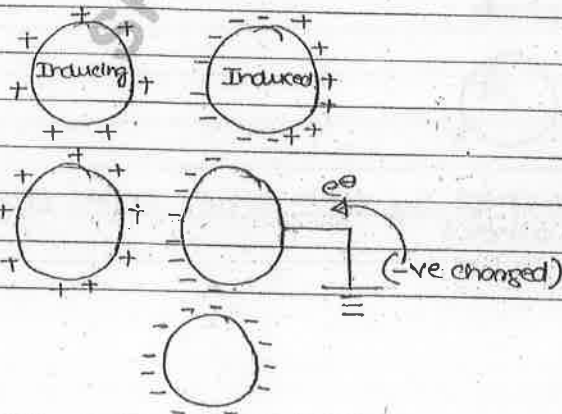*** (2) INDUCTION :-

When (2) Bodies are placed close to each other than their charge distribution is affected, this is called "Induction."



* $C_{induced} = C_{inducing} \left(1 - \frac{1}{\epsilon_r}\right)$

① of metal than; ($\epsilon_r = \infty$)


$\therefore C_{induced} = C_{inducing}$

② of Non-metal than; ($\epsilon_r \neq \infty$)

$\therefore C_{induced} > C_{inducing}$



**Ques > Two metallic plate 0 and 30 are placed parallel and close to each other than;

Ans >

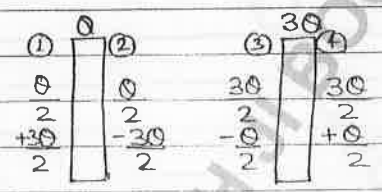


- $q_1 = +20$
- $q_2 = -0$
- $q_3 = +0$
- $q_4 = +20$

Ques > "Multiplate System":-

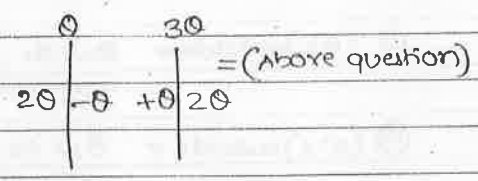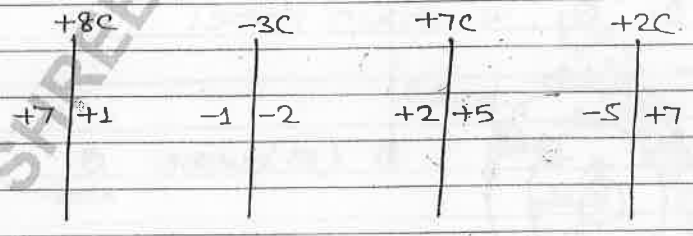


Ques) Multiple plates:-

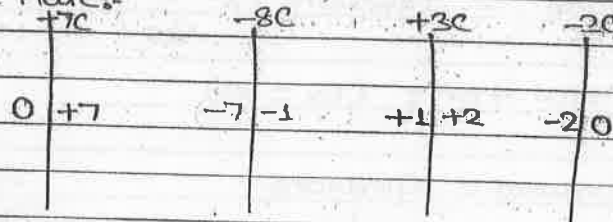

Ques) Hollow Metal sphere :-

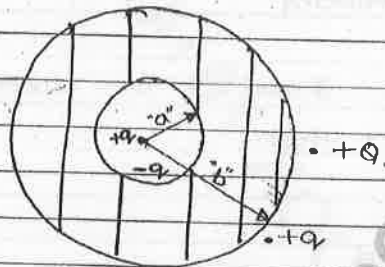small +q is placed at centre and +Q is given to sphere:-




$$\sigma_{\text{inner}} = \frac{-q}{4\pi a^2}$$

$$\sigma_{\text{outer}} = \frac{Q+q}{4\pi b^2}$$

AIEEE

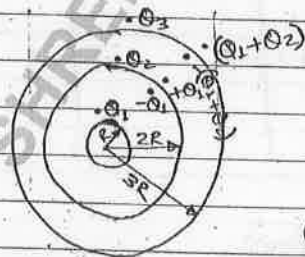Ques) Three concentric metal shells, are given charges Q_1 , Q_2 , Q_3 , as shown there;



(i) $(\sigma_1)_{\text{outside}} = \frac{Q_1}{4\pi R^2}$

(ii) $(\sigma_2)_{\text{outside}} = \frac{Q_1 + Q_2}{4\pi (2R)^2}$

(iii) $(\sigma_3)_{\text{outside}} = \frac{Q_1 + Q_2 + Q_3}{4\pi (3R)^2}$

⊛ Important Points of INDUCTION:-

- ⊙ (i) Induction Takes Place In Facing Layer's only.
- ⊙ (ii) Induction does not affect's the magnitude of charge But it affect's only Distribution of charge.
- ⊙ (iii) There will be attraction b/w charged and neutral Bodies.
- ⊙ (iv) There may be attraction b/w Two Bodies of same Nature charges, provided that magnitude of charges must be Different.
- ⊙ (v) Sure Test of Electrification is ^(charged) Repulsion only, Not the Repulsion. Attraction.

⊛ ⇒ COULOMB'S LAW:-



$$F \propto q_1 q_2$$

$$F \propto \frac{1}{r^2}$$

$$F \propto \frac{q_1 q_2}{r^2}$$

$$F = K \frac{q_1 q_2}{r^2}$$

$$K = \frac{1}{4\pi\epsilon_0} = 9 \times 10^9 \text{ (MKS)}$$

$$K = 1 \text{ (CGS)}$$

* q_1 "Attr" q_2

$$F_{air} = \frac{1}{4\pi\epsilon_0} \cdot \frac{q_1 q_2}{r^2}$$

q_1 // ϵ_r // q_2

$$F_{med} = \frac{1}{4\pi\epsilon_0\epsilon_r} \cdot \frac{q_1 q_2}{r^2}$$

$$F_{med} = \frac{F_{air}}{\epsilon_r}$$

$$\because \epsilon_r > 1 \Rightarrow F_{med} < F_{air}$$

* Electric Permittivity (ϵ):

$$\rightarrow \epsilon_0 = 8.85 \times 10^{-12} \frac{C^2}{N \cdot m^2}$$

$$\rightarrow \epsilon = (\text{different for different medium}) \frac{C^2}{N \cdot m^2}$$

$$\rightarrow \epsilon_r = \frac{\epsilon}{\epsilon_0} \text{ (unitless)}$$

$$1 \leq \epsilon_r \leq \infty$$

$$\epsilon_r(\text{metal}) = \infty$$

Ques) q_1 "Attr" q_2

$$F_{air} = 18 \text{ N}$$

(i) if $\epsilon_r = 6$ is filled then F_{med} :-

$$F_{med} = \frac{F_{air}}{\epsilon_r} = \frac{18}{6} = 3 \text{ N}$$

(ii) If metallic medium is filled :-

$$F_{\text{med}} = \frac{18}{\infty} = 0.$$

Ques) $e^- \quad \quad \quad e^- \quad \quad \quad \frac{F_e = ?}{F_g}$

← r →

Aus) $\frac{F_e}{F_g} = \frac{\left\{ \frac{K(e)(e)}{r^2} \right\}}{\left\{ \frac{G(m_e)(m_e)}{r^2} \right\}}$

$$= \frac{9 \times 10^9 (1.6 \times 10^{-19})^2}{6.6 \times 10^{-11} (9.1 \times 10^{-31})^2}$$

$$= 4 \times 10^{42}$$

$$= 10^{42}$$

** ⊕ ⇒ $F_e/F_g = ?$

$$\left. \begin{array}{l} p - p \rightsquigarrow 10^{36} \\ p - e \rightsquigarrow 10^{39} \\ e - e \rightsquigarrow 10^{42} \end{array} \right\}$$


Ques) calculate Min^m electric force betwⁿ two point charge placed at 1cm separatiⁿ?

Aus) $F_{\text{min}} = \frac{K(q_1 \cdot q_2)_{\text{min}}}{r^2}$


$$= \frac{9 \times 10^9 (1.6 \times 10^{-19})^2}{(1 \times 10^{-2})^2} = 23.9 \times 10^{-25}$$

$$\approx 0.23 \times 10^{-23} \text{ N}$$

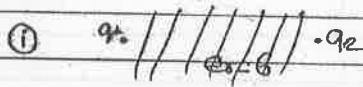Ques) Given; q_1 "Air" $-q_2$ $F_{air} = 18\text{ N}$



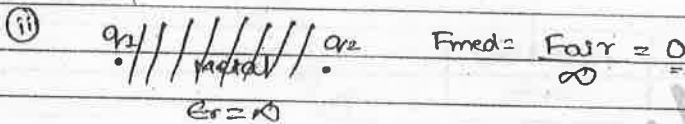
$$F_{med} = F_{air} = \frac{18}{6} = 3\text{ N}$$



$$F_{med} = \frac{F_{air}}{\infty} = 0$$

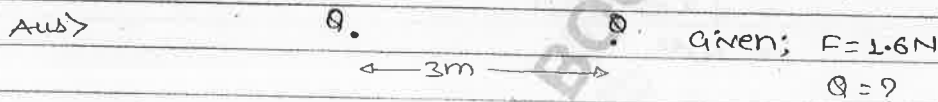Ques) Two equal charges placed at separation 3m and force b/w them is 1.6 N, calculate each charge?



$$F = \frac{k Q_1 Q_2}{r^2}$$

$$1.6 = \frac{9 \times 10^9 (Q)(Q)}{(3)^2}$$


$$Q^2 = \frac{1.6 \times 9}{9 \times 10^9} = 1.6 \times 10^{-9} = 16 \times 10^{-10}$$

$$Q^2 = 16 \times 10^{-10}$$

$$Q = 4 \times 10^{-5}$$

$$Q = 4 \times 10^{-5}$$

*** Ques) what should be two parts of charge so that there is max^m force b/w them when placed at fixed separation?

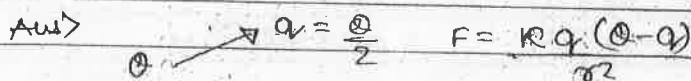Ans) 

$$F = \frac{k(Q-q)(Q-q)}{r^2}$$

⇒ Maxima - minima :-

$$y = f(x)$$

$$(i) \frac{dy}{dx} = 0$$

$$x = x_1, x_2, \dots$$

$$(ii) \left(\frac{d^2y}{dx^2} \right)_{x=x_1} = \ominus ve. \text{ (Maxima).}$$

$$= \oplus ve. \text{ (Minima).}$$


$$\frac{dF}{dq} = \frac{R}{r^2} (0 - 2q) = 0$$

$$\therefore q = \frac{0}{2}$$

$$\frac{d^2F}{dq^2} = \frac{R}{r^2} (0 - 2) = -\frac{2R}{r^2} = \ominus ve.$$

$$\therefore \boxed{q = \frac{0}{2}} \text{ Maxima}$$

*** ⇒ Important :-

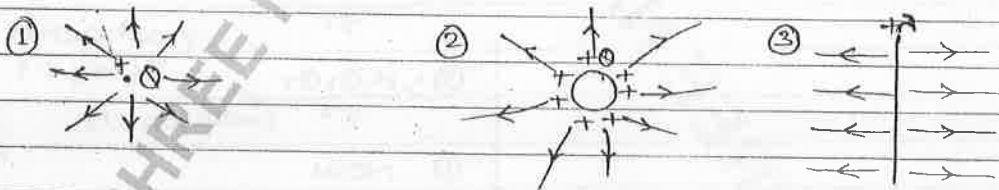

→ Electrical behaviour of spherical charge is similar to point charge, while linear charge have different behaviour so coulombs law is valid for "point charge" and "spherical charge".

Ques



$\frac{kQ_1Q_2}{r^2}$

$kQ_1Q_2 \checkmark$ (correct)

$\frac{2kQ_1Q_2}{r^2}$

$< \frac{kQ_1Q_2}{r^2}$ Here $r \uparrow$; so $F \downarrow$
(more correct)

$\frac{kQ_1Q_2}{2r^2}$


$> \frac{kQ_1Q_2}{r^2}$

$\frac{kQ_1Q_2}{4r^2}$

None

\Rightarrow Here; Due to Induction "centre of charges" shifted away. so Repulsion increases (means $r \uparrow$) and Force \downarrow

Ques

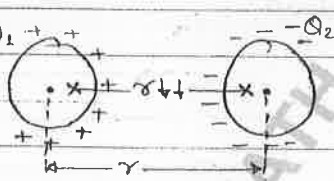

① $\frac{kQ_1Q_2}{r^2}$ (correct)

② $< \frac{kQ_1Q_2}{r^2}$

\therefore attraction \uparrow


③ $> \frac{kQ_1Q_2}{r^2}$ (more correct)

$F \downarrow$ so; $F \uparrow$

④ None

**

Ques

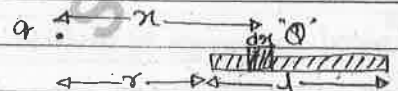

calculate Electric Force :-

Ans) $F = \frac{kQq}{r^2}$

$F = \frac{kQq}{(r+l/2)^2}$ \therefore (Coulomb's charge not applicable)

Force on Element:-

$$dF = \frac{kQq}{x^2} \left(\frac{Q}{L} dx \right)$$

$$F_{wt} = \int_r^{r+L} \frac{kQq}{x^2} dx$$

$$F_{wt} = \frac{kQq}{L} \left[-\frac{1}{x} \right]_r^{r+L}$$

$$= -\frac{kQq}{L} \left[\frac{1}{r+L} - \frac{1}{r} \right]$$

$$= -\frac{kQq}{L} \frac{r - r + L}{(r+L)r}$$

$$F_{wt} = \frac{kQq}{r(r+L)}$$

⊗ ⇒ If $F_{air} = F_{medium}$:-


$$\frac{1}{4\pi\epsilon_0} \cdot \frac{q_1 q_2}{r_{air}^2} = \frac{1}{4\pi\epsilon_0 \epsilon_r} \cdot \frac{q_1 q_2}{r_{med}^2}$$

$$r_{air}^2 = \epsilon_r \cdot r_{med}^2$$

$$r_{air} = \sqrt{\epsilon_r \cdot r_{med}^2}$$

Ques) $r_{med} = 5 \text{ cm}$; $\epsilon_r = 9$; $r_{air} = ?$

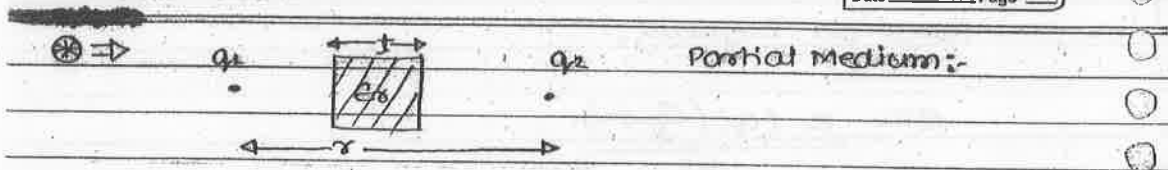Ans) $r_{air} = \sqrt{\epsilon_r} r_{med} \Rightarrow r_{air} = \sqrt{9} \times 5 = 15 \text{ cm}$



$$F_{\text{partial}} = \frac{L}{4\pi\epsilon_0} \frac{q_1 q_2}{\left[\frac{(r-l)}{2} + \frac{l\sqrt{\epsilon_r}}{2} \right]^2}$$

Ques> Force b/w 2-charges in air is F , if half separatrⁿ is filled by medm of $\epsilon_r = 4$; than calculate Force?

Ans> q_1 $\xrightarrow{\text{air}}$ q_2 $F = \frac{L}{4\pi\epsilon_0} \frac{q_1 q_2}{r^2}$

q_1 $\xrightarrow{\text{dielectric } \epsilon_0/4}$ q_2 $F' = \frac{L}{4\pi\epsilon_0} \frac{q_1 q_2}{\left[\frac{(r-r/2)}{2} + \frac{r/2\sqrt{4}}{2} \right]^2}$

$$F' = \frac{L}{4\pi\epsilon_0} \frac{q_1 q_2}{\left[\frac{r}{2} + \frac{r}{2} \right]^2}$$

$$F' = \frac{L}{4\pi\epsilon_0} \frac{4q_1 q_2}{9r^2}$$

$$F' = \frac{4F}{9}$$

⇒ coulomb Force is due to "Mutual Interactⁿ" b/w charges so;-

- (i) q1 is not affected by \oplus uce of other charges.
- (ii) q1 obey's Newton's action-Reaction.



$$\begin{aligned} F_{12} &= F_{21} \\ \vec{F}_{12} &= -\vec{F}_{21} \end{aligned}$$

Ques $q_1 = 1 \mu C$ $q_2 = 5 \mu C$
 $\leftarrow 10 \text{ cm} \rightarrow$

$$\frac{F_{1,2}}{F_{2,1}} = ? = 1:1 \quad (\text{Action-Reaction})$$


* vector Form:-

$$\vec{F} = \frac{k q_1 q_2}{r^2} \hat{r}$$

$$\vec{F} = \frac{k q_1 q_2}{r^3} \vec{r}$$

*** In any vector formula, charge must be with sign.

Ques H-atom

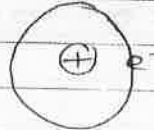

$\vec{F} = ?$ (Ans in vector form)

Ans


*** must take with sign

$$\vec{F} = \frac{k (e)(e)}{r^2} \hat{r}$$

$$= -\frac{k e^2}{r^3} \vec{r}$$

* \Rightarrow SUPERPOSITION PRINCIPLE:-
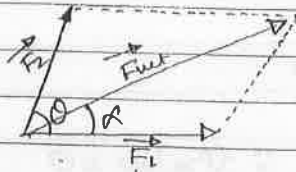
$$\vec{F}_{\text{net}} = \vec{F}_1 + \vec{F}_2 + \vec{F}_3 + \dots$$




$$\text{If } \vec{F}_{\text{net}} = \vec{F}_1 + \vec{F}_2$$

$$\therefore F_{\text{net}} = \sqrt{F_1^2 + F_2^2 + 2F_1 F_2 \cos \theta}$$


$$\therefore \tan \alpha = \frac{F_2 \sin \theta}{F_1 + F_2 \cos \theta}$$

Ques)

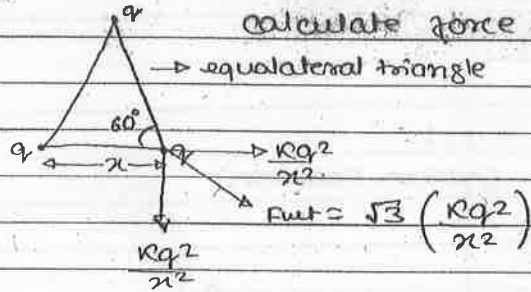


calculate force on any one charge.

Ques)

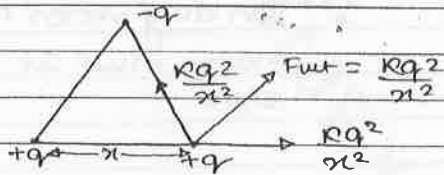

Ques)

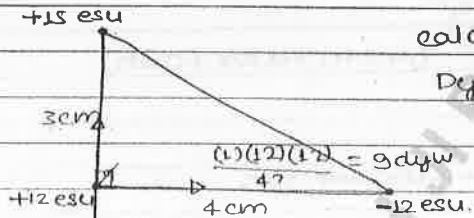

calculate force on +12 esu in Dyne?


$$F_{net} = \sqrt{20^2 + 9^2}$$

$$= \sqrt{481}$$

$$\approx 22 \text{ dyne.}$$

IEEE

Ques)

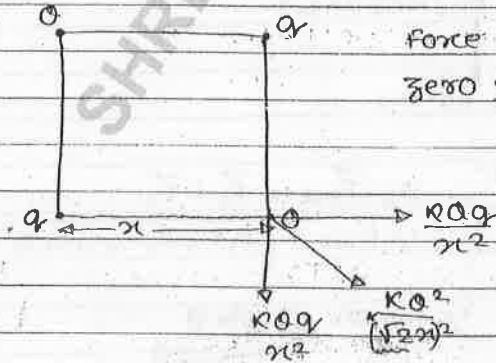


force on each capital 'q' is zero ; then $\frac{Q}{q} = 2$

$$\sqrt{2} \left(\frac{kQq}{r^2} \right) + \frac{kQ^2}{(\sqrt{2}r)^2} = 0$$

$$\sqrt{2} \left(\frac{kQq}{r^2} \right) = -\frac{kQ^2}{\sqrt{2}r^2}$$

$$\frac{q}{Q} = -2\sqrt{2}$$

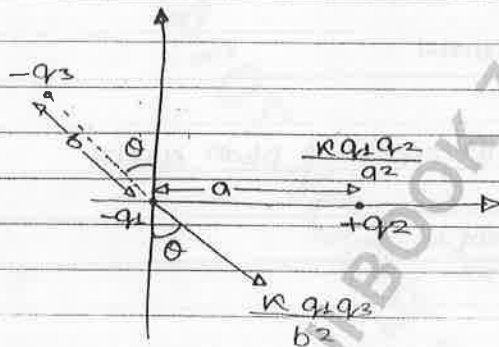
Ques) calculate x-component of force on charge $-q_1$?



$$(F_{-q_1})_{x\text{-comp}} = \frac{kq_1q_2}{a^2} + \frac{kq_1q_3}{b^2} \sin \theta$$

$$(F_{-q_1})_{y\text{-comp}} = \frac{kq_1q_3}{b^2} \cos \theta$$

Ques
✓

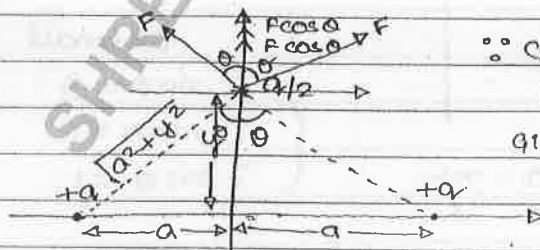

∴ calculate force on charge

$q/2$.

given:- $y \ll a$.


$$F_{net} = 2F \cos \theta$$

$$= 2 \left\{ \frac{k(q)(q/2)}{(\sqrt{a^2+y^2})^2} \right\} \left\{ \frac{y}{\sqrt{a^2+y^2}} \right\}$$

$$F_{\text{net}} = \frac{kq^2}{(a^2 + y^2)^{3/2}} \cdot y = \frac{kq^2 \cdot y}{a^3} \quad \because (y \ll a)$$

$$F_{\text{net}} \propto y$$

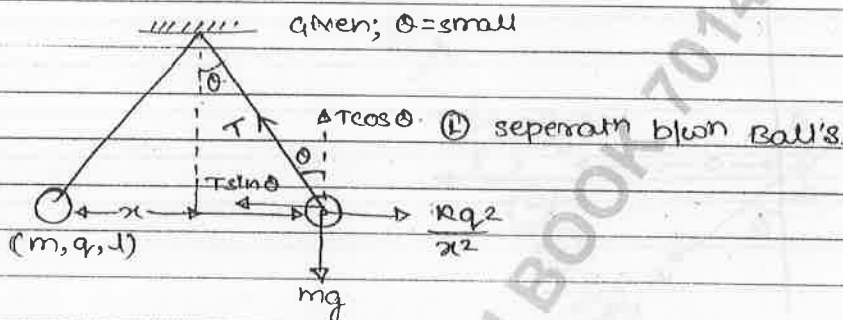*** Ques \rightarrow 2- Identical simple Pendulum, (m, q, l) are suspended from common point, in equilibrium strings are making "small angle" with vertical than;



At Balance condition (equilibrium):-

$$T \sin \theta = \frac{kq^2}{x^2} \quad \text{--- (1)}$$

$$T \cos \theta = mg \quad \text{--- (2)}$$

by (1)/(2) :- $\tan \theta = \frac{kq^2}{x^2 \cdot mg}$

Given $\theta = \text{very small}$

$$\tan \theta = \theta \approx \sin \theta = \frac{x}{l}$$


*** $\theta = \text{small}$

- $\because \sin \theta = \theta$
- $\because \tan \theta \approx \theta$
- $\because \cos \theta \approx 1$

$$\frac{x}{l} = \frac{kq^2}{x^2 \cdot mg}$$

$$x^3 = \frac{2kq^2 l}{mg} \Rightarrow \theta = \left[\frac{2kq^2 l}{mg} \right]^{1/3}$$

$$x \propto l^{1/3}$$

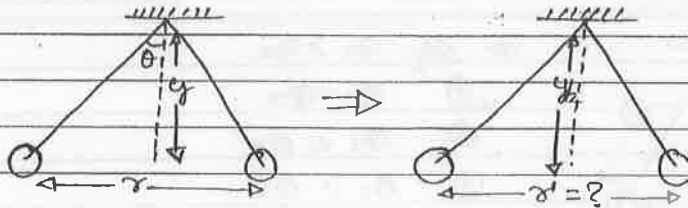

$$\tan \theta = \frac{kq^2}{r^2 mg} = \frac{r/2}{y}$$

$$r^3 \propto y \Rightarrow r \propto y^{1/3}$$

$$\frac{r'}{r} = \left(\frac{y/2}{y}\right)^{1/3} = \frac{1}{2^{1/3}}$$

$$\boxed{r' = \frac{r}{\sqrt[3]{2}}}$$

$$* \because 2\sqrt{2} = 2^{1/2}$$

$$\because \sqrt[3]{2} = 2^{1/3}$$

Ques > If charge of balls starts to die at a constant rate and balls come closer, with speed v then relation b/w v and x

Ans > $x^3 = \frac{2kq^2}{mg}$ \because (see previous question)


$$\because x^3 \propto q^2$$

$$\because q \propto x^{3/2}$$

$$\left(\frac{dq}{dt}\right)_{\text{const.}} \propto \left(\frac{3}{2}\right) x^{1/2} \cdot \left(\frac{dx}{dt}\right) = v$$

$$v \cdot x^{1/2} = \text{const.}$$

$$\therefore \boxed{v \propto x^{1/2}}$$

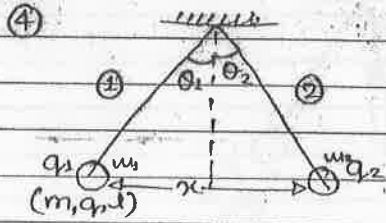

- ④ If $q_1 > q_2$
- ① $\theta_1 = \theta_2$
 - ② $\theta_1 < \theta_2$
 - ③ $\theta_1 > \theta_2$
 - ④ None


** ⑤ If $m_1 > m_2$

- ① $\theta_1 = \theta_2$
- ② $\theta_1 < \theta_2$ $\because \tan \theta \propto \frac{1}{m}$
- ③ $\theta_1 > \theta_2$
- ④ None

⑥ If this system is taken in space or artificial satellite?


Here; $g = 0$
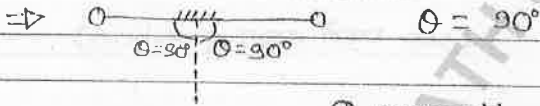
$$\tan \theta = \frac{kq^2}{r^2 m(g)} = \infty$$



- ① separation b/w balls = $L + L = 2L$
- ② Angle b/w strings = $90^\circ + 90^\circ = 180^\circ$
- ③ $F_e = \frac{kq^2}{(2L)^2} = \frac{kq^2}{4L^2}$
- ④ Tension in each string = $T = F_e = \frac{kq^2}{4L^2}$

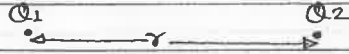★ \Rightarrow TO locate Equilibrium Position :-



- (i) If Q_1 and Q_2 is of "same nature" than between the charges.
- (ii) If Q_1 and Q_2 is of opposite nature than outside the charges.
- (iii) Always close to small "magnitude" charges.



\rightarrow Right side of Q (small charge)

$$Kq \cdot Q = \frac{Kq \cdot 4Q}{(r-x)^2}$$

$$\frac{1}{x^2} = \frac{4}{(r-x)^2}$$

$$\frac{1}{x} = \frac{2}{r-x}$$

$$r-x = 2x$$

$$\frac{r}{3} \text{ from } Q$$

$$r - \frac{r}{3} = \frac{2r}{3} \text{ from } 4Q$$

$$\boxed{x = \frac{r}{3}}$$

Ques \rightarrow



(1) Right side of 'Q'

$$(2) \frac{KQq}{x^2} = \frac{Kq(4Q)}{(r+x)^2} \Rightarrow \boxed{x=r}$$


$$\frac{1}{x^2} = \frac{4}{(r+x)^2}$$

Ques >



$$x = \frac{r}{2} \text{ (mid point)}$$

Ques >

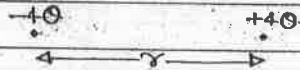

Here; equilibrium does not exist.

It means equilibrium point at "infinite"


* \Rightarrow EQUILIBRIUM :-

① Particle equilibrium. (Fut on "given particle" is zero)

② System equilibrium. (Fut on "each particle" of system is zero)

AIPMT

Ques >

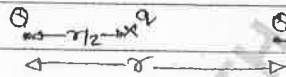

Find Posn and value of charge 'q'.

$$\frac{kQ^2}{r^2} + \frac{kQq}{(r/2)^2}$$

① For q's equilibrium

② For system equilibrium

Ans >


① $x = \frac{r}{2}$ (mid point)

 \Rightarrow q is in equilibrium for any value.

② $(F_e)_{\text{net}} = 0$

$$\frac{kQ^2}{r^2} + \frac{4kQq}{r^2} = 0$$
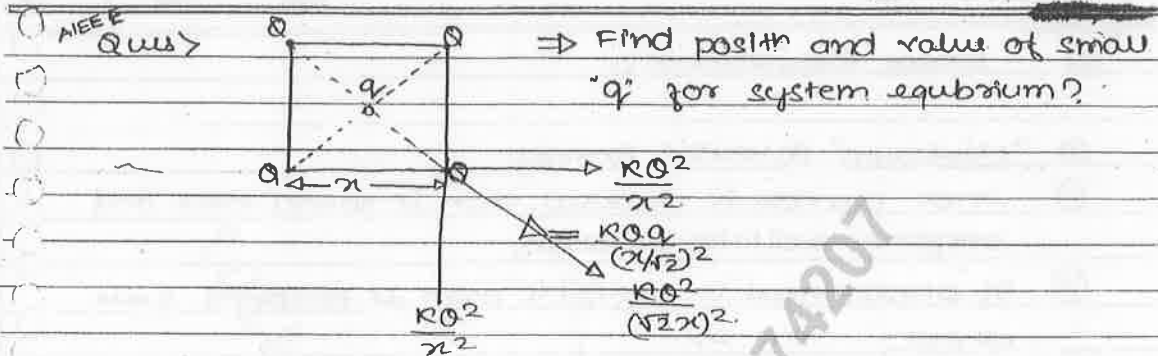
$$\frac{kQ^2}{r^2} = -\frac{4kQq}{r^2} \Rightarrow \boxed{q = -\frac{Q}{4}}$$



$$(F_a)_{\text{net}} = 0$$

$$\sqrt{2} \left(\frac{K0^2}{x^2} \right) + \frac{K0q}{(x/\sqrt{2})^2} + \frac{K0^2}{(\sqrt{2}x)^2} = 0$$


$$\frac{2K0q}{x^2} = -\frac{K0^2}{2x^2} - \frac{\sqrt{2}K0^2}{x^2}$$

$$= -\frac{K0^2}{x^2} \left(\frac{1}{2} + \sqrt{2} \right)$$

$$\frac{2K0q}{x^2} = -\frac{K0^2}{x^2} \left(\frac{2\sqrt{2}+1}{2} \right)$$

$$q = -\frac{0}{4} (2\sqrt{2}+1)$$

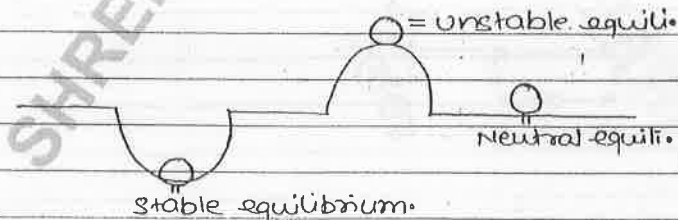$\star \Rightarrow$ TYPE OF EQUILIBRIUM :-



(B)

① Stable Equilibrium:-

(i) "Minimum" Potential Energy.

(ii) when particle is displaced, than it comes back and perform oscillatory motion.

(iii) If displacement is negligible than it performs S.H.M
where; $F \propto -x$

$$F = -Kx.$$

$$ma = -Kx$$

$$a = (-K/m)x.$$

S.H.M [$a = -\omega^2 x$] \Rightarrow standard.


② Unstable Equilibrium:-

(i) "Maximum" Potential Energy.

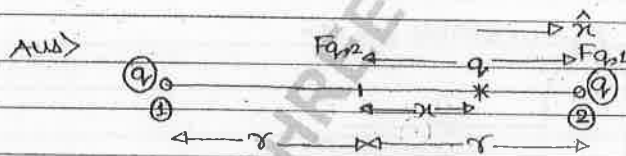(ii) when particle is displaced, than it moves away.



If mid particle is displaced slightly than calculate frequency of its oscillation?



$$\vec{F}_{q_1 2} = \frac{K q^2}{(r+x)^2} (\hat{x})$$

$$\vec{F}_{q_2 1} = \frac{K q^2}{(r-x)^2} (-\hat{x})$$

$$\begin{aligned}\vec{F}_{\text{net}} &= \vec{F}_{q_1,2} + \vec{F}_{q_1,2} \\ &= K q^2 \left[\frac{L}{(r+x)^2} - \frac{L}{(r-x)^2} \right] \hat{n} \\ &= K q^2 \left[\frac{-4rx}{(r^2-x^2)^2} \right] \hat{n}\end{aligned}$$

$$\vec{F}_{\text{net}} = - \frac{4Kq^2 \cdot x}{(r^2-x^2)^2} \hat{n}$$

\Rightarrow stable equilibrium.

$F_{\text{net}} \propto -x \Rightarrow$ oscillation motion

Given; $x \ll r$

$$\vec{F}_{\text{net}} = - \left(\frac{4Kq^2}{r^3} \right) x \hat{n}$$

$\vec{F}_{\text{net}} \propto -x \Rightarrow$ SHM.

$$m\vec{a} = - \left(\frac{4Kq^2}{r^3} \right) x \hat{n}$$


$$\vec{a} = - \left(\frac{4Kq^2}{mr^3} \right) x \hat{n}$$

S.H.M; $a = -\omega^2 x$


$$\therefore \omega = \sqrt{\frac{4Kq^2}{mr^3}}$$

$$f = \frac{\omega}{2\pi} = \frac{L}{2\pi} \sqrt{\frac{4 \left(\frac{L}{4\pi\epsilon_0} \right) q^2}{mr^3}}$$

$$f = \frac{q}{2\pi} \sqrt{\frac{L}{\pi\epsilon_0 mr^3}}$$


Ques > 
 ① Axial Direction.
 ② Equatorial Direction
 * If not given considered Axial Direction

Ans > ① Axial Direction:-

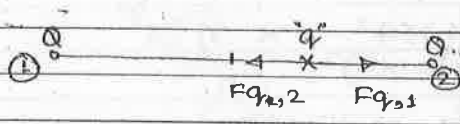


$\because r_1 > r_2$
 $\therefore F_{q_1,2} < F_{q_2,1}$
 $F_{net} \neq 0$ [∴ left-ward.]
 \Rightarrow stable equilibrium.

② Equatorial Direction:-

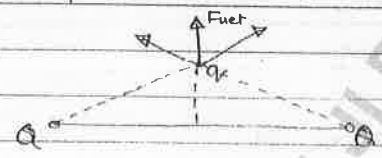

\Rightarrow Un-stable equilibrium.

Ques >

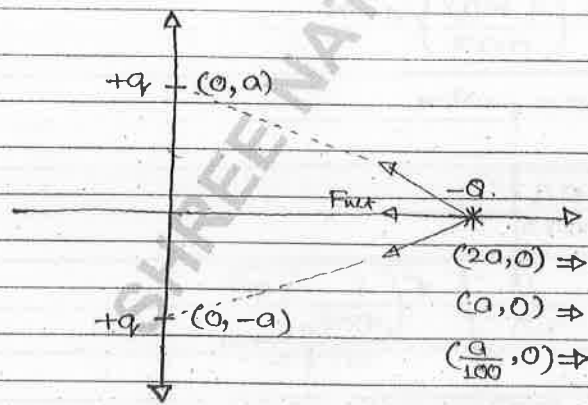


$(2a, 0) \Rightarrow$ Displ. not negligible = oscil.
 $(a, 0) \Rightarrow$ Displ. not negligible \Rightarrow oscil.
 $(\frac{a}{100}, 0) \Rightarrow$ Displ. negligible = SH.M

★ ⇒ ELECTRIC FIELD INTENSITY (E) :-


= It represents the strength of effect of charge at given point.

= It is equal to force acting on "unit positive test charge" placed at given point.
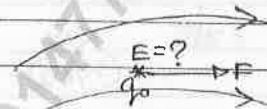
$$\vec{E} = \lim_{q_0 \rightarrow 0} \frac{\vec{F}}{q_0}$$



* Vector (HP to L.P)
+ve to -ve

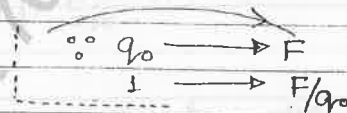


* Always from ⊕ve towards ⊖ve.

"Unit" :- $\frac{N}{C}$, $\frac{V}{m}$

E $\left\{ \begin{array}{l} \rightarrow \text{Uniform. (Position Independent)} \\ \rightarrow \text{Non-Uniform. (Position Dependent)} \end{array} \right.$

Ques) $\vec{E}_{room} = 20\hat{i} + 5\hat{j} - \hat{k} \Rightarrow \text{Non-Uniform.}$
 $\vec{E}_{room} = 2\hat{i} + 3\hat{j} - \hat{k} \Rightarrow \text{Uniform.}$

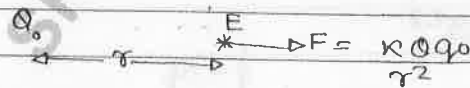① Electric Field (E) due to point charge :-




$$E = \lim_{q_0 \rightarrow 0} \frac{F}{q_0} = \lim_{q_0 \rightarrow 0} \frac{kQ_0q_0}{r^2 q_0}$$

$$\boxed{E = \frac{kQ}{r^2}} \quad \boxed{\vec{E} = \frac{kQ}{r^2} \hat{r}} \Rightarrow \text{vector Form.}$$

$$2E \times \frac{\sqrt{2}}{2} \cdot \frac{\sqrt{2}}{2}$$

Date _____ Page _____

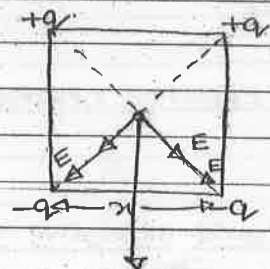
Ques)  Ecentre = ?

$$E_{\text{cent}} = \sqrt{2} E (2E)$$

$$= 2\sqrt{2} \frac{kq}{(\frac{x}{\sqrt{2}})^2}$$

$$= 4\sqrt{2} \frac{kq}{x^2} \quad \downarrow \text{(vt. downward)}$$


Ques)  Ecentre = ?

Ans) 

$$E_{\text{net}} = \sqrt{2} E$$

$$= \sqrt{2} \left\{ \frac{kq}{(\frac{x}{\sqrt{2}})^2} \right\}$$

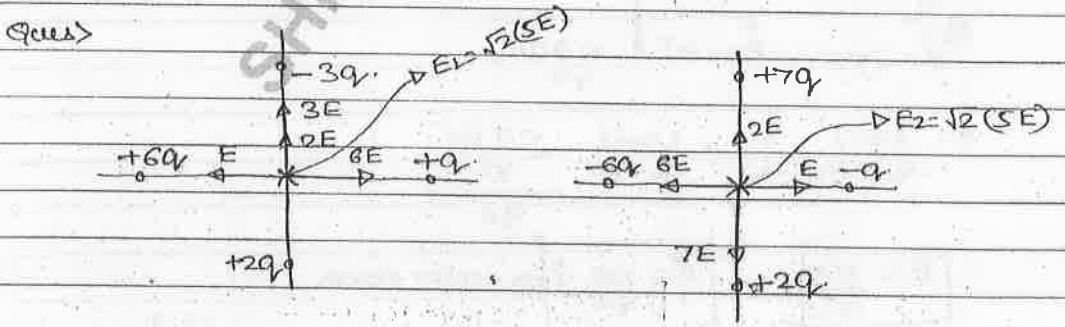
$$= 2\sqrt{2} \frac{kq}{x^2} \quad \uparrow \text{vt. upward.}$$



Each charges is at same distant from origin?

- Aus >
- ① $E_1 = E_2$ ↘
 - ② $\vec{E}_1 = \vec{E}_2$ ✗
 - ③ $\vec{E}_1 = -\vec{E}_2$ ↘

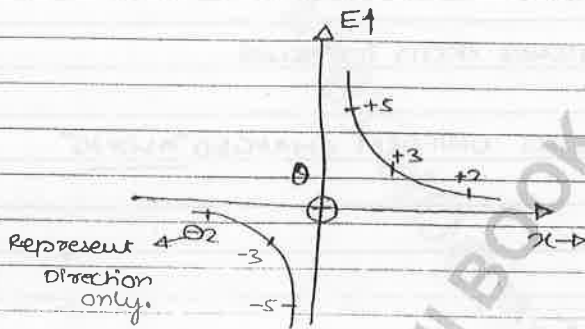Ques > $E = \frac{kQ}{r^2}$; $\propto \frac{1}{r^2}$




⇒ when moving away from charge, electric field continuously decreases

eg:- $-3 \text{ V/m} > +2 \text{ V/m}$
 $-1 \text{ V/m} < -5 \text{ V/m}$


Ques > "E" vs "r"

① +Q & +Q

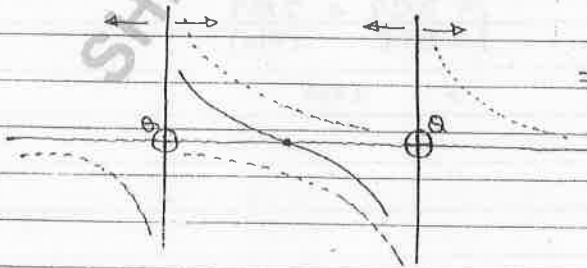


⇒ Electric field 1st decreases than increases.

(ii) $+Q$ \times $-Q$

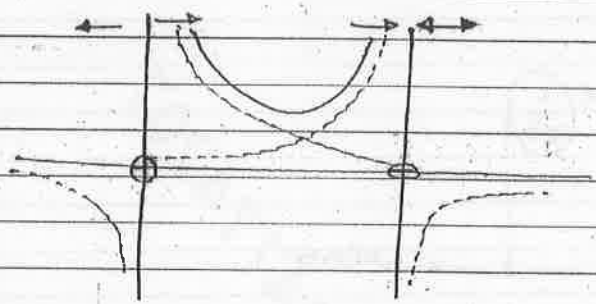


\Rightarrow Electric field \downarrow as distance increases

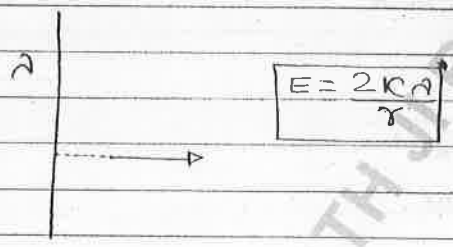(iii) ELECTRIC FIELD DUE TO UNIFORM CHARGED "ALONG" LONG WIRE :-



Ques)

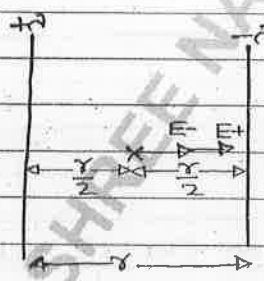


$E_{mid} = ?$

$$\begin{aligned}
 &= E_+ + E_- \\
 &= \frac{2k\sigma}{r/2} + \frac{2k\sigma}{r/2} \\
 &= \frac{8k\sigma}{r}
 \end{aligned}$$


Ques → Uniform charged arc :-

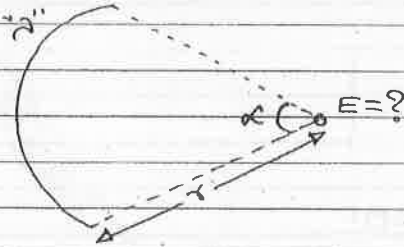(III) ELECTRIC FIELD DUE TO UNIFORM-CHARGED ARC?



$$E = \frac{2k\lambda \sin\left(\frac{\alpha}{2}\right)}{r}$$


case: (I) :-

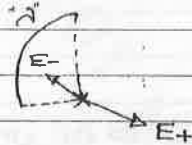

$\alpha = 90^\circ$

$$E = \frac{\sqrt{2}k\lambda}{r}$$

case: (II) :-

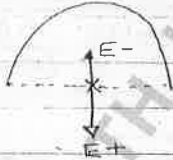


$\alpha = 180^\circ$

$\sin 180$

$$E = \frac{2k\lambda}{r}$$

case: (III) :-

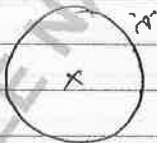


$\alpha = 360^\circ$

$$E = \frac{2k\lambda \sin\left(\frac{360}{2}\right)}{r}$$

$$E = 0$$

*** Ques →

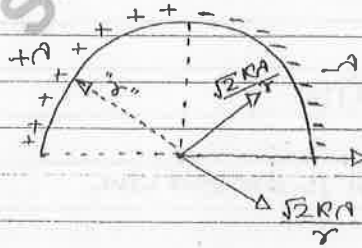


$E_{center} = ?$

$$E_{net} = \sqrt{2} \left(\frac{\sqrt{2}k\lambda}{r} \right)$$

$$E_{net} = \frac{2k\lambda}{r}$$

Ques ✓

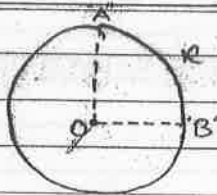of $E_{AKB} = E [R \text{ to } O]$ $E_{\text{resulting ring}} = ?$

A PD

$$\text{Ans} \rightarrow \vec{E}_{\text{ring}} = 0$$


$$\vec{E}_{AKB} + \vec{E}_{\text{resulting ring}} = 0$$

$$\vec{E}_{\text{resulting ring}} = -\vec{E}_{AKB}$$

$$= E (O \text{ to } R)$$

Q

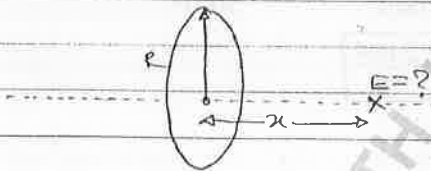ELECTRIC FIELD AT AXIAL POINT OF UNIFORM CHARGED RING:-



$$E_{\text{axis}} = \frac{kQx}{(R^2+x^2)^{3/2}}$$

$$\vec{E}_{\text{axis}} = \frac{kQ}{(R^2+x^2)^{3/2}} \vec{x}$$

case: (I) :- At centre ($x=0$):-

$$E_{\text{centre}} = 0$$

case: (II) :- Nearby point ($x \ll R$):-

$$E = \frac{kQ}{R^3} x \Rightarrow [E \propto x] \text{ :- straight line,}$$

$$\frac{2kq}{3\sqrt{3}R^2}$$

Date _____ Page _____

case:- (III) :- For Away Points :- ($x \gg R$)

$$E = \frac{kQ}{x^2} \Rightarrow \boxed{E \propto \frac{1}{x^2}} \Rightarrow \text{Hyperbola.}$$


case:- (IV) :- For E_{\max} :-

$$\frac{dE}{dx} = 0$$

$$\boxed{x = \pm \frac{R}{\sqrt{2}}}$$


$$E_{\max} = \frac{kQ(R/\sqrt{2})}{(R^2 + \frac{R^2}{2})^{3/2}} = \frac{kQ(R/\sqrt{2})}{(\frac{3R^2}{2})^{3/2}} = \frac{kQ(R/\sqrt{2})}{(\frac{3R^2}{2})^{3/2} (\frac{\sqrt{3}R}{\sqrt{2}})}$$
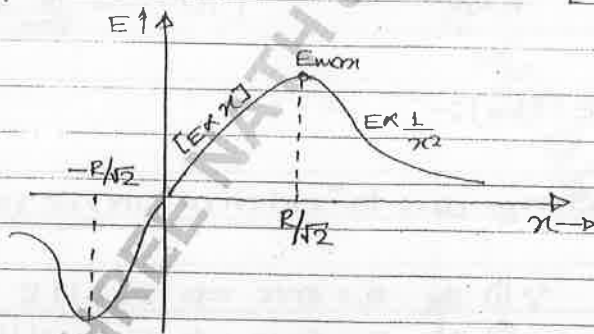
$$\boxed{E_{\max} = \frac{2kQ}{3\sqrt{3}R^2}}$$



Ques) For a uniformly charged ring (Q, R) of small (section) element, (dl) is removed from ring then Electric field at centre due to remaining part?

Ans >

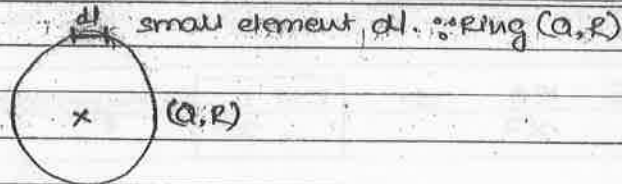

$$\therefore \vec{E}_{ring} = 0$$

$$\vec{E}_{dl} + \vec{E}_{ring} = 0$$

$$\therefore \vec{E}_{ring} = -\vec{E}_{dl}$$

$$\vec{E}_{ring} = E_{dl}$$

$$= \frac{k(dq)}{R^2}$$

$$= \frac{k \left(\frac{Q}{2\pi R} dl \right)}{R^2}$$

$$\therefore E_{ring} \text{ part } \propto \frac{1}{R^3}$$

$$\left\{ \begin{array}{l} 2\pi R \rightarrow Q \\ 1 \rightarrow \frac{Q}{2\pi R} \\ dl \rightarrow \frac{Q}{2\pi R} dl \end{array} \right.$$

★ \Rightarrow ELECTRIC FORCE (F_e):-


\rightarrow It is force on charge due to "external Electric field."

$$\boxed{F_e = q \cdot E}$$

$$\boxed{\vec{F}_e = q \cdot \vec{E}}$$


$$\therefore \text{(i) if } q = +ve \Rightarrow F_e \parallel E$$
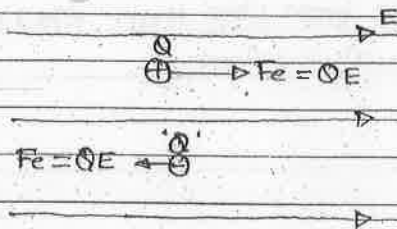
$$\text{(ii) if } q = -ve \Rightarrow F_e \text{ Antiparallel } E$$



* Ques > Find direction and magnitude of Required electric field to balance weight of electron in air?

Ans >

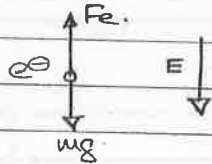

At Balance:-

$$F_e = mg$$


$$qE = mg$$

$$E = \frac{mg}{q} = \frac{9.1 \times 10^{-31} \times 10}{1.6 \times 10^{-19}}$$


$$= 5.6 \times 10^{-11} \text{ N/C}$$

* Ques > A proton is balanced in external electric field, if dirⁿ of Electric field is reverse than find accⁿ of Proton?

Ans >

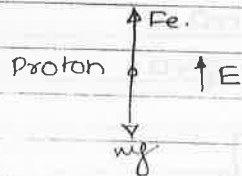

$$F_e = mg \dots \text{--- (1)}$$

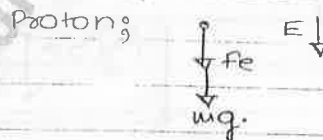


$$F_{\text{net}} = F_e + mg = mg + mg = 2mg$$

$$a = \frac{F}{m} = 2g$$

** Ques
AIPMT

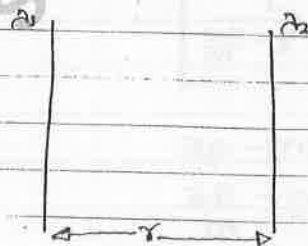Find force on unit length of each wire :-



$$\frac{F_{2,1}}{L_2} = \frac{q_2}{L_2} E_1$$

$$= (A_2) \left(\frac{2k A_1}{r} \right)$$

$$= \frac{2k A_1 A_2}{r}$$


Ques > simple Pendulum



$$T = 2\pi \sqrt{\frac{l}{g_{eff}}}$$

* \Rightarrow $g_{effective}$:- Acceleration corresponding to net force except Tension.

(i)

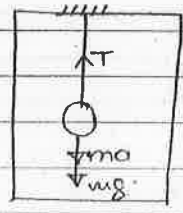


$$F_{net} = mg + ma$$

$$g_{eff} = \frac{F}{m} = g + a$$

$$T = 2\pi \sqrt{\frac{l}{g+a}}$$

(ii)

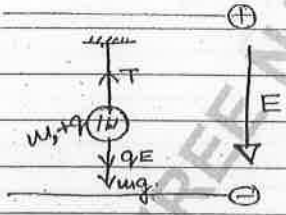


$$F_{net} = mg + qE$$

$$g_{eff} = g + \frac{qE}{m}$$

$$T = 2\pi \sqrt{\frac{l}{g + \frac{qE}{m}}}$$


(iii)

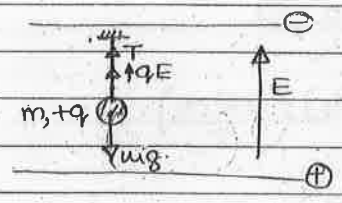

$$F_{net} = mg - qE$$

$$g_{eff} = g - \frac{qE}{m}$$
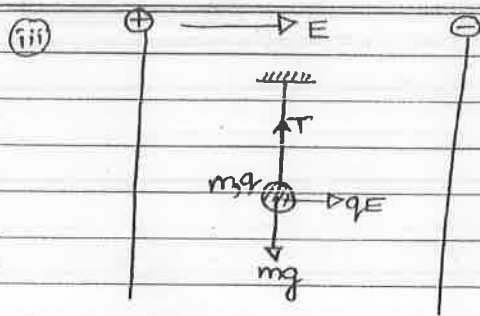
$$T = 2\pi \sqrt{\frac{l}{g - \frac{qE}{m}}}$$



$$F_{net} = \sqrt{(mg)^2 + (qE)^2}$$

$$g_{eff} = \sqrt{g^2 + \left(\frac{qE}{m}\right)^2}$$

$$T = 2\pi \sqrt{\frac{l}{\sqrt{g^2 + \left(\frac{qE}{m}\right)^2}}}$$

Ques

A uniformly charged ring (+Q, r) an electron is placed at its centre, if e^- is displaced slightly then calculate angular frequency of its oscillation?

Ans




$$E_{cent} = 0$$

$$\begin{aligned} \text{At centre } F_e &= qE \\ &= (-e)(0) \\ &= 0 \end{aligned}$$

[e^- is in equilibrium]

⊥ sq displace by "x"

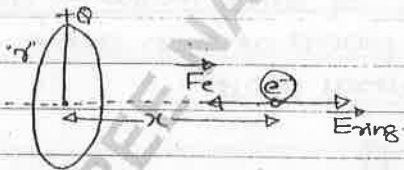

$$\begin{aligned} \vec{F}_e &= q\vec{E} \\ &= (-e) \left\{ \frac{kQ}{(\sigma^2 + x^2)^{3/2}} \right\} \vec{x} \end{aligned}$$

$$\vec{F}_e = - \left\{ \frac{kQe}{(\sigma^2 + x^2)^{3/2}} \right\} \vec{x}$$

$F_e \propto -x \Rightarrow$ oscillation (so only)

② \because given $x \ll r$.

$$\vec{F}_e = - \left(\frac{kQq}{r^3} \right) \vec{x}$$

$$F_e \propto -x \quad (\text{SHM})$$

$$a = - \left[\frac{kQq}{mr^3} \right] x$$


$$a = -\omega^2 x.$$

$$\therefore \omega = \sqrt{\frac{kQq}{mr^3}}$$

★ \Rightarrow NEUTRAL POINT:-

\rightarrow where $E_{\text{net}} = 0$.

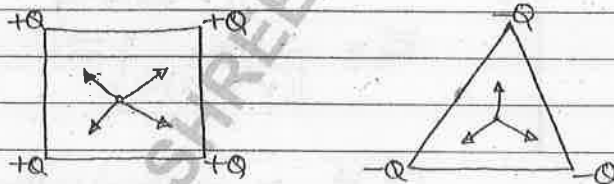\rightarrow In any regular Polygon, if "same magnitude and same nature" charges is placed at each corner then geometrical centre is Neutral Point.



\rightarrow Neutral Point and equilibrium point are same point.

Ques) $+10c$ $\xrightarrow{E_{10}}$ x $\xrightarrow{E_{20}}$ $+20c$ Find Neutral point?
 \xleftarrow{x} $\xrightarrow{80cm}$ $\xrightarrow{\quad}$

Ans) Right side of $+10c$;

$$E_{10} = E_{20}$$

$$\frac{K(10)}{x^2} = \frac{K(20)}{(80-x)^2}$$

$$\frac{1}{x^2} = \frac{2}{(80-x)^2}$$

$$\frac{1}{x} = \frac{1.4}{80-x}$$


$$80-x = 1.4x.$$

$$80 = 2.4x.$$

$$x = \frac{800}{2.4} = 33.33 \text{ cm}$$

★ \Rightarrow ELECTRIC POTENTIAL :- (V) :-

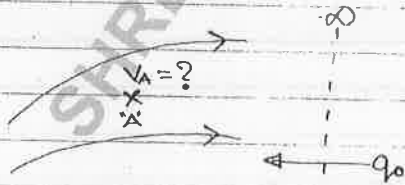\rightarrow It is equal to work done in shifting unit ^+ve q charge from reference to given point, where Kinetic Energy of charge should be constant.



$$q_0 \text{ ————— work} = W_{\infty \rightarrow A}$$

$$+1 \text{ ————— work} = \frac{W_{\infty \rightarrow A}}{q_0}$$

$$V_A = \frac{W_{\infty \rightarrow A}}{q_0}$$

$$V_A = - \int_{\infty}^A \vec{E} \cdot d\vec{r}$$

\Rightarrow q_0 scalar Quantity

- Unit:- ① MKS = J/c, volt.
 ② CGS = stat V.


$$1V = \frac{1}{30} \text{ stat V}$$

- ∴ $V_{\text{reference}} = 0$
- ∴ $V_{\text{at position}} = 0$
- ∴ $V_{\text{earth}} = 0$

→* Potential is defined for "conservative fields" only.

→* Potential depend on reference, so it is relative parameter.

eg:-

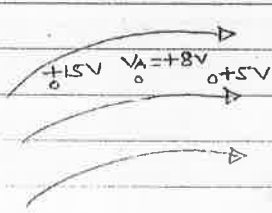

① Reference = ∞ position

$$V_A = +8V$$

② Reference = $+8V$

$$V_A = 0$$

③ Reference = $+5V$

$$V_A = +3V$$

④ Reference = $+15V$


$$V_A = -7V$$

Ques> which is more:-

① $-1V > -3V$

② $+3V > +3V$


(I) Potential due to Point charge :-

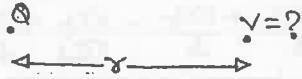

$$V = \frac{kQ}{r}$$

*** [Charge must be with sign.]

Ques)

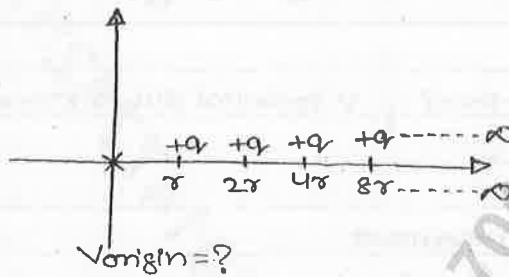

Ans)

$$V_{\text{origin}} = \frac{kq}{r} + \frac{kq}{2r} + \frac{kq}{4r} + \frac{kq}{8r} + \dots \infty$$

$$= \frac{kq}{r} \left[1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \dots \infty \right]$$

*** [Geometric Progression]


$$S_{\infty} = \frac{a}{(1-r)} \quad (r < 1)$$

(keep it with its sign)

$$S_{\infty} = \infty \quad (r \geq 1)$$

$$= \frac{2kq}{r}$$

Ques)

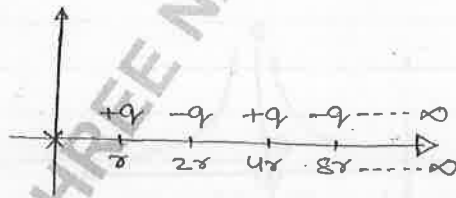


Ans)

$$V_{\text{origin}} = \frac{kq}{r} - \frac{kq}{2r} + \frac{kq}{4r} - \frac{kq}{8r} + \dots$$

$$= \frac{kq}{r} \left[1 - \frac{1}{2} + \frac{1}{4} - \frac{1}{8} + \dots \right]$$

$$= \frac{kq}{r} \left[\frac{1}{1 - (-1/2)} \right] = \frac{2}{3} \left(\frac{kq}{r} \right)$$


Ques >

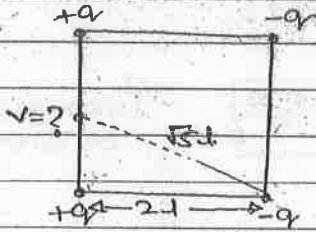

$$V = \frac{kq}{a} + \frac{kq}{a} - \frac{kq}{\sqrt{2}a} - \frac{kq}{\sqrt{2}a}$$

$$= \frac{2kq}{a} \left(1 - \frac{1}{\sqrt{2}} \right)$$

* Ques >

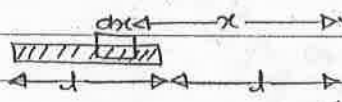

∴ Potential due to Element?

Ans > Potential due to element

$$= \frac{k \left(\frac{Q}{2a} dx \right)}{x}$$


$$V_{int} = \int_a^{2a} \frac{kQ}{2a} \frac{dx}{x} = \frac{kQ}{2a} \left[\log_e x \right]_a^{2a}$$

$$= \frac{kQ}{2a} [\log_e 2a - \log_e a]$$


$$= \frac{kQ}{2a} \log_e 2$$

** Ques >
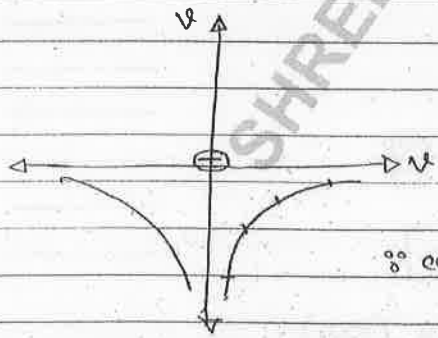
$$V = \frac{kQ}{r} \propto \frac{1}{r} \Rightarrow$$




∴ continuous Increasing.

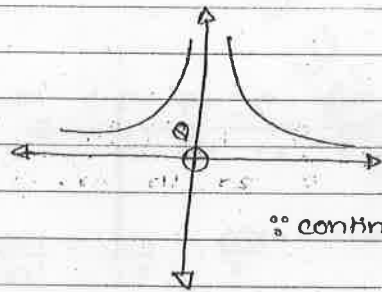


∴ continuous Decreasing.

⊗ ⇒ "V" v/s "r"

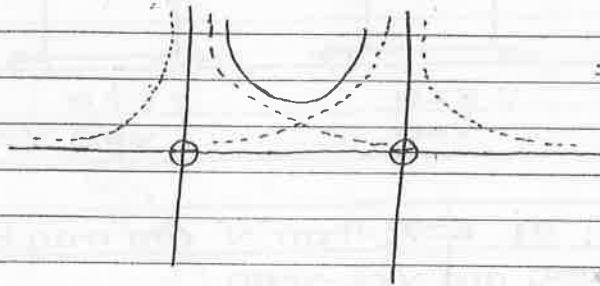


⇒ 1st Decreases than Increases.

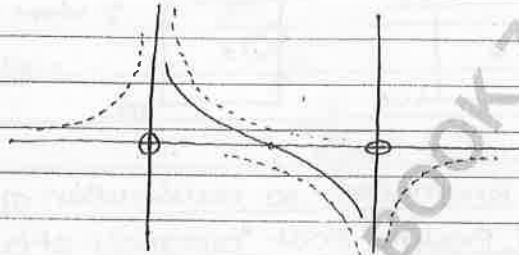


⇒ constantly decreasing.

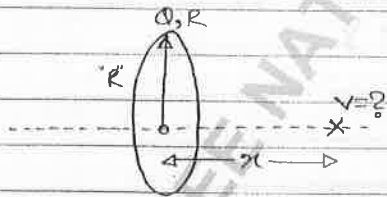Ⓜ POTENTIAL AT AXIAL POINTS OF CHARGED RING:-




$$\Rightarrow V_{axis} = \frac{KQ}{\sqrt{R^2+x^2}}$$
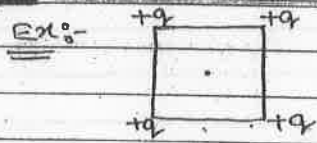
$$\Rightarrow \left[\begin{array}{l} V_{centre} = \frac{KQ}{R} \neq 0 \\ E_{centre} = 0 \end{array} \right]$$




$$\therefore E = 0$$

$$V \neq 0$$

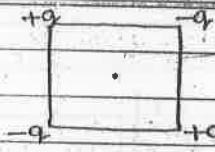

$$\therefore E = 0$$




$$V = 0$$

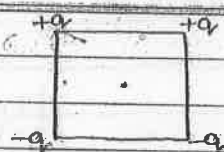

$$\therefore E \neq 0$$

$$V = 0$$

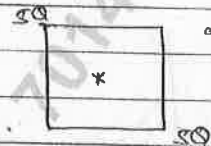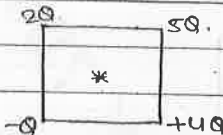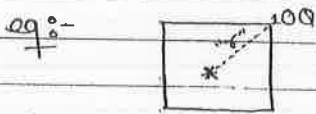⇒ At any point; if $E = 0$; then " V " can may be zero or non-zero and vice-versa.




$$\therefore V_{\text{cent}} = R(10q)$$

$$= \text{same.}$$

→ Potential is a scalar parameter, so distribution of charge doesn't matter, provided that "distances should be same."

Ques →

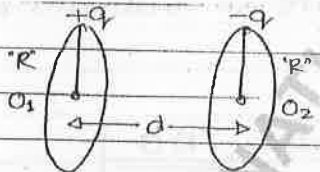

→ Potential Difference b/w centre ?

Ans →


$$V_{O1} = \frac{kq}{R} - \frac{kq}{\sqrt{R^2 + d^2}}$$

$$V_{O2} = -\frac{kq}{R} + \frac{kq}{\sqrt{R^2 + d^2}}$$

$$V_{O1} - V_{O2} = 2 \left[\frac{kq}{R} + \frac{kq}{\sqrt{R^2 + d^2}} \right]$$

⊛ ⇒ POTENTIAL DIFFERENCE :- (P.D) :-

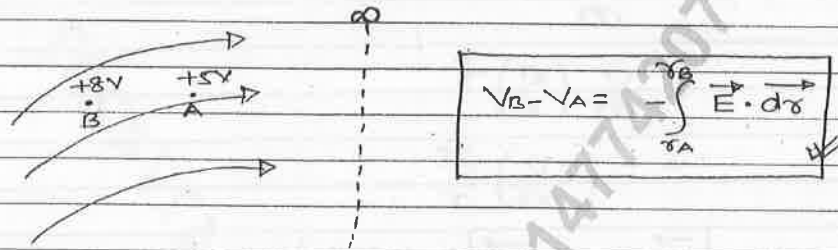It is equal to work done, in shifting unit \oplus ve charge from "one point" to "other" keeping its R.E constant.



Quis :-	Reference = ∞ posn	Reference = +2V
	$V_A = +5V$	$V_A = +3V$
	$V_B = +8V$	$V_B = +6V$
	$V_B - V_A = +3V$	$V_B - V_A = +3V$

** NOT :- Potential difference (P.D) does not depend on Reference so it is "absolute parameter."

⊛ ⇒ Relation b/w E & V :-

→ "Electric field" is Negative of "Potential gradient."

Type 1 :- If $V = f(r) \Rightarrow E = ?$

$$E = -\frac{dV}{dr}$$

$$\vec{E} = -\frac{dV}{dr} \hat{r}$$

Ques) In space; Potential is $[V = \frac{R}{r}]$ then $E = ?$,
at $\vec{r} = 2\hat{i} + 3\hat{j} + 6\hat{k}$

Ans) $\vec{E} = -\frac{dV}{dr} \vec{r}$

$$= -\frac{d}{dr} \left(\frac{R}{r} \right) \vec{r}$$

$$= - \left(-\frac{R}{r^2} \right) \vec{r}$$

$$\boxed{\vec{E} = \frac{R \vec{r}}{r^3}} \Rightarrow \text{Non-uniform Electric field.}$$

$$\vec{E}(2\hat{i} + 3\hat{j} + 6\hat{k}) = \frac{R}{7^3} (2\hat{i} + 3\hat{j} + 6\hat{k})$$

$$\vec{E}(3\hat{i} - 4\hat{k}) = \frac{R}{5^3} (3\hat{i} - 4\hat{k})$$

Type: ②:- If $V = f(x, y, z) \Rightarrow E = ?$

$$\vec{E} = - \left[\hat{i} \frac{\partial V}{\partial x} + \hat{j} \frac{\partial V}{\partial y} + \hat{k} \frac{\partial V}{\partial z} \right]$$

Ques) $V = 6x - 8xy^2 + 6yz - 8y - 4z^2 \Rightarrow \vec{E}_{(0,0,0)} = ?$

Ans) $\frac{\partial V}{\partial x} = 6(1) - 8y^2(1) + 0 - 0 - 0$

$$\frac{\partial V}{\partial y} = 0 + 16xy + 6z - 8 - 0 - 0 - 0$$

$$\frac{\partial V}{\partial z} = 0 - 0 + 6y(1) - 0 - 4(2z)$$

⇒ Depends on variable position, so Non-uniform

$$\vec{E} = - [i(6-8y^2) + j(-16xy+6z-8) + k(6y-8z)]$$


A $\vec{E}_{origin} = - [i(6) + j(-8) + k(0)]$
 $= -6i + 8j$

$$|E| = \sqrt{6^2 + 8^2} = 10 \text{ unit}$$

TYPE:-(3):- If $V-x$ graph $\Rightarrow E=?$

$$E = -\frac{dv}{dx}$$

$$E = -\text{slope}$$

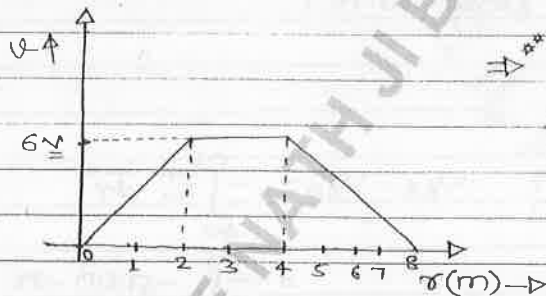

⇒ At $x = 2\text{m}$ & 4m , graph is not differentiable, so electric field is "undefined" at these points.

$$\text{slope} = \frac{y_2 - y_1}{x_2 - x_1}$$

$$E = -(\text{slope})$$

① $0-2 \Rightarrow \frac{6-0}{2-0} = +3 \quad -3 \text{ V/m.}$

② $2-4 \Rightarrow \frac{6-6}{4-2} = 0 \quad 0$

③ $4-8 \Rightarrow \frac{0-6}{8-4} = -1.5 \quad +1.5 \text{ V/m.}$

TYPE: (4) :- If $E = f(r) \Rightarrow P.D = ?$

$$P.D = - \int \vec{E} \cdot d\vec{r}$$

$$V_B - V_A = - \int_{r_A}^{r_B} \vec{E} \cdot d\vec{r}$$

$$V_A - V_B = - \int_{r_B}^{r_A} \vec{E} \cdot d\vec{r}$$

∴ If "E" is uniform $\Rightarrow P.D = - \vec{E} \cdot d\vec{r}$

Ques > Electric field due to charged wire is $\frac{-5000}{r}$ volt/m.

Then calculate Potential difference between 30cm and 60cm distance from wire?

Ans > $E = \frac{-5000}{r}$ volt/m

$$V = -5000 \int \frac{1}{r} \quad V_{60} - V_{30} = - \int_{0.3}^{0.6} \vec{E} \cdot d\vec{r}$$

$$= - \int_{0.3}^{0.6} \frac{-5000}{r} \cdot dr$$

$$= +5000 [\log_e r]_{0.3}^{0.6}$$

$$\therefore \log_e a - \log_e b = \log_e \frac{a}{b}$$

$$= 5000 \log_e 2$$

$$\text{So; } V_{60} - V_{30} = 3465 \text{ V}$$

$$= 5000 \times 0.693$$

$$V_{30} - V_{60} = -3465 \text{ V}$$

$$= 3465 \text{ volt.}$$

*∴ P.D = 3465 volt (always +ve)

⊗ $V_{60} > V_{30}$

* If $V_{30} = -2000$, then find $V_{60} = ?$

$$V_{60} - V_{30} = +3465 \Rightarrow V_{60} - (-2000) = +3465$$

$$V_{60} = +3465 - 2000$$

$$= 1465$$

* Ques \rightarrow In space electric field is $= 2\hat{i} + 3\hat{j} + 4\hat{k}$,
and $\vec{r}_a = \hat{i} - 2\hat{j} + \hat{k}$ and $\vec{r}_b = 2\hat{i} + \hat{j} - 2\hat{k}$.
Then; $V_a - V_b = ?$

Ans \rightarrow $V_a - V_b = -\vec{E} \cdot d\vec{r}$

$$V_a - V_b = -\vec{E} \cdot (\vec{r}_a - \vec{r}_b)$$

$$= -(2\hat{i} + 3\hat{j} + 4\hat{k}) \cdot (-\hat{i} - 3\hat{j} + 3\hat{k})$$

$$= -[-2 - 9 + 12]$$

$$= -1 \text{ volt.}$$

* $V_a - V_b = -1 \text{ volt.}$

* $V_b - V_a = +1 \text{ volt.}$

* P.D = +1 volt. (always +ve)

* $V_b > V_a$

* If $V_b = +3 \text{ volt}$, then find $V_a = ?$

$$\Rightarrow V_a - 3 = -1$$

$$V_a = -1 + 3 = +2 \text{ volt.}$$

Type: (5) :- If $E = f(x, y, z) \Rightarrow$ P.D = ?

$$P.D = - \int \vec{E} \cdot d\vec{r}$$

$$(E_x \hat{i} + E_y \hat{j} + E_z \hat{k}) (dx \hat{i} + dy \hat{j} + dz \hat{k})$$

$$P.D = - \int E_x \cdot dx - \int E_y \cdot dy - \int E_z \cdot dz$$

Ques> Due to a charge wire at origin, Electric field is:

$$\vec{E} = \frac{100}{x^2} \hat{j} \quad \frac{\text{volt}}{\text{m}}$$

$$V_{x=20\text{cm}} - V_{x=10\text{cm}} = - \int_{0.1}^{0.2} \frac{100}{x^2} dx$$

$$V_{20} - V_{10} = -100 \left[\frac{-1}{x} \right]_{0.1}^{0.2}$$

$$= +100 \left[\frac{1}{0.2} - \frac{1}{0.1} \right]$$

$$= +100 [5 - 10]$$

$$= -500$$

$$V_{20} - V_{10} = -500 \text{ volt}$$



$$V_{10} - V_{20} = 500 \text{ volt}$$

$$P.D = 500 \text{ volt (always in +ve)}$$

TYPE :- (B) :- If $E-x$ graph \Rightarrow P.D = ?

$$P.D = - \int \vec{E} \cdot d\vec{x}$$

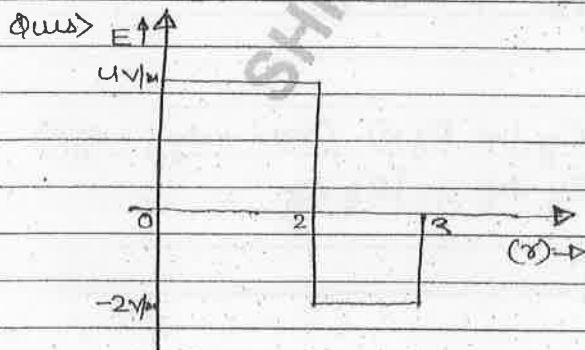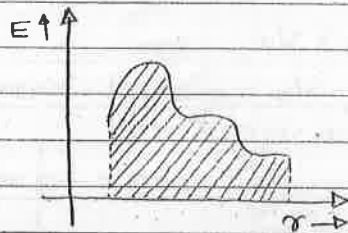\therefore P.D \equiv Area under the curve.



$$\textcircled{1} (P.D)_{0-2}$$

$$\textcircled{2} (P.D)_{2-3}$$

$$\textcircled{3} (P.D)_{0-3}$$

Ans \Rightarrow ① (P.D)₀₋₂ = $2 \times 4 = 8$ volt.

② (P.D)₂₋₃ = $-2 \times 1 = -2$ volt


③ (P.D)₀₋₃ = $+8 - 2 = 6$ volt.

$\star \Rightarrow$ Equipotential surface :-


① It has same potential at each point.

*② "conductors" are equipotential surface, it means potential at surface and all inside points are same


① spherical :-

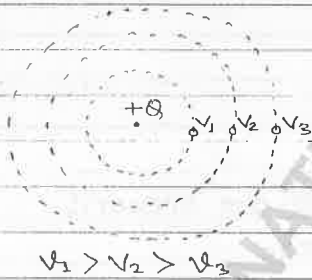

② cylindrical :-

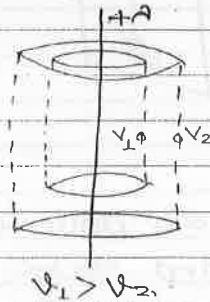


③ Plane surface :-

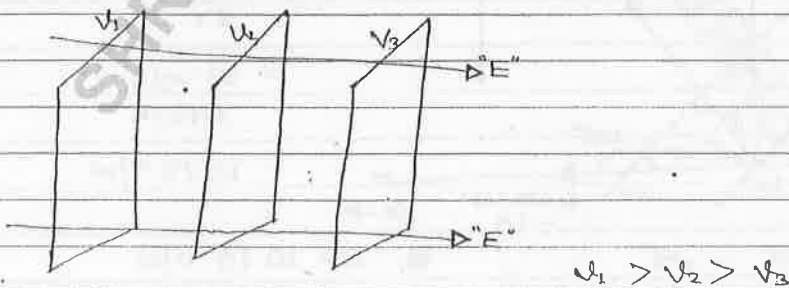

⊛ Properties of Equipotential surface:-

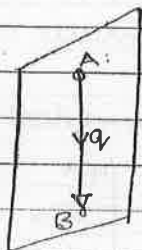- ① Never intersect each other.
- ② Electric field and Lin of Force are always \perp to equipotential surface.
- ③ Work- done for moving a charge b/w two points of Equipotential surface is always zero.




$$\because W = q(V_B - V_A)$$

$$\because V_A = V_B$$

$$\therefore \boxed{W = 0}$$

Ques
W

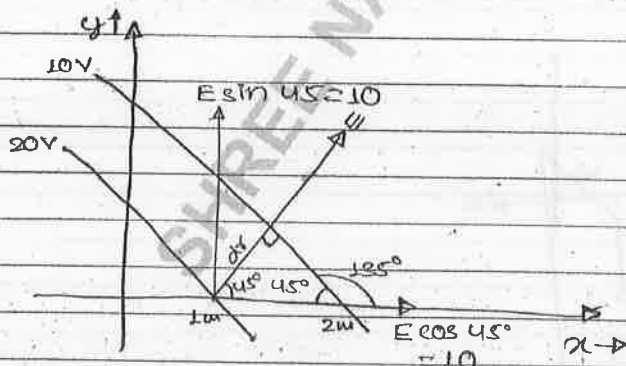Two plane equipotential surface are shown:-
Find electric field b/w surface:-



$$|E| = \frac{dv}{dr}$$

$$= \frac{10 \text{ volt}}{1/\sqrt{2} \text{ m}}$$

$$10\sqrt{2} \text{ V/m}$$



$$\sin 45 = \frac{dr}{1}$$

$$dr = \frac{1}{\sqrt{2}} \text{ m}$$

$$\therefore E = 10\sqrt{2} \text{ v/m}$$

(At 45° from $+x$ axis)
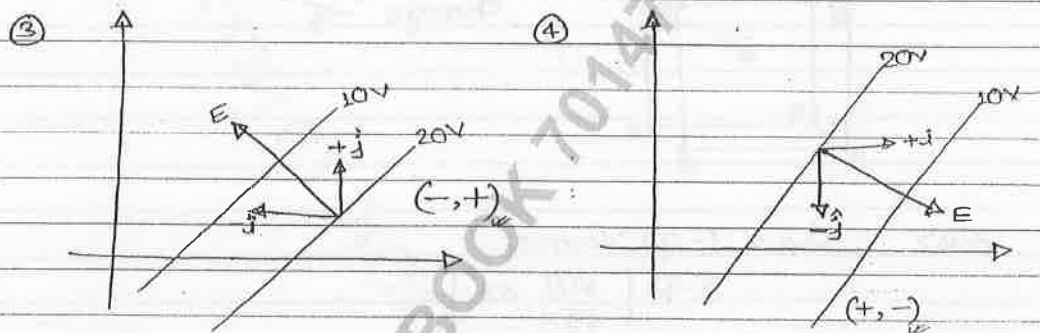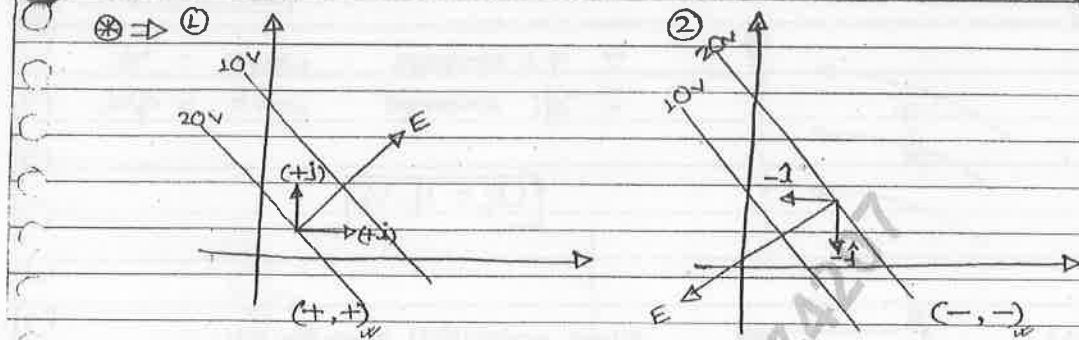
$$\therefore \vec{E} = 10\hat{i} + 10\hat{j}$$




☆ ⇒ ELECTROSTATIC POTENTIAL ENERGY (U):-


- (i) It is defined for "conservative fields only".
- (ii) It depends on reference; so a "relative parameter".
- (iii) It is energy of system due to its configuration.

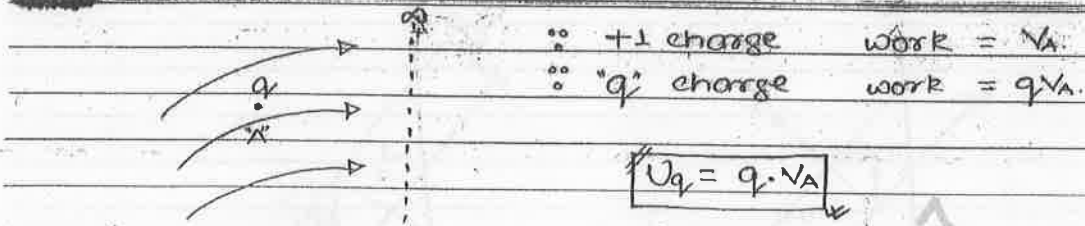(i) Potential Energy of single point charge:-

It is equal to workdone, in shifting that charge from reference to its position.



* AIPMT
 Ques >

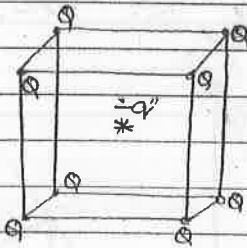

Find potential energy of charge "-q"

Ans > $U_q = (-q) V_{\text{centre}}$
 $(-q) \left[\frac{kq \times 8}{\frac{\sqrt{3}x}{2}} \right]$
 $= -16 kq^2 / \sqrt{3}x$

① Potential energy of system having 2 point charges:-



① $U = \frac{kq_1 q_2}{r}$

② $U_{\infty} = \frac{kq_1 q_2}{\infty} = 0$

* $\Rightarrow U = \oplus ve, \ominus ve, \text{ zero.}$

** $\Rightarrow -3J > -5J$

AIIEE
** Ques >



if $r \downarrow$

$$\Rightarrow U (+ve) \uparrow$$

$$\Rightarrow P.E \uparrow$$



if $r \downarrow$

$$\Rightarrow U (-ve) \uparrow$$

$$\Rightarrow P.E \downarrow$$


** \rightarrow when two charges are brought close to each other than Potential energy may "increase" or "Decrease".

(III) Potential Energy of system having "n" point charges:

It is algebraic sum of all Potential Energy of all possible pairs of 2-point charges.

$$\Rightarrow \text{no. of possible pairs} = \frac{n(n-1)}{2}$$

*** Ques >

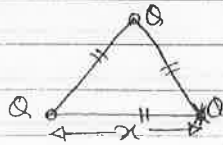


\Rightarrow Find potential energy of any one charge:-

$$\begin{aligned} \text{Ans} > \text{(i)} \quad U_0 &= [Q] \left[\frac{kQ}{x} + \frac{kQ}{x} \right] \\ &= \frac{2kQ^2}{x} \end{aligned}$$

$$\begin{aligned} \text{(ii)} \quad U_{\text{system}} &= \frac{kQ^2}{x} + \frac{kQ^2}{x} + \frac{kQ^2}{x} \\ &= \frac{3kQ^2}{x} \end{aligned}$$


-q

Date _____ Page _____

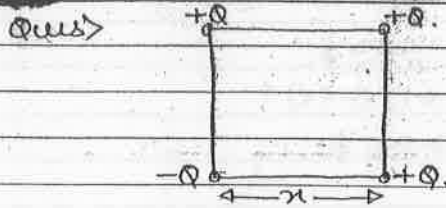

$$U_{\text{system}} = \frac{-kQ^2}{x} + \frac{kQ^2}{x} + \frac{kQ^2}{x} - \frac{kQ^2}{x} - \frac{kQ^2}{\sqrt{2}x} + \frac{kQ^2}{\sqrt{2}x}$$

$$= 0$$

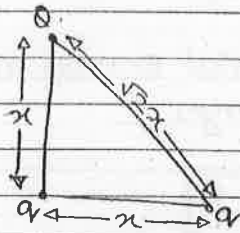III
Ques >
 $U_{\text{system}} = 0$ then find $Q = ?$

Ans >


$$kq^2 \frac{1}{x} + \frac{kQq}{x} + \frac{kQq}{\sqrt{2}x} = 0$$

$$kq^2 \cdot \frac{(1+1)}{\sqrt{2}} = -kq^2 \frac{1}{x}$$

$$Q \left(\frac{\sqrt{2}+1}{\sqrt{2}} \right) = -q$$

$$Q = \frac{-\sqrt{2}q \times \sqrt{2}}{\sqrt{2}+1} = \frac{-2q}{2+\sqrt{2}}$$

Ques >

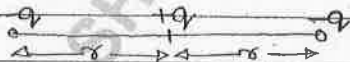

Ans >

$$U_{\text{system}} = -\frac{kq^2}{r} + \frac{kq^2}{r} + \frac{kq^2}{2r} = \frac{-2kq^2 + kq^2}{2r}$$

$$= \frac{-kq^2}{2r}$$

Ques > / w


★ ⇒ WORK DONE BY ELECTROSTATIC FIELD:-

when conservative field works, energy is spent so stored potential energy decreases.

$$*// W_{\text{conservative}} = -\Delta U \quad *(\text{always})$$

$W_{\text{elect. field}} = -\Delta U$ $= -q (\Delta V)$ $= -q (V_f - V_i)$
--

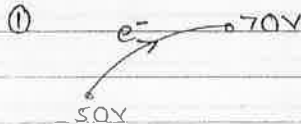Ques > calculate work done by electric field if:-



$$W_{50 \rightarrow 70} = -q (V_f - V_i)$$

$$= -(-e) (70V - 50V)$$

$$= +20eV.$$



$$W_{70 \rightarrow 50} = -(-e) (50V - 70V)$$

$$= -20eV.$$

③ If e^- is shifted from 70V to 70V in closed loop

$$W_{70 \rightarrow 70} = -(-e) (70V - 70V)$$

$$= 0.$$

$$\Rightarrow W_{70 \rightarrow 70} = W_{70 \rightarrow 50} + W_{50 \rightarrow 70}$$

$$= +20 - 20$$

$$= 0$$

⇒ work done in a closed loop is zero and work is independent of actual path (depends on initial & final path only), so electrostatic field is "conservative field".

Ques) A charge is shifted as shown:



$$W_{A \rightarrow B} = -2J$$

$$W_{B \rightarrow C} = +3J$$

$$W_{C \rightarrow A} = ?$$

$$W_{\text{loop}} = 0$$

$$-2 + 3 + W_{C \rightarrow A} = 0$$

$$W_{C \rightarrow A} = -1J$$

$$W_{A \rightarrow C} = 1J$$

☆ ⇒ WORK ENERGY RELATION :-

$$W_{\text{total}} = \Delta R \cdot E$$

$$W_{\text{external}} + W_{\text{conservative}} + W_{\text{non-conservative}} = \Delta R \cdot E$$

$$W_{\text{external}} - \Delta U = \Delta R \cdot E$$

$$W_{\text{ext}} = \Delta R + \Delta U$$

TYPE :- (I) If $W_{\text{ext}} = ?$

Keeping $K.E = \text{constant}$.


$$\therefore \Delta R = 0$$

$$W_{\text{ext}} = \Delta U$$

$$= q(\Delta V) = q(V_f - V_i)$$

TYPICAL # 11

Ques >

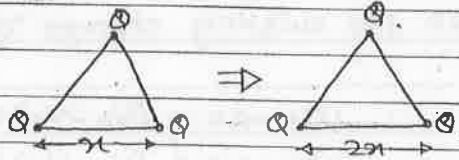


⇒ calculate work for making separate double?

Aus >

$$U_i = \frac{3kQ^2}{r} \qquad U_f = \frac{3kQ^2}{2r}$$

$$W_{ext} = U_f - U_i \\ = -\frac{3kQ^2}{2r}$$


Ques >

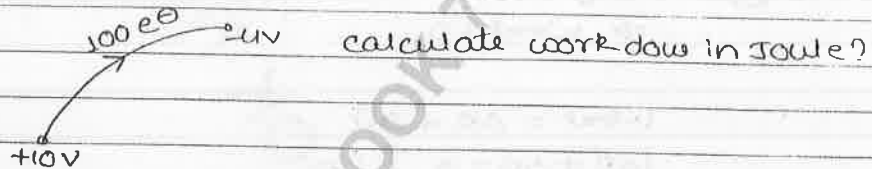

Aus >

$$W_{ext} = q (V_f - V_i) \\ = (-100 \times 1.6 \times 10^{-19}) (-4 - 10) \\ = +2.24 \times 10^{-16} \text{ J}$$

* Ques >

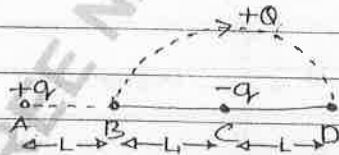


calculate work for shifting +Q from B → D

Aus >

$$W = (+Q) (V_D - V_B) \\ = (+Q) \left[\frac{kq}{3L} - \frac{kq}{L} \right] - \left[\frac{+kq}{L} - \frac{kq}{L} \right] \\ = +Q \left(\frac{-2kq}{3L} \right) \Rightarrow -\frac{2kQq}{3L} = -\frac{2}{3} \frac{kQq}{L}$$

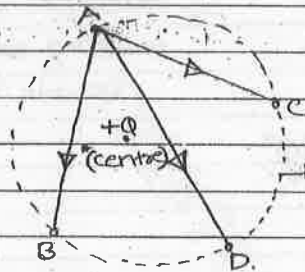Ques) calculate work for shifting charge "q" as shown:



$$W_{A \rightarrow B} = q(V_B - V_A) = 0$$

$$W_{A \rightarrow C} = q(V_C - V_A) = 0$$

$$W_{A \rightarrow D} = q(V_D - V_A) = 0$$

→ circular path.


$$\because V_A = V_B = V_C = V_D$$

TYPE: - (II) :- If K.E \neq constant
 $\Rightarrow W_{ext} = 0$

$$W_{ext} = \Delta K + \Delta U$$

$$\left. \begin{array}{l} \Delta K + \Delta U = 0 \\ K + U = \text{const} \end{array} \right\} \text{(COME)}$$

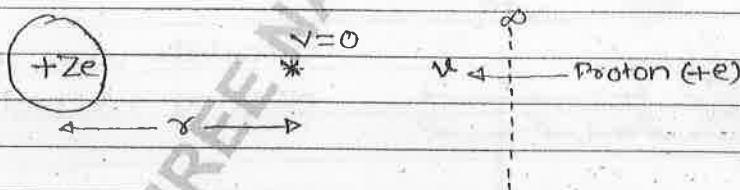 Ques) A proton is thrown with velocity "v" towards a nucleus of atomic no "Z", calculate closed distance of approach



$$K.E \neq \text{const.}$$


$$K + U = \text{const.}$$

$$(K + U)_{\infty} = (K + U)_r$$

$$\frac{1}{2}mv^2 + 0 = 0 + K(Ze)(e)$$

$$\therefore \boxed{r = \frac{2KZe^2}{mv^2}} \quad \because \boxed{r \propto \frac{1}{m}} \quad \because \boxed{r \propto \frac{1}{v^2}}$$

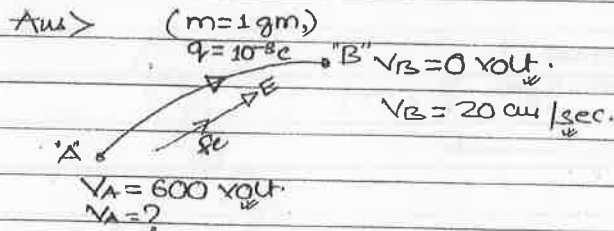*Ques> A particle (1gm , 10^{-8}c) is moving from 600V posn to 0V posn. At 0V posn it's speed become 20cm/sec , Then find its speed at 600V posn. ?



$$K \cdot E \neq \text{const}$$

$$\Delta K + \Delta U = 0$$

$$\Delta K = -\Delta U$$

$$\frac{1}{2} m V_B^2 - \frac{1}{2} m V_A^2 = -q (V_B - V_A)$$

$$\frac{m}{2} (V_B^2 - V_A^2) = -q (0 - 600)$$

$$V_B^2 - V_A^2 = \frac{1200 q}{m}$$

$$(0.2)^2 - V_A^2 = \frac{1200 \times 10^{-8}}{1 \times 10^{-3}}$$

$$0.04 - V_A^2 = 0.012$$

$$V_A^2 = 0.04 - 0.012$$

$$= 0.028$$

$$= 280 \times 10^{-4}$$

$$V_A = 16.8 \times 10^{-2} \text{ m/sec.}$$


$$= 16.8 \text{ cm/sec.}$$

श्री नाथ जी बुक डिपो

ALLEN सत्यार्थ गेट नं. 2

के सामने शॉप नं. 2

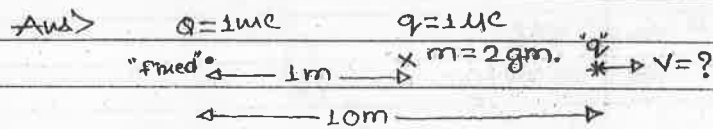* Ques > ② point charges "Q" and "q" are placed at 1m. separation. If small "q" is released then find its speed at 10m distance from "Q"?



(i) ∵ K.E ≠ const

$$(K+U)_{1m} = (K+U)_{10m}$$

$$0 + \frac{kQq}{1} = \frac{1}{2} m v^2 + \frac{kQq}{10}$$

$$\frac{9}{10} (kQq) = \frac{1}{2} m v^2$$

$$v^2 = \frac{9}{5} \frac{kQq}{m}$$

$$v^2 = \frac{9}{5} \times 9 \times 10^9 \times 1 \times 10^{-6} \times 1 \times 10^{-6} \times 2 \times 10^{-3} \times 10^{-3}$$

$$v^2 = 9 \times 10^7 \times 10^{-6}$$

$$v^2 = 81 = 8100$$

$$10^{-2} v = 90 \text{ m/sec.}$$

(ii) If "q" is released then find its terminal velocity (max^m velocity) ∴

→ ∞ It acquires max^m velocity at "∞" only.

$$(K+U)_{1m} = (K+U)_{\infty}$$

$$0 + \frac{kQq}{1} = \frac{1}{2} m v_{\text{max}}^2 + 0$$

$$v_{\text{max}}^2 = \frac{2 \times 9 \times 10^9 \times 1 \times 10^{-6} \times 1 \times 10^{-6}}{2 \times 10^{-3}}$$

$$v_{\text{max}} = \sqrt{9000}$$

$$= 90\sqrt{10} = 95 \text{ m/sec.}$$

Ans) 2 particles having "same mass" and charges "+q", "+4q" are at rest, if these are passed through same Potential Difference (P.D) then find ratio of K.E?

$$\begin{aligned} \text{Ans} > \Delta K &= \Delta U = 0 \\ \Delta K &= -q(\Delta V) \\ K \cdot E_1 - K \cdot E_2 &= -q(\Delta V) \\ K \cdot E_1 &= -q(\Delta V) \end{aligned}$$


$$\frac{K \cdot E_1}{K \cdot E_2} = \frac{-q(\Delta V)}{-4q(\Delta V)} = \frac{1}{4}$$

$$\frac{\frac{1}{2} m v_1^2}{\frac{1}{2} m v_2^2} \Rightarrow \frac{1}{4} \Rightarrow \frac{v_1}{v_2} = \frac{1}{2}$$

☆ \Rightarrow ELECTRIC LINE OF FORCE (ELF) :-

① It is an Imaginary Lines.

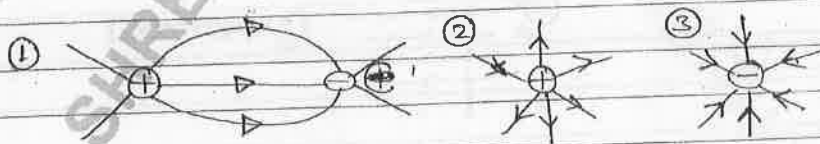② start's from \oplus ve charge and terminates on \ominus ve charge




③ Never Form's close loop.

④ Tangent Drawn on any point of ELF, indicates direction of Field.

⑤ Never Intersect each other.

*6/ ✓ NO. of E.L.F. \propto mass of charge.


Ques

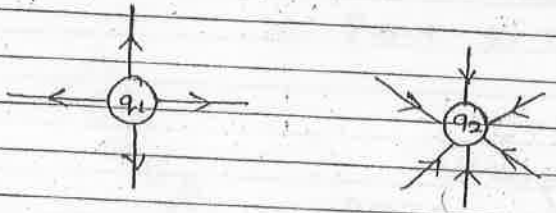



$q_1 = \oplus ve$ $q_2 = \ominus ve.$
 $\frac{|q_1|}{|q_2|} = \frac{4}{6} = \frac{2}{3}$

*7/ ✓ "E" $\propto \frac{1}{L}$
 "seperath b/w Lines."



Ques

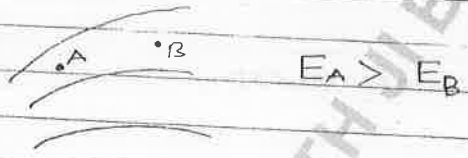

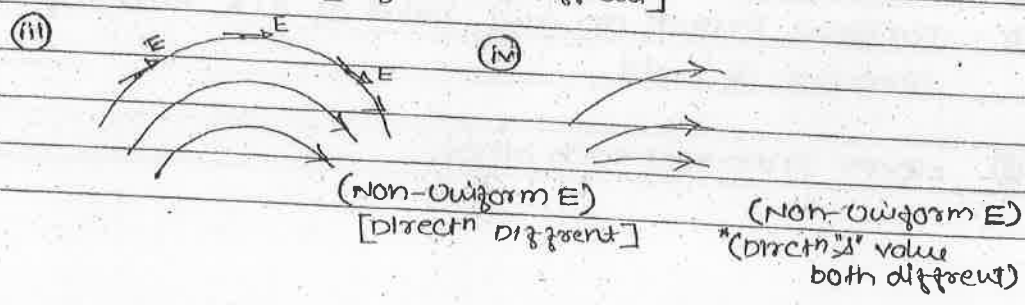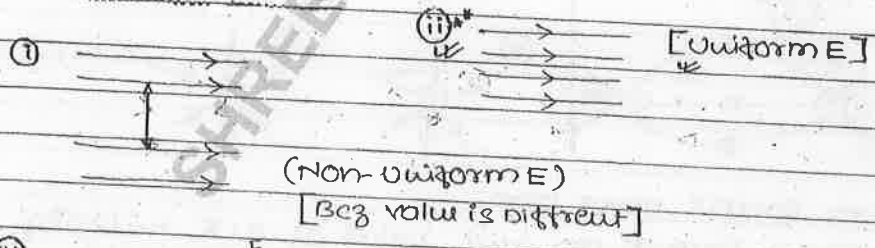8/ *Equi-distant parallel lines represent *uniform Electric field.



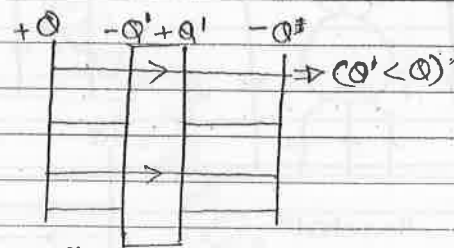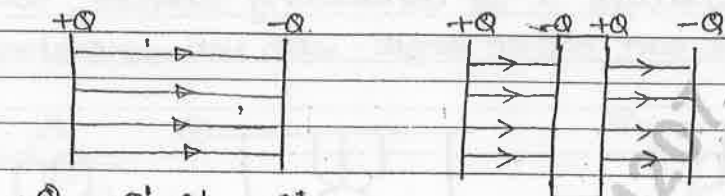*9) In ~~di-~~ conductor's ^{E-LF} can not enter, in Non-conductor, few E-L-F can enter.



Metal.
Inside slab:-
∴ $E_{app} \rightarrow$
∴ $E_{induced} \leftarrow$
∴ $E_{indu} < E_{app}$
∴ $E_{net} \neq 0$

"Di-electric" (Non-Meta)


Inside slab:-
∴ $E_{app} \rightarrow$
∴ $E_{induced} \leftarrow$
∴ $E_{ind} = E_{app}$
∴ $E_{net} = 0$

"Metal"

$\otimes \rightarrow$
 μ $E_{med} = \frac{E_{air}}{\epsilon_r}$



$\epsilon_r > 1$
∴ $E_{med} < E_{air}$

AIRMT
Ques >

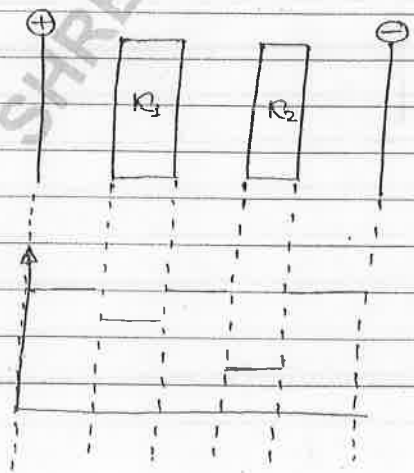

Given; $K_1 < K_2$
∴ $E_{air} > E_1 > E_2$

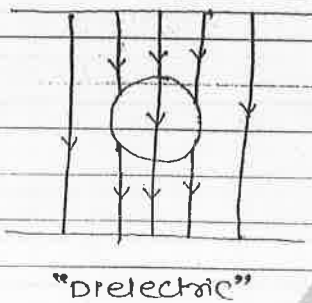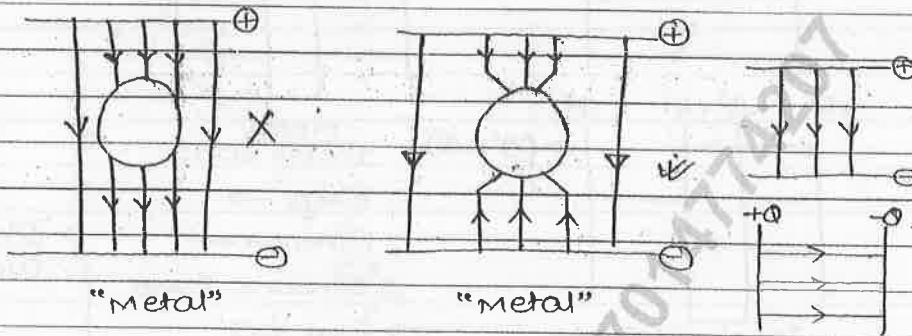
- 10) Electric field and Electric Line Force are always \perp to conducting surface, while these can make angle with non-conducting surface.



SHREE NATHJI BOOK TO

★ ⇒ ELECTRIC FLUX (Φ) :-

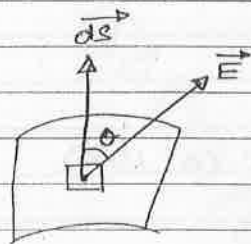It is number of line of force passing through surface.
Placed Normally in Electric Field.




\vec{ds} \perp to surface
Flux with element

$$\begin{aligned} d\Phi &= E \cdot ds \cos\theta \\ d\Phi &= \vec{E} \cdot \vec{ds} \end{aligned}$$

⊗ → scalars

$$\Rightarrow \text{Unit} = \frac{V \times m^2}{m} = V \cdot m$$

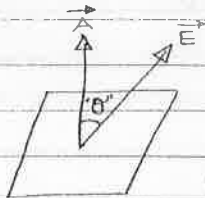★ ⇒ case :- I :- If surface is plane and \vec{E} is uniform :-



$$\begin{aligned} \Phi &= \int E \cdot ds \cos\theta \\ &= E \cos\theta \int ds \end{aligned}$$

$$\begin{aligned} \Phi &= EA \cos\theta \\ \Phi &= \vec{E} \cdot \vec{A} \end{aligned}$$

Ques) surface of Area 10 cm^2 is placed in electric field 10^5 V/m , when field is making 30° with surface,
then flux?

should from
Normal from
surface

$$\begin{aligned} \text{Ans) } \Phi &= EA \cos\theta \\ &= 10^5 \times 10 \times 10^{-4} \times \cos 60^\circ \\ &= 10^6 \times 10 \times \frac{\sqrt{3}}{2} \times \frac{1}{2} = 50 \end{aligned}$$

Ques > surface of Area; 10m^2 ; placed in $\vec{E} = 2\hat{i} + 3\hat{j} + 6\hat{k} \text{ V/m}$
calculate Flux if :-

① surface is in $(x-z)$ plane. ($A = 10\hat{j}$)

Ans > ① $\Phi = \vec{E} \cdot \vec{A}$
 $= (2\hat{i} + 3\hat{j} + 6\hat{k}) \cdot (10\hat{j})$
 $= 30 \text{ V.m.}$

② surface is in $(x-y)$ plane :- ($A = 10\hat{k}$)

$$\Phi = \vec{E} \cdot \vec{A}$$

$$= (2\hat{i} + 3\hat{j} + 6\hat{k}) \cdot (10\hat{k})$$

$$= 60 \text{ V.m}$$

⊛ case :- II :- Flux with closed surface :-

$$\rightarrow \Phi_{\text{net}} = \oint \vec{E} \cdot d\vec{s}$$

$$\rightarrow \Phi_{\text{net}} = \Phi_1 + \Phi_2 + \Phi_3 + \dots$$


$\rightarrow \vec{A} \rightarrow$ Normal "s" outward

$$\rightarrow \Phi_{\text{incoming}} = -ve$$

$$\Phi_{\text{outgoing}} = +ve$$

Ques > A cylindrical close surface is placed in uniform electric field \vec{E} as shown; calculate flux with cylin.?

Ans >

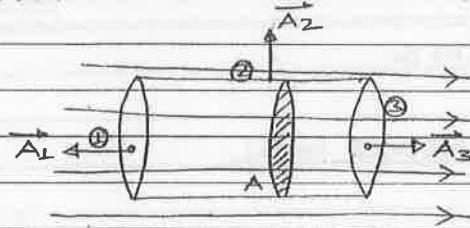


$$\Phi_1 = EA \cos 180 = -EA$$


$$\Phi_2 = EA \cos 90 = 0$$

$$\Phi_3 = EA \cos 0 = +EA.$$

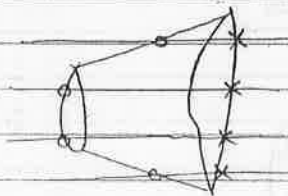
$$\Phi_{\text{net}} = \Phi_1 + \Phi_2 + \Phi_3 = 0$$



$$(-4) + (+4)$$

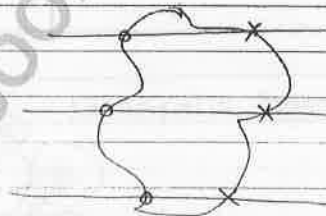

$$(-3) + (+3)$$

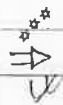

Net Flux of closed surface is decided by Inside charges only, "Not" by "External Field" and "Exte. charges".

$$q_{\text{inside}} = +ve \Rightarrow \begin{array}{l} -10 \\ +15 \end{array} \left. \vphantom{\begin{array}{l} -10 \\ +15 \end{array}} \right\} +5$$

$(+q) =$ above Released
Line (Exit)

$$q_{\text{inside}} = -ve \Rightarrow \begin{array}{l} -10 \\ +5 \end{array} \left. \vphantom{\begin{array}{l} -10 \\ +5 \end{array}} \right\} -5$$

$(-q) =$ above Lines
↓

$$q_{\text{inside}} = \text{zero} \Rightarrow \begin{array}{l} -10 \\ +10 \end{array} \left. \vphantom{\begin{array}{l} -10 \\ +10 \end{array}} \right\} \text{zero}$$

★ ⇒ GAU'SE THEOREM :-

- (i) valid for "close surface" only.
- (ii) valid for all conservative force.
- (iii) Net Flux (Φ_{net}) with close surface is $\frac{1}{\epsilon_0}$ time of total charge enclosed in the surface.


$$\Phi_{net} = \frac{\sum q}{\epsilon_0}$$

$$\Phi_{net} = \oint \vec{E} \cdot d\vec{s}$$

$$\oint \vec{E} \cdot d\vec{s} = \frac{\sum q}{\epsilon_0}$$

→ submission sign \oint


Ques > "3" closed surfaces;

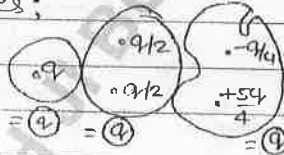

$$\Phi_{net} = \frac{\sum q}{\epsilon_0} = \frac{q}{\epsilon_0}$$

⇒ Net Flux (Φ_{net}) is independent of shape & size of Gaussian surface and inner charge distribution.

Ques >

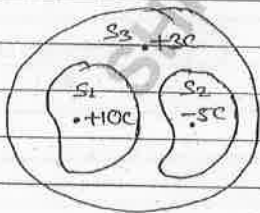


$$(i) \Phi_{S1} = \frac{+10}{\epsilon_0}$$

$$(ii) \Phi_{S2} = \frac{-5}{\epsilon_0}$$

$$(iii) \Phi_{S3} = \frac{8}{\epsilon_0} = \frac{[-10 + 3 + (-5)]}{\epsilon_0}$$

$$\Phi_{net} = \frac{8}{\epsilon_0}$$


Ques >

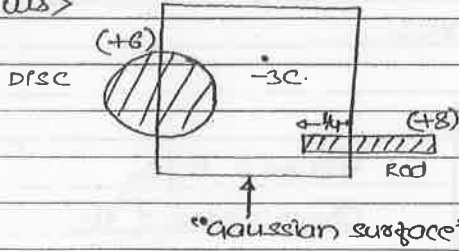

$$\Phi_{net} = \frac{\sum q}{\epsilon_0} = \frac{-3 + 3 + 2}{\epsilon_0} = \frac{2}{\epsilon_0}$$

Ques > A long wire of charge density 'a', passing through a cube; calculate max^m flux with cube?


Ans >

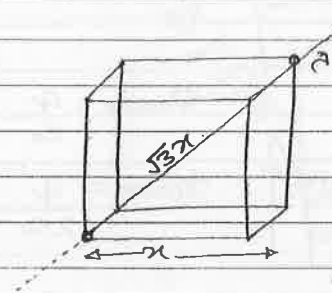

$$(\Phi_{net})_{max} = \frac{(\sum q)_{max}}{\epsilon_0} = \frac{(\sqrt{3}a)a}{\epsilon_0}$$

*** Ques >


$\Phi_{Bowl} = ?$

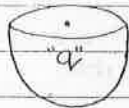

Ans >



Gaussian surface (unsymet^s)

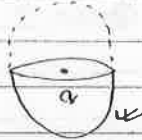

Gaussian surface (symmetrical)


$$\Phi_{Gaussian} = \frac{q}{\epsilon_0}$$

$$\Phi_{Bowl} = \frac{q}{2\epsilon_0}$$

Ques >

small \otimes


*//ques> cube:- (1) "q" at centre:-

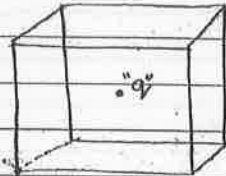

$$\Phi_{\text{cube}} = q / \epsilon_0$$

$$\Phi_{\text{each surface}} = \frac{q}{6\epsilon_0}$$


(2) "q" at the centre of one face:-

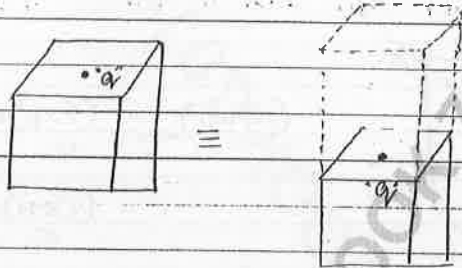

$$\Phi_{\text{gauss}} = \frac{q}{\epsilon_0}$$

$$\Phi_{\text{cube}} = \frac{q}{2\epsilon_0}$$

(3) "q" at one corner:-

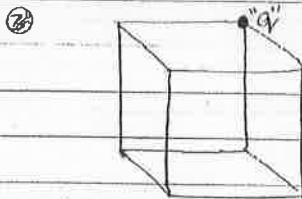

Gaussian has 8 cube.

so;

$$\Phi_{\text{cube}} = \frac{q}{8\epsilon_0}$$


*//> surface in which charges lies, Flux Remains Zero.

$$\Phi_{\text{each shaded face}} = 0$$

$$\Phi_{\text{each unshaded face}} = \frac{1}{3} \left(\frac{q}{8\epsilon_0} \right)$$

$$= \frac{q}{24\epsilon_0}$$

Ques >

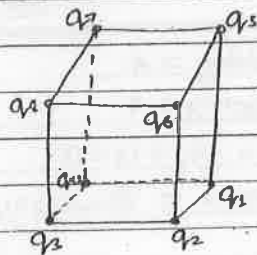

$$\Phi_{\text{cube}} = \frac{q_1}{8\epsilon_0} + \frac{q_2}{8\epsilon_0} + \frac{q_3}{8\epsilon_0} + \dots + \frac{q_6}{8\epsilon_0}$$

$$= \frac{1}{8\epsilon_0} (q_1 + q_2 + q_3 + \dots + q_6)$$


Ques > on a close surface; 5×10^5 entering and 4×10^5 leaving then calculate enclosed charge?

Ans > $\Phi_{\text{net}} = -1 \times 10^5$
 $\frac{\epsilon q}{\epsilon_0} = -1 \times 10^5$

$$\epsilon q = -1 \times 10^5 \times (8.85 \times 10^{-12})$$

$$= -8.85 \times 10^{-7}$$

Ques >

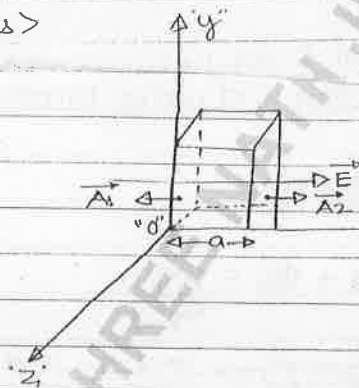

$$\Rightarrow \vec{E} = 600\sqrt{2} \hat{i}$$

\Rightarrow enclosed charge in cube = ?

Ans > $\Phi_3 = \Phi_4 = \Phi_5 = \Phi_6 = 0$ bcz $\vec{E} \perp \vec{A}$

$$\Phi_1 = E_1 A_1 \cos \theta_1$$

$$= (600\sqrt{2}) (a^2) \cos 0^\circ$$

$$\Phi_2 = E_2 A_2 \cos \theta_2$$


$$= (600\sqrt{2}) (a^2) \cos 0^\circ$$

$$= 600 a^2 \sqrt{2}$$

$$\Phi_{\text{net}} = \Phi_1 + \Phi_2 + \dots + \Phi_6$$

$$\frac{\epsilon q}{\epsilon_0} = 600 a^2 \sqrt{2} \Rightarrow \boxed{q = 600 a^2 \sqrt{2} \epsilon_0}$$

Ques >

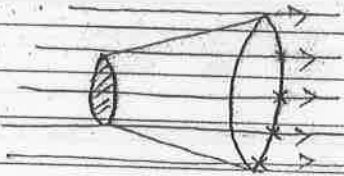

$$\Phi_{\text{incoming}} = 4$$


$$\Phi_{\text{outgoing}} = 4$$

$$\Phi_{\text{net}} = -4 + 4 = 0$$

$$\therefore \Phi_{\text{incom}} = \Phi_{\text{outgoing}}$$

$$\Rightarrow E \times \text{Maxim. Cross-section Area.}$$

Ques > CONE:-

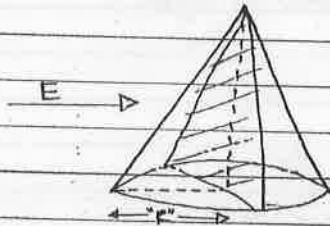

$$\Phi_{\text{incoming}} = \Phi_{\text{outgoing}}$$


$$= E \times \left(\frac{1}{2} \times 2\pi r \times h \right)$$

$$= E \cdot \pi r h$$

☆ ⇒ APPLICATION OF GAUSS THEOREM:-

- ① It is used to calculate Electric Field due to charge distribution of large size and large dimension

① LONG WIRE (UNIFORMLY CHARGED):-

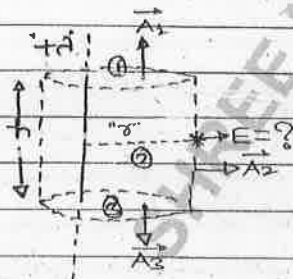


$$\therefore \Phi_1 + \Phi_2 + \Phi_3 = \frac{Eq}{\epsilon_0}$$


$$0 + E(2\pi r l) \cos 0^\circ + 0 = \frac{\lambda l}{\epsilon_0}$$

$$E = \frac{\lambda}{2\pi \epsilon_0 r} \Rightarrow \boxed{E = \frac{2k\lambda}{r}}$$

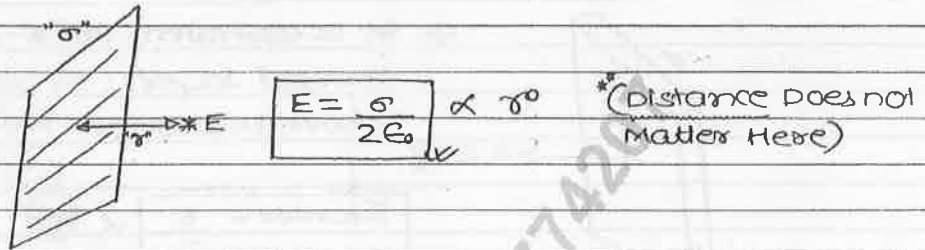
II UNIFORMLY CHARGED NON-CONDUCTING SHEET :-



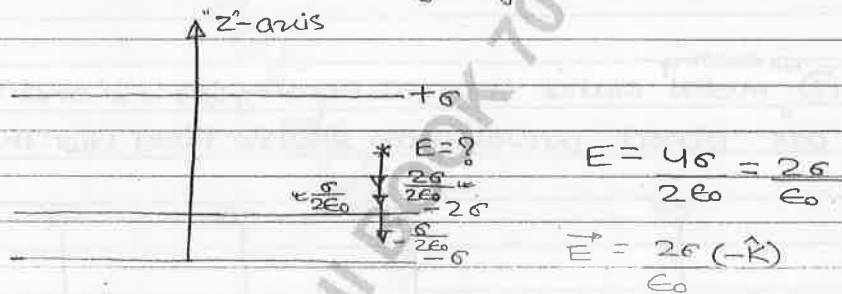III ques \rightarrow ③ Non conducting layers are placed as shown :-



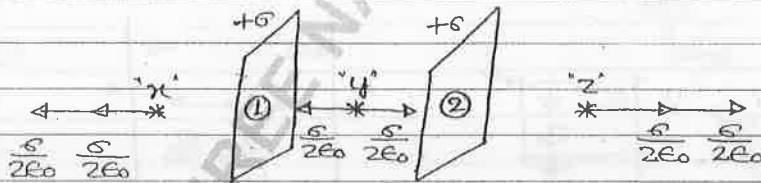
ques \rightarrow ② Non conducting layers are placed as shown :-



Ans \rightarrow Here ;

$E_x = E_z = \frac{\sigma}{\epsilon_0}$
$E_y = 0$

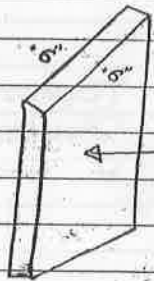III) UNIFORMLY CHARGED CONDUCTING PLATE :-




⇒ It is equivalent to "2" parallel charged layers; so according to above question :- Previous Questⁿ

$E_{\text{outside}} = \frac{\sigma}{\epsilon_0} \propto \sigma^0$
$E_{\text{inside}} = 0$


AIMS 2006

Ques) ②- Metal plates charged density (σ) " $+\sigma$ " and " $-\sigma$ " are placed parallel than electric field b/w them.

Ans)

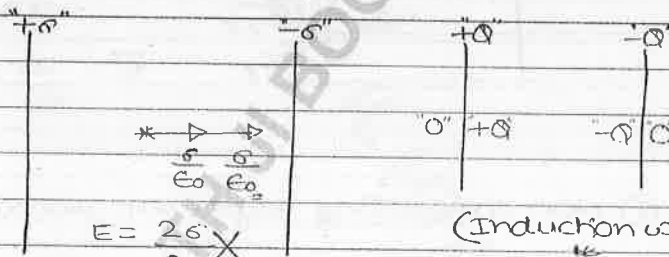


(Induction will occur)

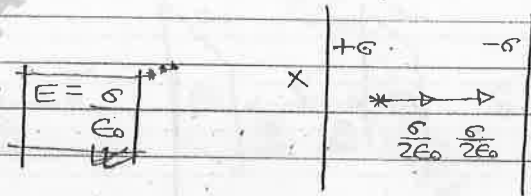

AIIEEE

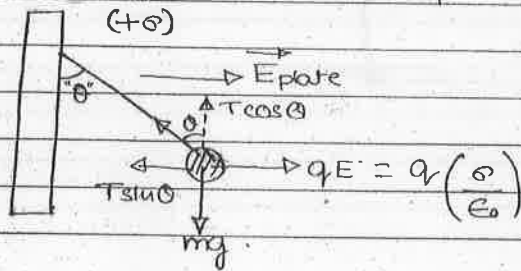Ques) conducting plate :- In equilibrium " σ " is proportional to :-



At Balance :- $T \sin \theta = \frac{q\sigma}{\epsilon_0} \dots (1)$

$T \cos \theta = mg \dots (2)$


(1) $\tan \theta = \frac{q\sigma}{\epsilon_0 mg} \Rightarrow \sigma \propto \tan \theta$ (Ans)

(2)

$\therefore T \sin \theta = \frac{q\sigma}{\epsilon_0} \Rightarrow \sigma \propto \sin \theta$

$T = \frac{q\sigma}{\epsilon_0 \sin \theta} \neq \text{const.} \therefore \sigma$ is variable

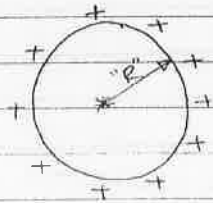(IV) ALL CONDUCTING SPHERE AND HOLLOW NON-CONDUCT. SPHERE :-




"r" \Rightarrow distance of observation point from centre of sphere.


	Position	"E"	V
(1)	$r > R$	$\frac{RQ}{r^2}$	$\frac{RQ}{r}$
(2)	$r = R$	$\frac{RQ}{R^2}$	$\frac{RQ}{R}$
(3)	$r < R$	0	$\frac{RQ}{R}$
(4)	$r = 0$	0	$\frac{RQ}{R}$

V.V.IMP


Ques) (i) $V \propto \frac{1}{r}$

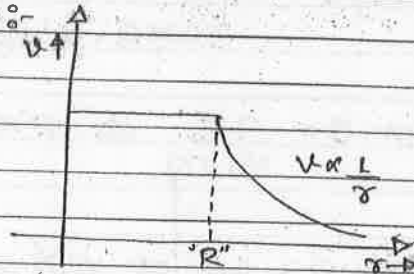

(ii) $E \propto \frac{1}{r^2}$

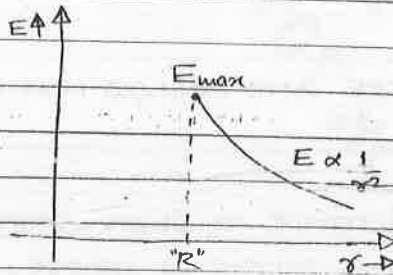

Ques)

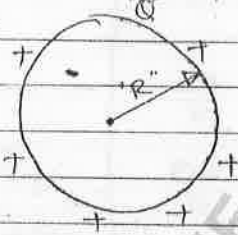

$$\sigma = \frac{Q}{4\pi R^2}$$

$$Q = \sigma \cdot 4\pi R^2$$

$$(1) E_{\text{surface}} = \frac{Q}{R^2}$$

$$= \frac{L}{4\pi\epsilon_0} \times \frac{\sigma \cdot 4\pi R^2}{R^2} = \frac{\sigma}{\epsilon_0}$$

$$(2) V_{\text{surface}} = \frac{Q}{R} = \frac{L}{4\pi\epsilon_0} \times \frac{\sigma \cdot 4\pi R^2}{R^2} = \frac{\sigma R}{\epsilon_0}$$


 \Rightarrow FOR CONDUCTOR OF ANY SHAPE $\Rightarrow E_{\text{surface}} = \frac{\sigma}{\epsilon_0}$

Ques $\Rightarrow E_{\text{surface}} = \frac{kQ}{R^2} \propto \frac{1}{R^2} \Rightarrow$ (if $Q = \text{const.}$)

$E_{\text{surface}} = \frac{\sigma}{\epsilon_0} \propto R^0 \Rightarrow$ (if $\sigma = \text{const.}$)

$E_{\text{surface}} = \frac{V_{\text{surface}}}{R} \propto \frac{1}{R} \Rightarrow$ (if $V = \text{const.}$)

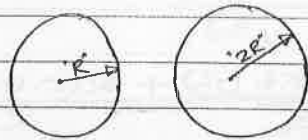Ques \Rightarrow (2) metal sphere; A these surface; $E_1 = ?$ if:-
 E_2



(1) Both have same charges

(2) $\sigma = \text{same}$

(3) If Both are Touched with each other?


Ans \Rightarrow (1) $E = \frac{kQ}{R^2} \propto \frac{1}{R^2} \Rightarrow E_1 : E_2 = 4 : 1$

(2) $E_{\text{surface}} = \frac{\sigma}{\epsilon_0} \propto R^0 \Rightarrow E_1 : E_2 = 1 : 1$

(3) If Touched then $V = \text{same}$ for both sphere;
 $(V = \text{const.})$

$E = \frac{V}{R} \propto \frac{1}{R} \Rightarrow E_1 : E_2 = 2 : 1$

NPMT
 * Ques

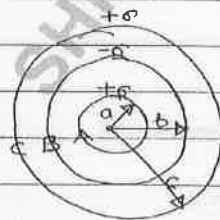

3- conducting concentric spheres;

If; $C = a + b$ then; V_A, V_B, V_C ?

(1) $V_A = \frac{k(\sigma \cdot 4\pi a^2)}{a} + \frac{k(-\sigma \cdot 4\pi b^2)}{b} + \frac{k(\sigma \cdot 4\pi c^2)}{c}$

$= k \cdot \sigma \cdot 4\pi (a - b + c)$

$= k \cdot \sigma \cdot 4\pi (a - b + a + b)$

$= k \cdot \sigma \cdot 4\pi (2a) \dots \textcircled{1}$

$$V_B = \frac{R \cdot (\sigma \cdot 4\pi a^2)}{b} + R \frac{(-\sigma \cdot 4\pi b^2)}{b} + R \frac{(\sigma \cdot 4\pi c^2)}{c}$$

$$= R \cdot \sigma \cdot 4\pi \left(\frac{a^2 - b^2 + c}{b} \right)$$

$$= R \cdot \sigma \cdot 4\pi \left(\frac{a^2 - b^2 + a + b}{b} \right)$$

$$= R \cdot \sigma \cdot 4\pi \left(\frac{a^2 - b^2 + ab + b^2}{b} \right)$$

$$= R \cdot \sigma \cdot 4\pi \left(\frac{a^2 + ab}{b} \right) \text{ --- (2)}$$

$$V_C = \frac{R \cdot (\sigma \cdot 4\pi \cdot a^2)}{c} + R \frac{(-\sigma \cdot \pi + b^2)}{c} + R \frac{(\sigma \cdot 4\pi \cdot c^2)}{c}$$

$$= R \cdot \sigma \cdot 4\pi \left(\frac{a^2 - b^2 + c}{c} \right)$$

$$= R \cdot \sigma \cdot 4\pi \left(\frac{a^2 - b^2 + a + b}{a + b} \right)$$

$$= R \cdot \sigma \cdot 4\pi (a - b + a + b)$$

$$= R \cdot \sigma \cdot 4\pi (2a) \text{ --- (3)}$$

$$\Rightarrow V_A = V_C \neq V_B$$

AIIEE

Ques > If $V_A = V_C$ then; relate a, b, c ?

$$\text{Ans} > V_A = R \cdot \sigma \cdot 4\pi (a - b + c)$$

$$V_C = R \cdot \sigma \cdot 4\pi \left(\frac{a^2 - b^2 + c}{c} \right)$$


$$V_A = V_C \Rightarrow (a - b + c) = \frac{a^2 - b^2 + c^2}{c}$$

$$\Rightarrow ca - cb + c^2 = a^2 - b^2 + c^2 \Rightarrow c(a - b) = a^2 - b^2$$

$$\Rightarrow c(a - b) = (a - b)(a + b)$$

$$\Rightarrow c = a + b$$

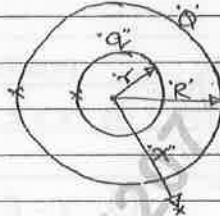Ques → Two metallic concentric shell, with radius r and R & charges " Q " and " q " ?



$$V_{\text{small}} = \frac{RQ}{r} + \frac{KQ}{R}$$

$$V_{\text{big}} = \frac{Rq}{R} + \frac{KQ}{R}$$

$$V_x = \frac{Rq}{r} + \frac{KQ}{r}$$

- ① $V_{\text{small}} > V_{\text{big}}$ ($R > r$)
 ② Potential difference b/w spheres

$$P.D = V_{\text{small}} - V_{\text{big}}$$

$$P.D = KQ \left(\frac{1}{r} - \frac{1}{R} \right)$$


* $P.D \propto q$ ⇒ P.D is not dependent of Q (outside charge)

This P.D is independent of "outer sphere charge" so;

$$\text{If: } 0 \rightarrow -3Q$$

then; P.D = Remains same

iii)

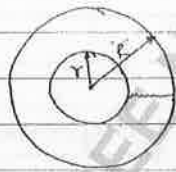

⇒ If sphere's are connected internally as shown, then :- conduction takes place and finally potential become same ($P.D=0$)

$$\Rightarrow P.D=0 \Rightarrow \because Kq \left(\frac{1}{r} - \frac{1}{R} \right) = 0$$


- ① $K=0$ ✗ ② $q=0$ ✗ ③ $r=R$ ✗
 (not possible) (possible) (not possible)

$$\text{so; } q_{\text{small}} = 0$$

$$q_{\text{big}} = Q + q$$

⇒ This is only method to transfer Total charge of one conductor to Another.


⑤ SOLID NON-CONDUCTING SPHERE:

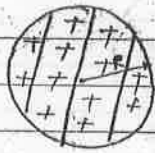


Position	(E)	(V)
① $r > R$	$\frac{KQ}{r^2}$	$\frac{KQ}{r}$
② $r = R$	$\frac{KQ}{R^2}$	$\frac{KQ}{R}$
③ $r < R$	$\frac{KQ \cdot r}{R^3}$	$\frac{KQ (3R^2 - r^2)}{2R^3}$
④ $r = 0$	0	$\frac{3}{2} \left(\frac{KQ}{R} \right)$

* ⇒ GRAPHS:

① 'E' v/s 'R' ⇒ E ↑

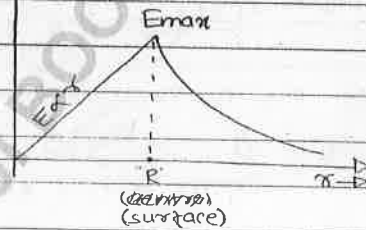

② V v/s r ⇒

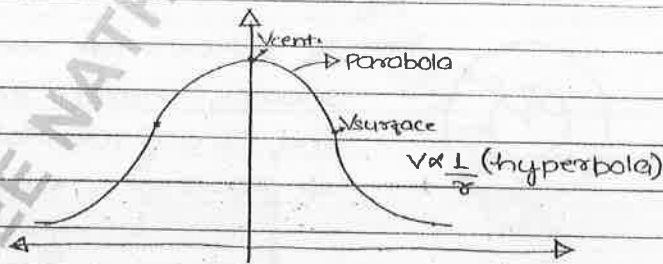

Ques) A uniformly +ve charged sphere of Radius 'R',
if $V_{\text{surface}} = V_0$ then find distance from centre

where:- ① $V_1 = \frac{5}{4} V_0$ ③ $V_3 = \frac{V_0}{2}$

② $V_2 = \frac{3}{4} V_0$ ④ $V_4 = \frac{3}{2} V_0$

⇒ if Nothing given than take sphere as a solid sphere.

Ans \rightarrow ① $V_1 = \frac{5V_0}{4}$

H.W ③ $V_3 = \frac{V_0}{2}$

$$KQ \left(\frac{3R^2 - r_1^2}{2R^3} \right) = \frac{5}{4} \left(\frac{KQ}{R} \right)$$

$$\frac{KQ}{r_3} = \frac{KQ}{2R}$$

$$6R^2 - 2r_1^2 = 5R^2$$

$$2r_1^2 = R^2$$

$$\therefore r_1 = \frac{R}{\sqrt{2}}$$

② $V_2 = \frac{3V_0}{4}$

H.W ④ $V_4 = \frac{2V_0}{3}$

$$\frac{KQ}{r_2} = \frac{3}{4} \left(\frac{KQ}{R} \right)$$

$$KQ \left(\frac{3R^2 - r_4^2}{2R^3} \right) = \frac{3}{2} \left(\frac{KQ}{R} \right)$$

$$r_2 = \frac{4R}{3}$$

$$\therefore r = 0 \text{ (centre)}$$

Ques \rightarrow $e = \frac{Q}{\frac{4}{3}\pi R^3}$ than; $E_{\text{inside}} = ?$

Ans \rightarrow $E_{\text{inside}} = \frac{KQ}{R^3} r = \frac{1}{4\pi\epsilon_0} \left(\frac{e \times \frac{4}{3}\pi R^3}{R^3} \right) r$
 $= \frac{e r}{3\epsilon_0}$

* Ques \rightarrow For a Uniformly charged sphere $\therefore V_{\text{inside}} = ar^2 + b$ than, Find volume charge density?

Ans \rightarrow $V_{\text{inside}} = -dv = -2ar$

$$\frac{e r}{3\epsilon_0} = -2ar$$

$$\therefore e = -6\epsilon_0 a$$

★ ⇒ BIG LIQUID DROP \longleftrightarrow n - Identical small drop

- ① $R_{BIG} = n^{1/3} r_{small}$.
- ② $Q_{BIG} = n q_{small}$.
- ③ $\sigma_{BIG} = n^{1/3} \sigma_{small}$.
- ④ $E_{BIG} = n^{1/3} E_{small}$.
- ⑤ $C_{BIG} = n^{1/3} C_{small}$.
- ⑥ $V_{BIG} = n^{2/3} V_{small}$.

$$\text{eg: } ① \frac{4}{3} \pi R^3 = n \left(\frac{4}{3} \pi r^3 \right)$$

$$R^3 = n r^3.$$

$$R = n^{1/3} r.$$

$$② \sigma = \frac{Q}{4\pi R^2} \propto \frac{n}{(n^{1/3})^2} \propto n^{1/3}$$


$$③ E = \frac{\sigma}{\epsilon_0} \propto \sigma \propto n^{1/3}$$

$$④ C = 4\pi \epsilon_0 R \propto R \propto n^{1/3}$$

$$⑤ V = \frac{Q}{R} \propto \frac{n}{n^{1/3}} \propto n^{2/3}$$

★ ⇒ ELECTRIC DIPOLE :-

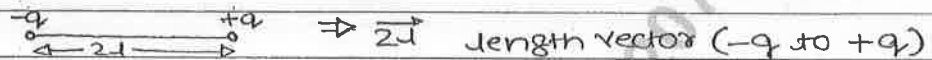→ It has TWO CHARGES of "some magnitude" and "opposite nature" at some distances.



① DIPOLE MOMENT (P) :-

$$P = \text{charge} \times \text{length vector} \quad \text{vector} = \text{"-q" to "+q"}$$


unit = Cm .

$$P = q \cdot 2l$$


$$P = q \cdot 2l$$

$$1 \text{ Debye (D)} = 3.3 \times 10^{-30} \text{ Cm}$$

Ques > Net Dipole Moment = ?

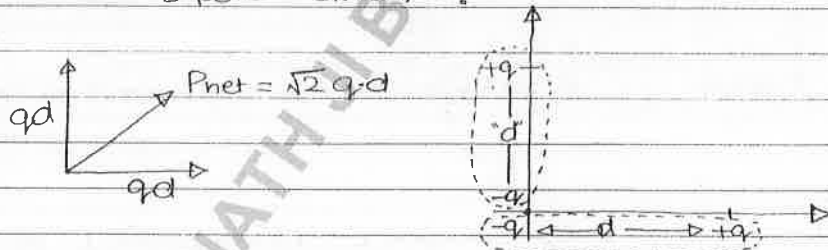


② 'E' due to DIPOLE :-

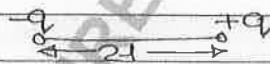


$$P = q(2l)$$

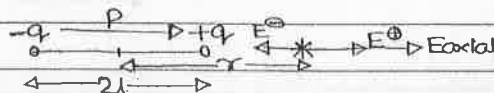case: I → Axial / End on / Longitudinal / Tan A



$$* E_{\text{axis}} = \frac{2 \cdot K P r}{(r^2 - l^2)^2} \approx \frac{2 K P}{r^3} \text{ (Along } \vec{P} \text{)}$$

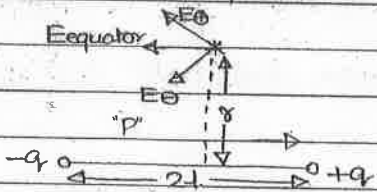
② case:- 2 \Rightarrow Equatorial / Broadside / Transverse / Tan B:



$$E_{\text{equator}} = \frac{Kp}{(r^2 + l^2)^{3/2}} \approx \frac{Kp}{r^3}$$

Direction: (opposite to \vec{p})

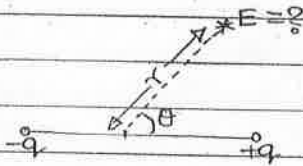③ case:- 3 \Rightarrow GENERAL POINT (r, θ) :-



① $E = \frac{Kp}{r^3} \sqrt{(1 + 3\cos^2\theta)}$


② Angle b/w "E" and "P"
 $= \theta + \tan^{-1}(\frac{1}{2} \tan\theta)$

Ques \Rightarrow For a short Dipole at same Distance : $E_{\text{axis}} = ?$
 E_{equator}

Ans \Rightarrow $\frac{E_{\text{axis}}}{E_{\text{equator}}} = \frac{2Kp/r^3}{Kp/r^3} = 2 \Rightarrow 2:1$ ✓ correct
 $= 2:1$ (Approx) ✗ More correct
 $= -2:1$ (Approx) ✗ More, More correct

Ques \Rightarrow ① $E_{\text{dipole}} \propto \frac{1}{r^3}$ ② $E_{\text{point charge}} \propto \frac{1}{r^2}$ ③ $E_{\text{long wire}} \propto \frac{1}{r}$ ④ E_{sheet}

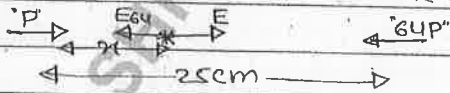Ques \Rightarrow 2 dipole 'P' & '64P' are placed as shown; Find Distance from 'P' at which Electric field is 'zero'?



$$E_p = E_{64P}$$

$$\frac{2Kp}{x^3} = \frac{2K(64p)}{(25-x)^3} \Rightarrow x^3 = \frac{(25-x)^3}{64}$$

$$x = \frac{25-x}{4}$$

$$x = 5\text{cm}$$


Ques \rightarrow $-q_0$ \leftarrow $6m$ \rightarrow $+q$ \Rightarrow Find Ratio of Electric field at Axis and Equator at distance $4m$ from center.

Ans \rightarrow $E_{axis} = ?$
 E_{equat}

$$E_{axis} = \frac{2RP}{(r^2 + l^2)^{3/2}} = \frac{2 \times 4 \times 125}{(4^2 + 3^2)^{3/2}} = \frac{1000}{49}$$

$$E_{equat} = \frac{RP}{(r^2 + l^2)^{3/2}} = \frac{4 \times 125}{(4^2 + 3^2)^{3/2}} = \frac{500}{49} \approx \frac{20}{1}$$

Ques \rightarrow

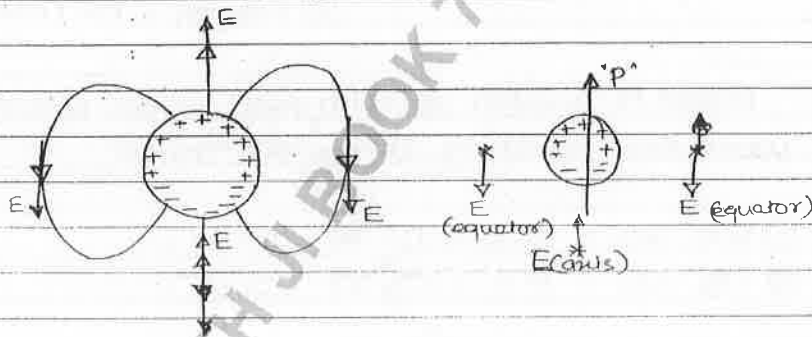

(3) Potential Due to DIPOLE :-

$$V = \frac{kP \cos \theta}{r^2 - l^2 \cos^2 \theta} \approx \frac{kP \cos \theta}{r^2}$$

(i) At "AXIS" :- ($\theta = 0$)


$$V_{axis} = \frac{kP}{r^2 - l^2} = \frac{kP}{r^2}$$

(ii) At Equator ($\theta = 90$)

$$V_{equator} = 0$$

\Rightarrow (So; work for moving a charge on Equator of dipole is always zero)

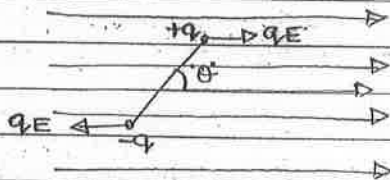★ ⇒ BEHAVIOUR IN EXTERNAL UNIFORM ELECTRIC FIELD:



$$(i) F_{net} = 0$$

$$(ii) \tau = PE \sin \theta$$

$$\vec{\tau} = \vec{P} \times \vec{E}$$

$$(iii) U = -PE \cos \theta$$

$$U = -\vec{P} \cdot \vec{E}$$

$$(iv) W_{\theta_1 \rightarrow \theta_2} = PE (\cos \theta_1 - \cos \theta_2)$$

* Ques > Dipole is making 30° with field, then calculate work for rotating it ⁽¹⁾ by 60° ⁽²⁾ to 60°

$$\text{Ans} > (1) W_{0 \rightarrow 90} = P \cdot E (\cos 30^\circ - \cos 90^\circ)$$

$$(2) W_{90 \rightarrow 60} = P \cdot E (\cos 30^\circ - \cos 60^\circ)$$

⊗ ⇒ SPECIAL CASE:

$$(1) \text{ If } \theta = 0;$$

$$F_{net} = 0$$


$$\tau = PE \sin \theta = 0$$

$$U = -PE \cos \theta = -PE \text{ (Minimum)}$$

⇒ Dipole is in stable Equilibrium.

⇒ If Dipole is given "small Angular Displacement" then it

performs "Angular S.H.M" with Time Period (T) = $2\pi \sqrt{\frac{I}{PE}}$

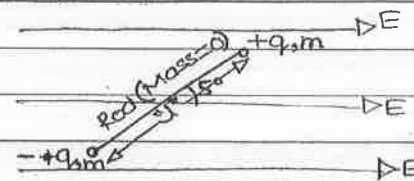Ques)  \Rightarrow If Dipole is Released, then calculate Time, when it becomes "Along the field" 1st Time?

Ans)
$$T = 2\pi \sqrt{\frac{m \times \left(\frac{l}{2}\right)^2 + m \left(\frac{l}{2}\right)^2}{(q \cdot l) E}} = 2\pi \sqrt{\frac{ml}{2qE}}$$


And Dipole Becomes along 'E' at $t = \frac{T}{4}$

$$t = \frac{\pi}{2} \sqrt{\frac{ml}{2qE}}$$

★ \Rightarrow CONDUCTOR OF IRREGULAR SHAPE

'R' \rightarrow "radius of curvature"

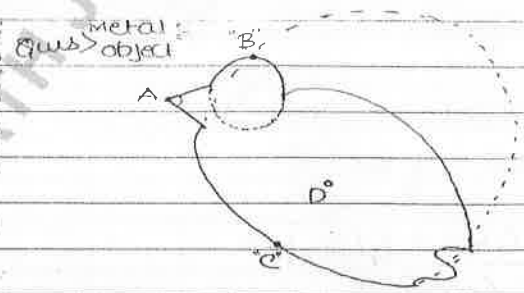- ① $Q \propto R$
- ② $\sigma \propto \frac{1}{R}$
- ③ $E = \frac{\sigma \times l}{\epsilon_0 R}$
- ④ $V \propto R^0$




Ans) $\otimes R_c > R_B > R_A$

- ① $q_C > q_B > q_A > q_D = 0$
- ② $\sigma_A > \sigma_B > \sigma_C$
- ③ $E_A > E_B > E_C > E_D = 0$
- ④ $V_A = V_B = V_C = V_D$ *(conductors are equi-potential surface!)

☆ ⇒ CORONA DISCHARGE

In conductors, migration of charge and approach of charge takes place at "sharp corner" 1st (First).

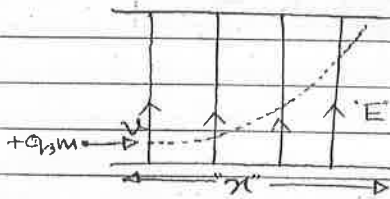☆ ⇒ Path of charge particle in uniform Transverse Electric Field (gravity = Negligible):-



⊗ X-Direction :-

$$U_x = v$$

$$a_x = 0$$

"x" distance in time "t"

$$s = ut + \frac{1}{2} at^2$$

$$x = vt + \frac{1}{2} 0(t^2)$$

$$x = vt \quad \text{--- (1)}$$

⊗ ⇒ Y-direction :-

$$U_y = 0$$

$$a_y = \frac{qE}{m}$$

"y" height in time "t"

$$s = ut + \frac{1}{2} at^2$$

$$y = 0(t) + \frac{1}{2} \left(\frac{qE}{m} \right) t^2$$

$$y = \left(\frac{qE}{2m} \right) t^2$$

$$y = \frac{qE}{m} \times \left(\frac{x}{v} \right)^2$$

Deviation (y)

bt AIPMT 2005

$y = \left(\frac{qE}{2mV^2} \right) x^2$	(Parabola)	∴ $y = \left(\frac{qE}{4(K \cdot E)} \right) x^2$
---	------------	--

SHREE NATH JI BOOK 7014774207

Date _____ Page _____

SHREE NATH JI BOOK 7014774207

QUESTION DISCUSSION (ELECTROSTAT):-

Date _____ Page _____


32) :- 6.75 micro coulomb.

34) $F = q \cdot E \Rightarrow E = \frac{F}{q} = \frac{3000}{30} = 1000 = \frac{dv}{dr} = \frac{dv}{0.1 \times 10^{-2}}$

$dv = 10 \text{ volt}$

41) $E = \frac{dv}{dr} = 0$
 $v = \text{const.}$

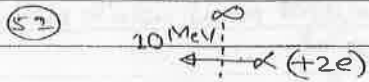51) $\Delta K + \Delta U = 0$
 $\Delta K = -q(\Delta V)$
 $= -(+2e)(50V - 70V)$
 $= +40 \text{ eV}$




$(K+U)_\alpha = (K+U)_\gamma$


$10 \text{ MeV} + 0 = 0 + K(50e)(2e)$

$10 \times 10^6 \times 1.6 \times 10^{-19} = K(50e)(2e)$

58)

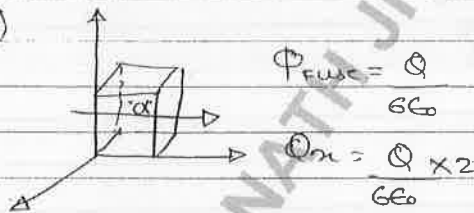

68)

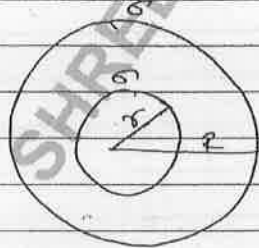

$Q(4\pi r^2) + \sigma(4\pi R^2) = 0$

$\sigma = \frac{Q}{4\pi(R^2 + r^2)}$ ①

$V_C = \frac{\sigma r}{\epsilon_0} + \frac{\sigma R}{\epsilon_0} \Rightarrow V_C = \frac{\sigma(R+r)}{\epsilon_0}$

106)



$\frac{kQ}{r} - \frac{kQ}{3r} = V$

$\frac{2kQ}{3r} = V$ ①


$\frac{kQ}{(3r)^2} = E$ ②
 $E = \frac{V}{3r}$

(116) $\sqrt{3} = PE \sin 30^\circ \dots\dots (1)$
 $U = -PE \cos 30^\circ \dots\dots (2)$

(115) $e^- \xrightarrow{r} e^- \quad (K+U)_i = (K+U)_f$
 $2\left(\frac{1}{2}mv^2\right) + 0 = 0 + K_{fc}$


EX:- (2):-


* (48) $U = K \frac{q_1 q_2}{r}$ $q, 2q$

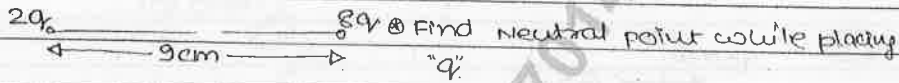

EX:- (3):-

(20) (1) and (2) options both same.

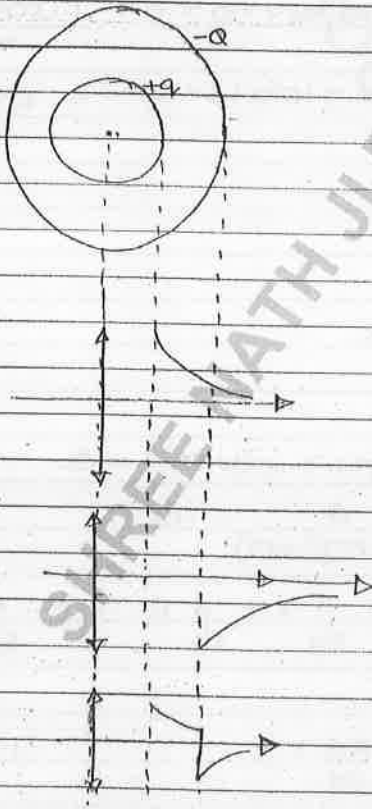

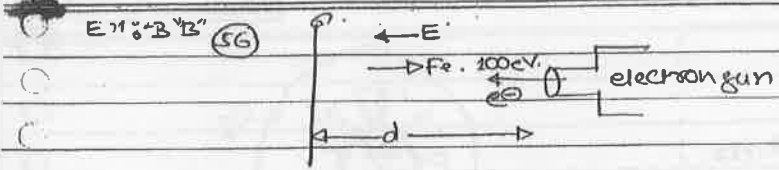


$$\Delta K + \Delta U = 0$$

$$\Delta K = -q(\Delta V)$$

$$0 - 100 \text{ eV} = - (e) (E \cdot d)$$
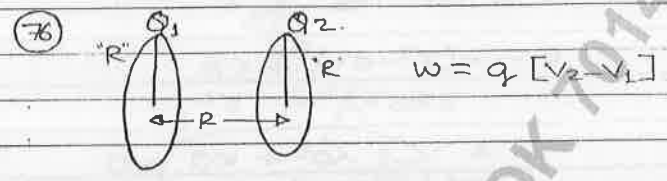
$$= +e \left(\frac{\sigma}{\epsilon_0} \cdot d \right)$$





$$W = q [V_2 - V_1]$$

101

$$\left(\frac{N_A \times 10}{63} \right) \times \frac{1}{10^6} = n$$

$$R \frac{(ne)(ne)}{r^2}$$

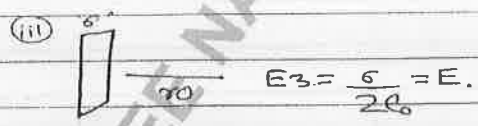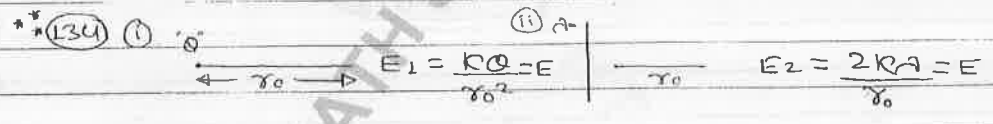

(i) $E_1 = E_3 \Rightarrow \frac{q}{4\pi\epsilon_0 r_0^2} = \frac{\sigma}{2\epsilon_0}$

$$q = \sigma (2\pi r_0^2)$$

(ii) $E_2 = E_3 \Rightarrow \frac{A}{2\pi\epsilon_0 r_0} = \frac{\sigma}{2\epsilon_0}$

$$r_0 = \frac{A}{\sigma}$$


$$\left. \begin{aligned} E_1' &= 4E \\ E_2 &= 2E \end{aligned} \right\} E_1' = 2E_2'$$

$$(128) \int_0^R (4\pi r^2) \cdot dr$$

$$\int_0^R \frac{A \cdot 4\pi r^2 \cdot dr}{r}$$

$$4\pi A \left[\frac{r^2}{2} \right]_0^R$$

$$2\pi A (R^2 - 0)$$

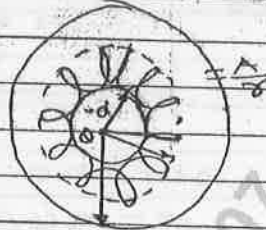

$$\oint \vec{E} \cdot d\vec{s} = \frac{\Sigma q}{\epsilon_0}$$

$$E (4\pi r^2) = \frac{1}{\epsilon_0} \cdot 2\pi A (R^2 - 0)$$

$$E = \frac{A(R^2 - 0)}{2\epsilon_0 r^2} + \frac{RQ}{r^2}$$

$$= \frac{A}{2\epsilon_0} \left(\frac{R^2 + RQ}{r^2} \right) = 0$$

$$\frac{AR^2}{2\epsilon_0 r^2} = \frac{1}{4\pi\epsilon_0} \cdot \frac{Q}{r^2}$$

$$A = \frac{Q}{2\pi R^2}$$

SHREE NATH

SHREE NATH JI BOOK 7014774207

Date _____ Page _____


SHREE NATH JI BOOK 7014774207

SHREE NATH JI BOOK 7014774207

Date _____ Page _____

SHREE NATH JI BOOK 7014774207

★ ⇒ CONDUCTOR WITHOUT BATTERY :-

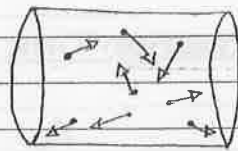

⇒ Due to thermal speed, Free electron perform Random motion, and collide with Metal Ion, so Net Displacement of charge Remains '0' so, charge = 0.

① Free e^- Density (n):-

→ It is No. of Free e^- in "Unit volume of Metal."

$$n = 10^{28} \text{ } e^- / \text{m}^3 \text{ or } (10^{22} \text{ } e^- / \text{cm}^3)$$

→* " n " depends on Nature of Metal.

② Thermal speed ($V_{T\text{ms}}$):-

→ Speeds of Free e^- due to surrounding Temperature.

K.E of one Free e^-

$$\frac{1}{2} m V_T^2 = \frac{3}{2} K T$$

$$V_{T\text{ms}} = \sqrt{\frac{3KT}{m}}$$

∴ If $T = 300 \text{ K}$; $V_T = 10^5 \text{ m/sec}$

∴ Temp. $\uparrow \Rightarrow V_T \uparrow$

③ Relaxation Time (τ):-

The "Average Free Time" b/wn 2 consecutive-collisions

$$\tau = 10^{-14} \text{ sec.}$$


τ depends = ① $T \uparrow \Rightarrow \tau \downarrow$

④ Mean Free Path (λ) :-

Distance covered in ^{1/e⁻} One Relaxation Time.

$$\lambda = 10 \text{ \AA}$$

☆ \Rightarrow CONDUCTOR WITH BATTERY :-

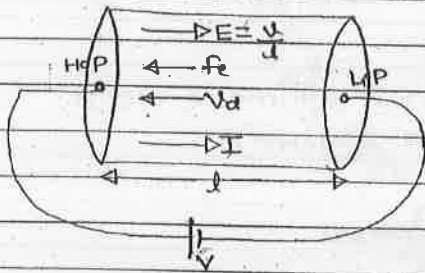

⑤ Drift velocity :- (V_d)

After applying battery, free e^- moves ahead with almost constant velocity is called "Drift velocity".

$$V_d = 10^{-4} \text{ m/sec} = 0.1 \text{ mm/sec}$$

$$V_d = \left(\frac{e\tau}{m}\right) E \Rightarrow V_d = \left(\frac{e\tau}{m}\right) \left(\frac{V}{l}\right)$$

⑥ Mobility (μ) :-


It is drift velocity for unit Applied Electric field.

$$\because E \rightarrow V_d \quad \because \mu = \frac{V_d}{E} = \frac{e\tau}{m}$$

$$\text{Temp} \uparrow \Rightarrow \tau \downarrow \Rightarrow V_d \downarrow \Rightarrow \mu \downarrow$$

⑦ Electric current (I) :-

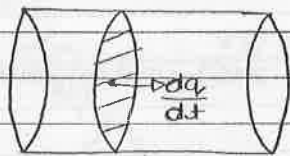It is rate of charge flow, through cross section of current carrying system.



$$I = \frac{dq}{dt}$$

→ scalar

→ unit $\begin{cases} \rightarrow \text{M.R.S} = \text{C/sec, Amperes.} \\ \rightarrow \text{C.G.S} = \text{AbA, Biot (Bi)} \end{cases}$

$$1 \text{ A} = \frac{1}{10} \text{ AbA.}$$

Ques > $q = 3t^2 + 2t$; $I = ?$ at $t = 2 \text{ sec}$.

Ans > $I = \frac{dq}{dt} = 6t + 2 \Rightarrow I(t=2) = 6(2) + 2 = 14 \text{ units}$

Ques > calculate total charge flow from 2sec to 4sec;
 $I = 3t^2 + 2t$?

Ans > $I = \frac{dq}{dt} \Rightarrow dq = I \cdot dt \Rightarrow q = \int I \cdot dt$

$$q = \int_2^4 (3t^2 + 2t) dt$$

$$= \int_2^4 (t^3 + t^2) dt$$

$$= (4^3 + 4^2) - (2^3 + 2^2)$$

$$= (64 + 16) - (8 + 4)$$


$$= 68 \text{ units.}$$

Ques > $Q = at - bt^2$; Find instance when current become "ZERO" ?

Ans > $I = \frac{dQ}{dt} = a - 2bt = 0$

$$\therefore t = \frac{a}{2b}$$

⊗ ⇒ CURRENT DUE TO CIRCULATING CHARGE:-

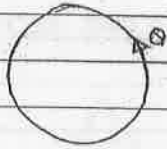


$$v = \omega r$$

$$\omega = \frac{2\pi f}{T} = \frac{2\pi}{T}$$

$$I = \frac{dq}{dt} = \frac{Q}{T} = Qf = Q\omega = Qv$$

$\frac{Q}{2\pi} \cdot \frac{2\pi}{T}$ - used only in this formula.

⊕ ⇒ CURRENT IN CONDUCTOR:-

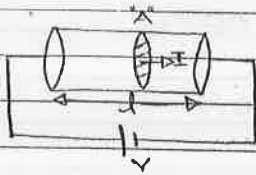

$$I = neAv_d$$

$$\therefore I = \left(\frac{N}{V_0}\right) eAv_d \Rightarrow I = \left(\frac{N}{l}\right) eV_d$$

*** Ex:- $V_d = \frac{I}{neA} = \frac{I}{ne(\pi r^2)}$

$$V_d = \frac{e\tau \cdot v}{m \cdot l}$$

(i) If current (I) = constant $\Rightarrow V_d = \frac{I}{ne(\pi r^2)}$ → (use this only)

$$r' = 2r \Rightarrow V_d' = \frac{V_d}{4}$$


$$l' = 2l \Rightarrow V_d' = V_d \text{ (same)}$$

(ii) If voltage (V) = constant $\Rightarrow V_d = \frac{e\tau \cdot v}{m \cdot l} \Rightarrow V_d = \frac{e\tau \cdot v}{m \cdot l}$ → (use this only)

$$r' = 2r \Rightarrow V_d' = V_d$$

$$l' = 2l \Rightarrow V_d' = \frac{V_d}{2}$$

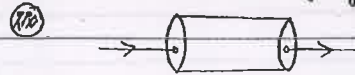
⇒ In current carrying conductor, NO of electrons entering at one end is equal to NO. of e⁻ leaving at other end so; *① current carrying conductor is always neutral.



$$E_{\text{outside}} = 0.$$

$E_{\text{inside}} \neq 0$ (Due to Battery) not wire.

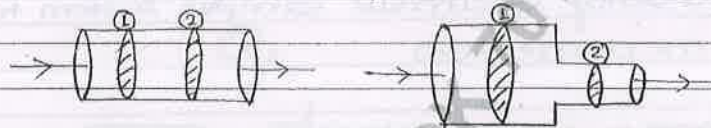*② Current at each point of conductor remains same irrespective of cross-section Area.



$$I_1 = I_2$$

$$I_1 = I_2$$

$$\therefore V_d = \frac{I}{neA}$$

$$\therefore V_d = \frac{I}{neA} \propto \left(\frac{1}{A}\right)^*$$

$$\therefore * V_{d1} = V_{d2}$$

$$\therefore * V_{d1} < V_{d2} \therefore (A_1 > A_2)$$

⑧ CURRENT DENSITY (J) :-

It is current through "unit ^{cross} section Area"

$$J = \frac{I}{A}$$

$$\rightarrow \text{unit} = \text{A/m}^2$$

\rightarrow vector (Along the current flow)



$$\Rightarrow J = \frac{I}{A} = \frac{neAv_d}{A}$$

$$A \rightarrow I$$

$$J = ne \left(\frac{e\tau}{m} \right) E$$

$$l \rightarrow I/A$$

$$J = \left(\frac{ne^2\tau}{m} \right) E$$

$$J = \sigma E$$

9) CONDUCTIVITY OR SPECIFIC-CONDUCTANCE (σ) :-

$$\sigma = \frac{ne^2\tau}{m} = \frac{1}{\rho}$$

" σ " Depends on :- ① Metal.
② Temperature.

10) RESISTANCE (R) :-

It is Tendency of current carrying system to oppose the charge flow.


Resistance = Applied voltage \Rightarrow $R = \frac{V}{I}$
Resulting current.

\rightarrow Scalar Quantity.

\rightarrow Unit = ohm (Ω)

\rightarrow conductance (G) = $\frac{1}{R}$ (ohm⁻¹, mho, siemen)

* \Rightarrow Resistance of conductor :-

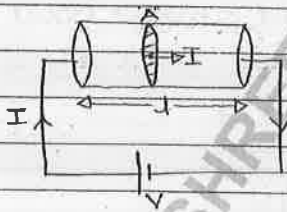

$$I = neA v_d$$

$$= neA \left(\frac{e\tau}{m} \right) \frac{V}{l}$$

$$\frac{V}{I} = \left(\frac{m}{ne^2\tau} \right) \times \frac{l}{A}$$

$$R = \left(\frac{m}{ne^2\tau} \right) \frac{l}{A}$$

$$R = \frac{\rho l}{A}$$

⊗ ⇒ Resistivity (ρ) :-

$$(i) \rho = \frac{m}{ne^2\tau} = \frac{L}{\sigma}$$

$$(ii) \text{unit} = \Omega \times m.$$

(iii) ρ depends on :- (1) Metal.
(2) Temperature.


ex:- Temp. $\uparrow \Rightarrow \tau \downarrow \Rightarrow \rho \uparrow \Rightarrow R \uparrow$.

☆ ⇒ OHM'S LAW :-

At constant Temperature in Metal, current is "Directly Proportional" to Applied voltage.

At; const. Temp. ; $V \propto I$


$$\frac{V}{I} = R = \text{constant}$$

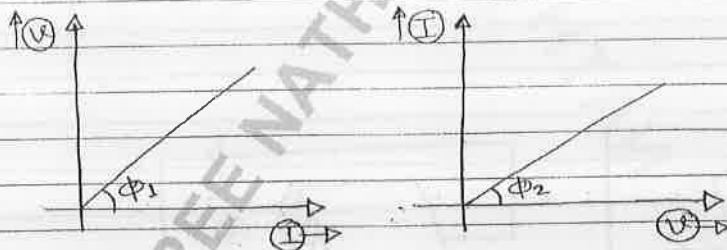

$$\tan \phi_1 = \frac{V}{I} = R$$

$$\tan \phi_2 = \frac{I}{V} = \frac{1}{R}$$

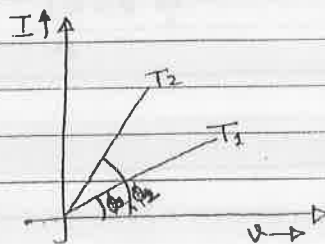* Ex:- For some metal at two temp's; graphs are:



$$\because \phi_1 < \phi_2$$

$$\because \tan \phi_1 < \tan \phi_2 \quad \because \tan \phi = \frac{1}{R}$$

$$\because \frac{1}{R_1} < \frac{1}{R_2}$$

$$\because R_1 > R_2 \quad \because T_1 > T_2$$

★ ⇒ DEPENDANCE OF CONDUCTOR RESISTANCE :-

$$R = \frac{\rho l}{A}$$

① Length :- (l) ⇒ **separation b/w Terminal Point's.

① If Area = const. ⇒ $R = \frac{\rho l}{A} \Rightarrow R \propto l$

② If Volume = const. ⇒ $R = \frac{\rho l}{A} \Rightarrow R = \frac{\rho R}{\text{Volm.}} \Rightarrow R \propto l^2$


② Cross section (A) :-

If $J = \text{const.} \Rightarrow R = \frac{\rho l}{A} \Rightarrow R \propto \frac{l}{A}$

If Vol. = const. ⇒ $R = \frac{\rho \text{Volm.}}{A^2} \Rightarrow R \propto \frac{l}{A^2}$

- ③ Metal } ρ depends.
④ Temp. }

AIEEE
Ques

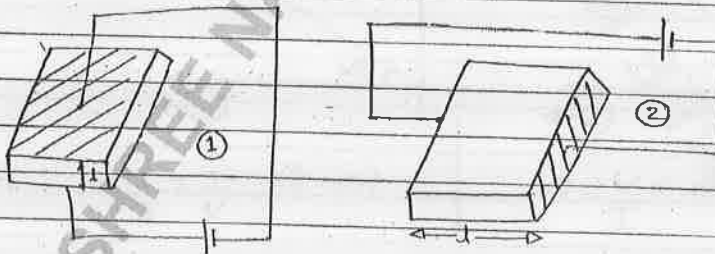


$$\left(\frac{l}{A}\right)_{①} < \left(\frac{l}{A}\right)_{②} \quad \because R = \frac{\rho l}{A}$$

$$\left(\frac{\rho l}{A}\right)_{①} < \left(\frac{\rho l}{A}\right)_{②}$$

$$R_{①} < R_{②}$$

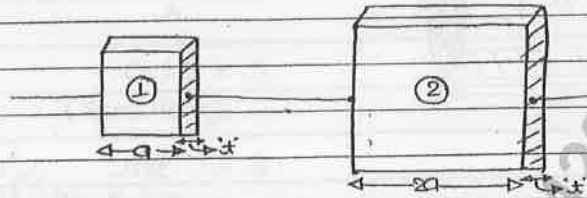Ques > Two square shape metal plates, same metal same thickness are shown, compare their Resistance?



$$R_1 = \frac{\rho(l)}{A} = \frac{\rho}{a \times t}$$

$$R_2 = \frac{\rho(2a)}{(2a \times t)} = \frac{\rho}{a \times t}$$

$$\therefore R_1 = R_2$$

Ques > Find Ratio of Maxm and Minm Resistance b/w Parallel Faces metal Block (2x3x4) cm


$$\text{Ans} \rightarrow \frac{R_{\max}}{R_{\min}} = ? \quad R = \frac{\rho l}{A}$$

$$R_{\max} = \frac{\rho l_{\min}}{A_{\min}} = \frac{\rho (4 \text{ cm})}{(2 \times 3) \text{ cm}} = \frac{\rho \cdot 2}{3}$$

$$R_{\min} = \frac{\rho l_{\max}}{A_{\max}} = \frac{\rho (2 \text{ cm})}{(3 \text{ cm} \times 4 \text{ cm})} = \frac{\rho}{6}$$

$$\frac{R_{\max}}{R_{\min}} = \frac{82 \times 64}{38} \Rightarrow 4:1$$


Ques > Metal Block (1cm x 1cm x 100 cm)

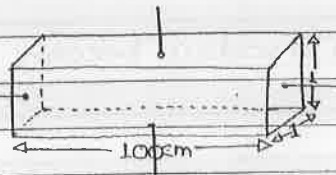

$$R_{\text{square face}} = \frac{\rho (100 \text{ cm})}{(1 \text{ cm} \times 1 \text{ cm})}$$

$$R_{\text{rectang face}} = \frac{\rho (1 \text{ cm})}{(1 \text{ cm} \times 100 \text{ cm})}$$

Ques >

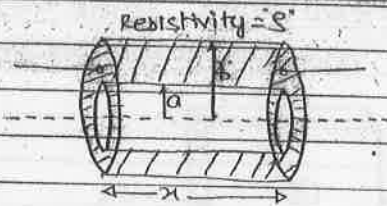


$$R = \frac{Sl}{A}$$

$$R = S(l) \cdot (\pi b^2 - \pi a^2)$$

$$R = \frac{Sl}{\pi(b^2 - a^2)}$$

Ques > 22778 last ques

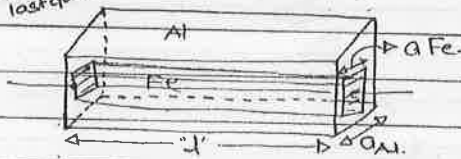

$$R_{Fe} = \frac{S_{Fe} l}{(A_{Fe})^2}$$

$$R_{Al} = \frac{S_{Al} l}{(A_{Al})^2 - (A_{Fe})^2}$$

$$R_{Al} \parallel R_{Fe}$$

*Note:- ① Bending ② Melting ③ compressing ④ stretching
⑤ moulding

In all Above cases volume = constant

Ques > Resistance of a wire = 'R', then Find New Resistance; if:-

① It's length becomes 'n' times by stretching it.

$$\because l' = nl$$

$$\because \text{volume} = \text{constant}$$

$$\because R \propto l^2$$

$$\because \boxed{R' = n^2 R}$$

② By stretching a wire its radius become $\frac{1}{n}$ times;

$$\because r' = \frac{r}{n}$$

$$\because \text{volume} = \text{const}$$

$$\because R \propto \frac{1}{r^4} \Rightarrow \boxed{R' = n^4 R}$$

Ques) By stretching a wire, its length is increased by 50% than % change in Resistance.?

Ans) $l' = l + 0.5l = 1.5l$

∵ volume = constant

$$R \propto l^2$$

$$R' = (1.5)^2 R = 2.25 R$$

$$\% \text{ change} = \frac{2.25R - R}{R} \times 100 = 125\%$$

Ques) By stretching a wire length is increased by 100% than find % change in Resistance?

Ans) ∵ $l' = l + l = 2l$

∵ volume = constant

$$R \propto l^2$$

$$\therefore R' = (2)^2 R = 4R$$

$$\therefore \% \text{ change} = \frac{4R - R}{R} \times 100 = 300\%$$

**Note:- SMALL % change *(upto 5%) at constant volume:-

(i) If $\Delta l = x\% \Rightarrow \Delta R = 2x\%$ $*(R \propto l^2) \checkmark$

(ii) If $\Delta A = x\% \Rightarrow \Delta R = 2x\%$ $*(R \propto A^{-2}) \checkmark$

(iii) If $\Delta r = x\% \Rightarrow \Delta R = 4x\%$ $*(R \propto r^{-4}) \checkmark$

eg: ① By stretching a wire: $l = 3\% \uparrow$ than; $R = 6\% \uparrow$

② By stretching a wire: $r = 2\% \downarrow$ than; $R = 8\% \uparrow$

Ques> By stretching a wire; Length is ↑sed by 10% than
Percentage change in Resistance?

Ans> $l' = l + 0.1l = 1.1l$
 \because volm = const.
 \because $R \propto l^2$
 \because $R = (1.1)^2 R = 1.21R$
 \because $\% = \frac{1.21R - R}{R} \times 100 = 21\%$

EX:- $P = I^2 R$

of $\Delta I = 1\%$ (small change) $\Rightarrow \Delta P = 2\%$

(i) of I $1\% \uparrow$
 \Rightarrow ; P $2\% \uparrow$

(ii) of R $0.5 \downarrow$
 \Rightarrow ; P $1\% \downarrow$

★ \Rightarrow DEPENDENCE OF RESISTANCE ON TEMPERATURE:-

(1) In metals; (conductor)

Temp. $\uparrow \Rightarrow \rho \downarrow \Rightarrow S \uparrow \Rightarrow R \uparrow$

(2) In; semiconductor:-

Temp. $\uparrow \Rightarrow$ No. of charge carrier $\uparrow \Rightarrow R \downarrow$

(3) Temperature Resistance Coefficient (α):-

(i) $\alpha = \frac{\Delta R/R}{\Delta t}$ per unit Temperature, ($^{\circ}\text{C}$ or K)

(ii) If $\alpha = +ve \Rightarrow \text{Temp.} \uparrow \Rightarrow R \uparrow$ eg:- conductor (Met)

If $\alpha = -ve \Rightarrow \text{Temp.} \uparrow \Rightarrow R \downarrow$ eg:- semi-conductor.

If $\alpha = 0 \Rightarrow \text{Temp.} \uparrow \Rightarrow R \text{ (const)}$ eg:- Non-conductor.

(iii) High $\alpha \Rightarrow$ Effect of Temp. on Resistance is High.

$$\alpha = \frac{\Delta R / R}{\Delta t}$$

$$\int_{R_{t_1}}^{R_{t_2}} \frac{\Delta R}{R} = \int_{t_1}^{t_2} \alpha \cdot dt$$

$$R_{t_2} = R_{t_1} [1 + \alpha (t_2 - t_1)] \rightarrow \text{Rarely used (at only } 20^\circ\text{C)}$$

at $t_1 = 0^\circ\text{C}$ and $t_2 = t$

$$R_t = R_0 (1 + \alpha t) \rightarrow \text{Most of the time. (} t = ^\circ\text{C)}$$

⊗ Important Points:-

(i) Temperature should be in $^\circ\text{C}$ only.

(ii) Reference temp. is $0/20^\circ\text{C}$ only.

(iii) These Eqn are valid for "small Temperature Differences".

^{Ques} For a metal; At $300\text{K} \rightarrow R = 1\ \Omega$ than find Temp.
Temp. (Kelvin) $\rightarrow R' = 2\ \Omega$.

Given; $\alpha = 0.00125 \text{ per } ^\circ\text{C}$

$$\text{Ans} \rightarrow 1 = R_0 [1 + \alpha(27)]. \therefore 0^\circ\text{C} \text{ is } 27^\circ\text{C}.$$

$$2 = R_0 [1 + \alpha t] \therefore 0^\circ\text{C} \text{ is } t^\circ\text{C}.$$

$$1 + \alpha t = 2 + 54\alpha.$$

$$\alpha(t - 54) = 2 - 1$$

$$\alpha(t - 54) = 1$$

$$t - 54 = \frac{1}{\alpha} = \frac{1}{0.00125}$$

$$= 800$$

$$t = 854^\circ\text{C}$$

$$t = 854 + 273$$

$$= 1127\text{K}$$

** Ques \rightarrow 2-wires ; wire ① R_1, α_1 } $\alpha_{\text{series}} = ?$
 wire ② R_2, α_2 }

Ans \rightarrow $t^\circ\text{C} \rightarrow R_{\text{series}} = R_1 + R_2$

$t'^\circ\text{C} \rightarrow R'_{\text{series}} = R'_1 + R'_2$

$$= R_1 [1 + \alpha_1(t' - t)] +$$

$$R_2 [1 + \alpha_2(t' - t)]$$

$$= (R_1 + R_2) + (R_1\alpha_1 + R_2\alpha_2)(t' - t)$$

$$(R_1 + R_2) \left[1 + \frac{(R_1\alpha_1 + R_2\alpha_2)}{R_1 + R_2}(t' - t) \right]$$

$$R'_{\text{series}} = R_{\text{series}} \left[1 + \left(\quad \right) (t' - t) \right]$$

$$\alpha_{\text{series}} = \frac{R_1\alpha_1 + R_2\alpha_2}{R_1 + R_2} \quad \checkmark\checkmark$$

** MEE Ques \rightarrow $R_1 = R_2 = R$

then $\alpha_{\text{series}} = \frac{\alpha_1 + \alpha_2}{2}$

** \Rightarrow If series, resistance is "INDEPENDENT OF TEMPERATURE"

in that condition :- $\alpha_{\text{series}} = 0$

$$\frac{R_1\alpha_1 + R_2\alpha_2}{R_1 + R_2} = 0$$

$$R_1 \alpha_1 + R_2 \alpha_2 = 0 \Rightarrow \text{SO; one wire should be "conductor" } (\alpha = \oplus \text{ve}) \text{ and other should must be "semi-conductor" } (\alpha = \ominus \text{ve})$$

$$R_1 = \ominus \alpha_2$$

$$R_2 = \oplus \alpha_1$$


★ ⇒ GRAPHS :-

① Resistance (R) v/s Temperature

$$R_t = R_0 (1 + \alpha t)$$

$$\begin{matrix} \text{"y"} \\ \text{"x"} \end{matrix} \quad \begin{matrix} \text{"c"} \\ \text{"m"} \\ \text{"n"} \end{matrix} \quad \begin{matrix} \text{"x"} \\ \text{"t"} \end{matrix}$$

$$R_t = R_0 + (R_0 \alpha) t$$

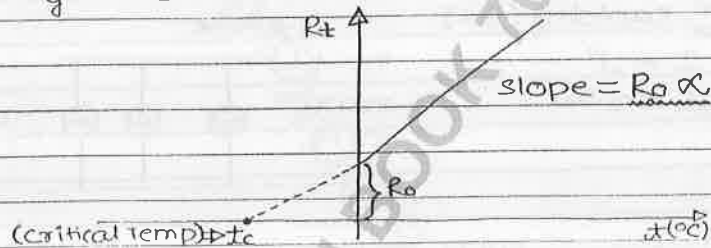

① $t > t_c \Rightarrow R \neq 0 \Rightarrow$ "CONDUCTOR".


② $t \leq t_c \Rightarrow R = 0 \Rightarrow$ "SUPER-CONDUCTOR".

⇒ t_c super-conductor would be feasible (existence) at ordinary temperature than;

- ① A small cell could provide large current. $\because \left[\begin{matrix} \text{I} = \frac{V}{R} = \frac{0.01}{0} \\ = \infty \end{matrix} \right]$
- ② And for "LONG-LASTING" periods.

Note :- $(\text{Hg})_{t_c} = -269^\circ\text{C} (= 4\text{K})$

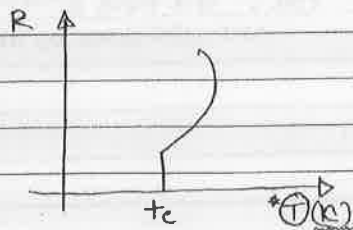t_c — $\begin{cases} \text{"}^\circ\text{C"} & \text{(Always } \ominus \text{ve)} \\ \text{"K"} & \text{(Always } \oplus \text{ve)} \end{cases}$



☆ ⇒ STUDY OF CIRCUITS:-

① ⇒ FUSE WIRE:-


- (i) It is used to protect the circuit's from "Excess current"
 (ii) Always connected in series and at starting of circuit.

⇒ $\frac{Sn}{(83\%)} + \frac{Pb}{(37\%)}$ * Fuse wire should have Low Melting Pt.

(iii) current capacity (I):-

$$\text{AIPMT } I \propto d^2$$

$$* I \propto r^{3/2}$$

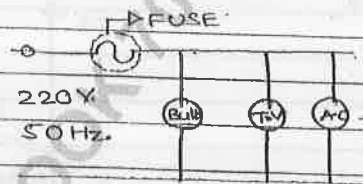

NEET

- Ques > 10 Bulbs ; each 60W
 5 Fans ; each 80W
 1 Heater ; each 1kW (1000W)

$$\text{soln} = P = VI \Rightarrow I = \frac{P}{V}$$

$$I_{\text{total}} = \left(\frac{60 \times 10}{220} \right) + \left(\frac{80 \times 5}{220} \right) + \left(\frac{1000 \times 1}{220} \right)$$

$$I_{\text{total}} = \frac{200}{22} = (9.1) \text{ A.}$$

so; required minimum current capacity of Fuse $\rightarrow (>9.1)$


- ① 9 A ③ 10 A (9.1; 9.5 has given than
 ② 11 A ④ 12 A Ans will goes to that 9.5)

⇒ फिर Battery का ⊕ धरा सब का Plus. (Everywhere)


Date _____ Page _____

② GROUPING OF RESISTANCE :-

SERIES

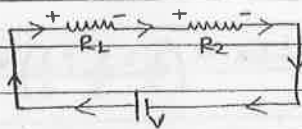

PARALLEL

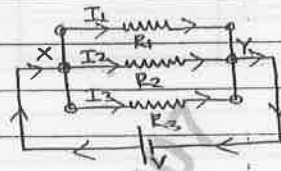

→ $I = \text{same.}$ (Due to single route)

→ $V = \text{same.}$

→ $R_{eq} = R_1 + R_2 + R_3 + \dots$
*(Bigger than the Biggest)

→ $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$

→ voltage distribution: *(I=same)

$R_{eq} = \frac{R_1 * R_2}{R_1 + R_2}$


$V = IR \Rightarrow V \propto R$

↓
*(Smaller than the smallest)



$V_1 : V_2 : V_3 = R_1 : R_2 : R_3$

→ current distributn *(I≠ same)

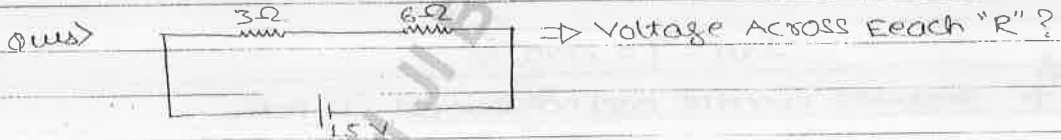
$V = IR \Rightarrow I \propto \frac{1}{R}$



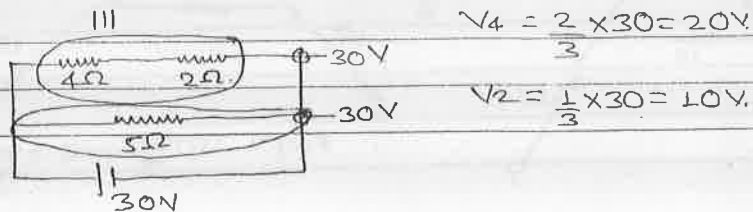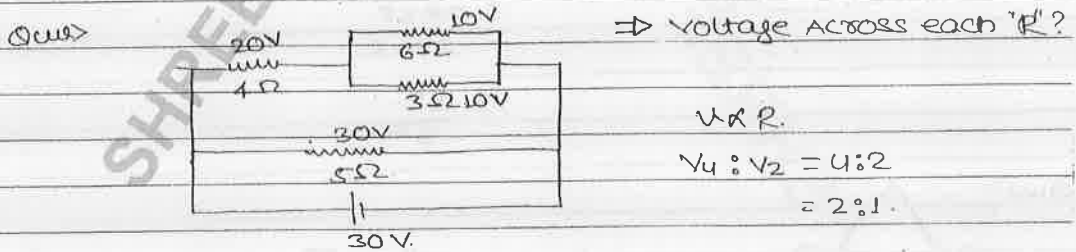Soln ⇒ $V \propto R$
 $V_3 : V_6 = 3 : 6 \Rightarrow 1 : 2$
 $V_3 = \frac{1}{3} \times 15 = 5V$ $V_6 = \frac{2}{3} \times 15 = 10V$



Ques >

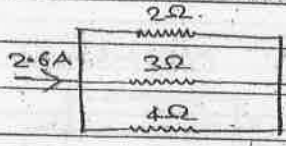

$I \propto \frac{1}{R}$


$I_2 : I_3 : I_4 = \left(\frac{1}{2} : \frac{1}{3} : \frac{1}{4} \right) \times (12) \text{ LCM}$
 $= 6 : 4 : 3$

$I_2 = \frac{6}{13} \times 2.6 = 1.2 \text{ A}$

$I_3 = \frac{4}{13} \times 2.6 = 0.8 \text{ A}$

$I_4 = \frac{3}{13} \times 2.6 = 0.6 \text{ A}$

Ques >

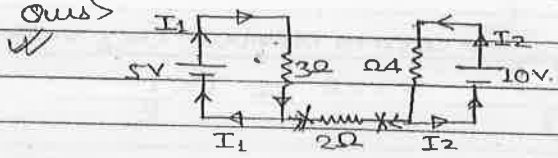


$I_{2\Omega} = ? = \text{zero}$

v.i.m.p

→ Because:- current does not repeat its path.

Ques >

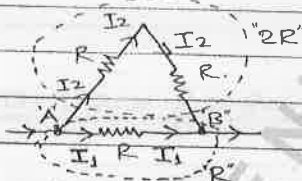



$R_{AB} = ?$

$R_{AB} = 2R \parallel R$

$= \frac{2R \times R}{2R + R}$


$= \frac{2R}{3}$

Ques >

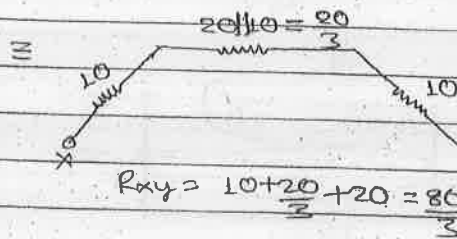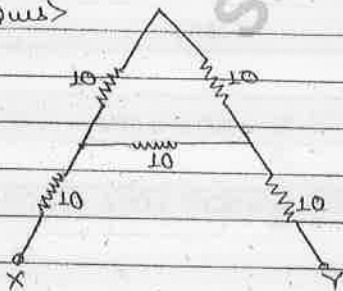

$R_{xy} = 10 + \frac{20 \times 20}{2} + 10 = 80$

Ques >

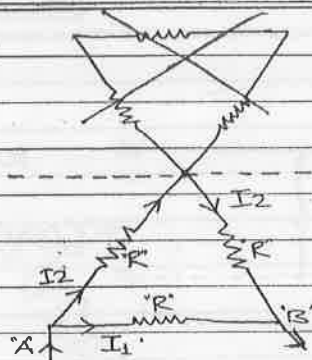


$$R_{AB} = 2R \parallel R$$

$$= \frac{2R \cdot R}{2R + R}$$

$$= \frac{2R}{3}$$

Ques >

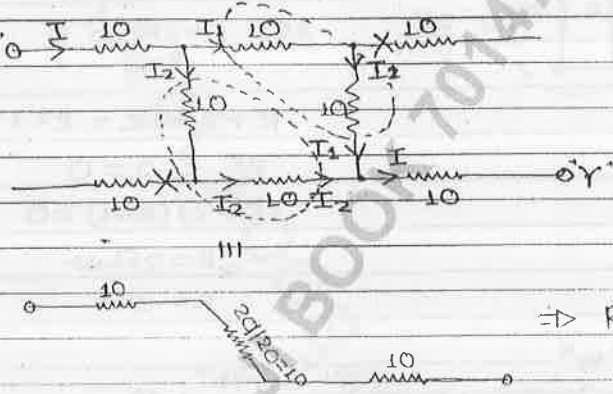


$R_{XY} = ?$

$$\Rightarrow R_{XY} = 10 + 10 + 10$$

$$= 30$$

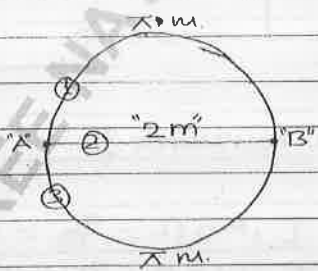**Ques > This loop is made of conducting wire :-



"Radius" = 1m.
Resistance = $\frac{1}{2} \Omega/m$ } $\Rightarrow R_{AB} = 2$

Circumference = $2\pi r = 2\pi \times 1 = 2\pi m$

$$R_{eq} = \frac{2 + 1 + 2}{\pi + 1 + \pi}$$

$$= \frac{2 + \pi + 2}{\pi + 1 + \pi}$$



$\therefore 1m \rightarrow \frac{1}{2} \Omega$

$2m \rightarrow \frac{1}{2} \times 2 = 1 \Omega$

$\pi m \rightarrow \frac{1}{2} \times \pi = \frac{\pi}{2} \Omega$

$$R_{eq} = \frac{\pi}{\pi + 4}$$

⇒ "INFINITE LADDER" :-

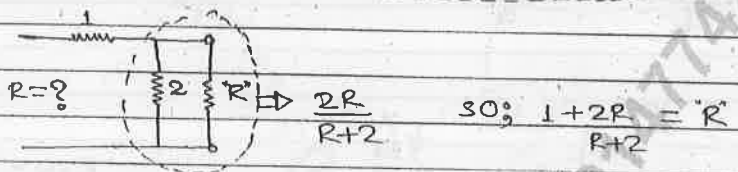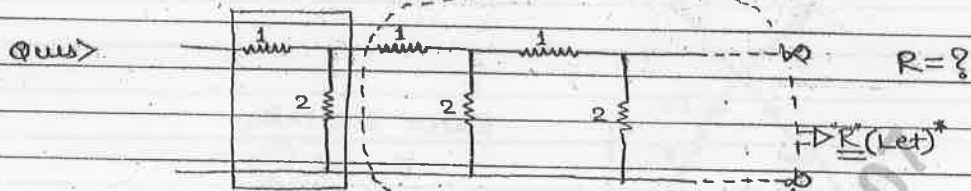


$$R + 2 + 2R = R^2 + 2R$$

$$R^2 - R - 2 = 0$$


$$(R - 2)(R + 1) = 0$$

$$R = 2\Omega$$

$$R = -1\Omega$$

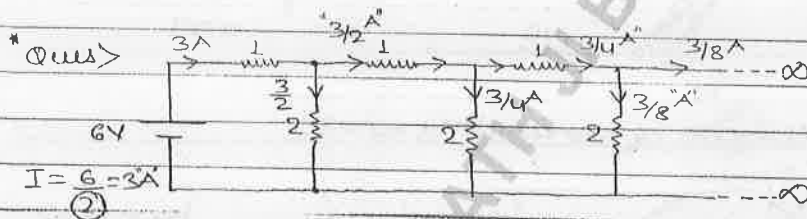

Find current in 1st 2Ω Resistance?

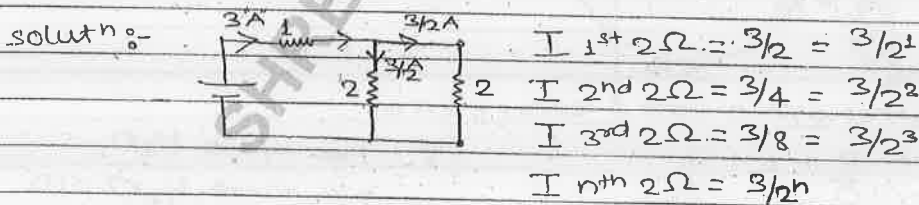



$$I_{1^{st}} 1\Omega = 3 = 3/2^0$$

$$I_{2^{nd}} 1\Omega = 3/2 = 3/2^1$$

$$I_{3^{rd}} 1\Omega = 3/4 = 3/2^2$$

$$I_{n^{th}} 1\Omega = \frac{3}{2^{n-1}}$$


⊛ ⇒ SHORT CIRCUIT (CKT) :-

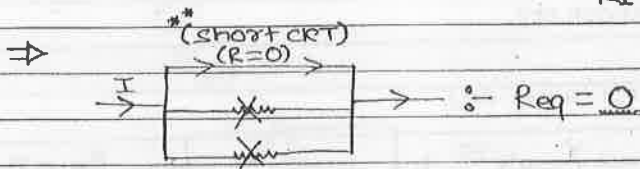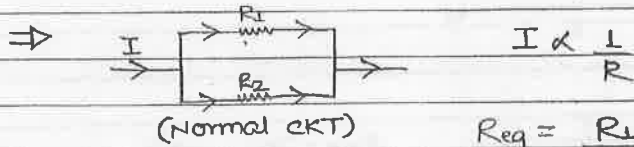


CONCLUSION:-

- ① It is the path of "zero" (0) resistance so total current passes through it.
- ② so; All component parallel to short circuit are useless.

⊛ ⇒ OPEN CIRCUIT (CKT) :-

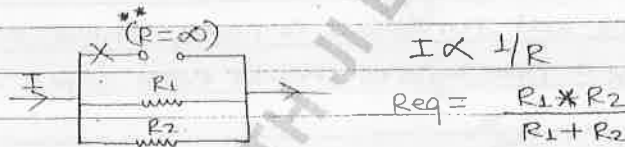



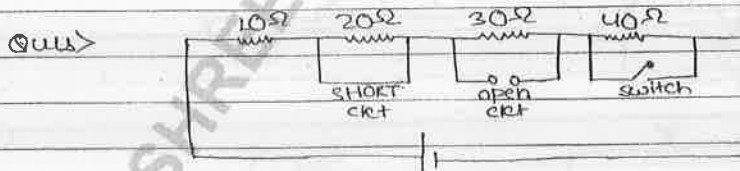
→ It is path of $R = \infty$; so, current is zero through it.



- ① switch off:- $R_{eq} = 10 + 0 + 30 + 40 = 80 \Omega$.
- ② switch on:- $R_{eq} = 10 + 0 + 30 + 0 = 40 \Omega$

$\frac{R \times R}{3R}$

Date _____ Page _____

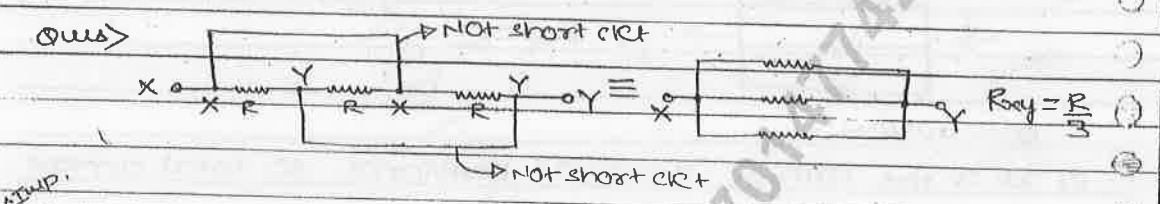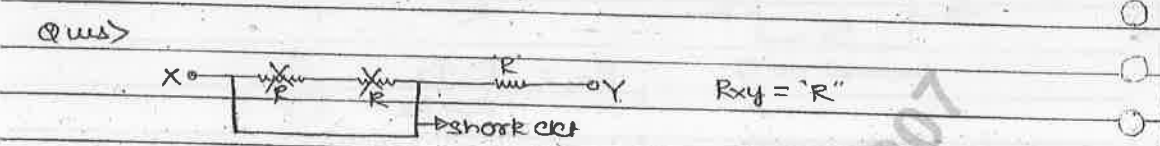
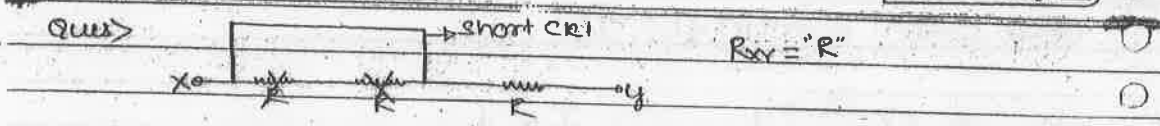


IMP. \Rightarrow Point Potential method :-

usefull in ckts having Direct wire (component (R) Free)

step 1 :- Numbering of all Junctions is done, where Junction connected by a Direct wire should have same No.

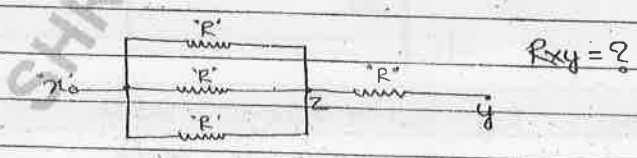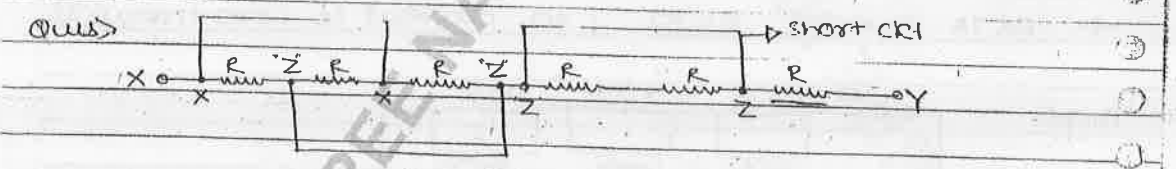step 2 :- Rearranged the ckts component in the new Diagram




$$R_{xy} = \frac{R + R}{3} = \frac{4R}{3}$$

$$\frac{2R \times 2R \times R}{5R} = \frac{4R}{5}$$

Date _____ Page _____

Ques >

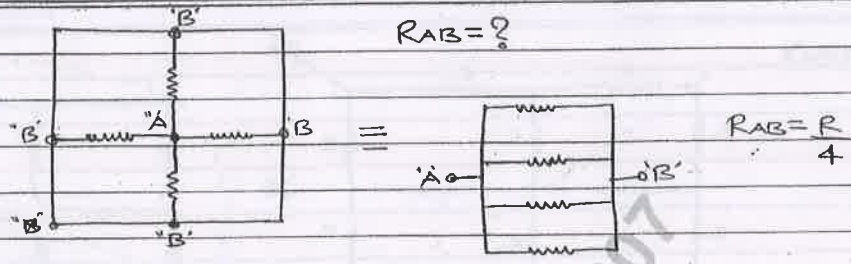


★ ⇒ SYMMETRICAL LINE METHODS:-

Only Useful in symmetrical circuits.

step: ①: Draw the "⊥ Bisector" of the line, joining terminal point's. And this symmetrical line should must divide the ckt into "TWO MIRROR IMAGES".


step: ②: stretch the ckt along symmetrical line to remove all junction lying on symmetrical line.

Ques >

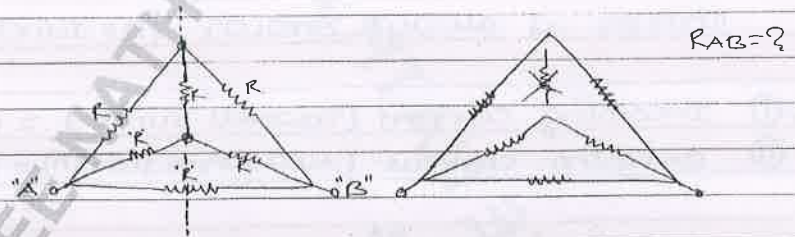


$$R_{AB} = 2R \parallel 2R \parallel R = R/2$$

Ques >

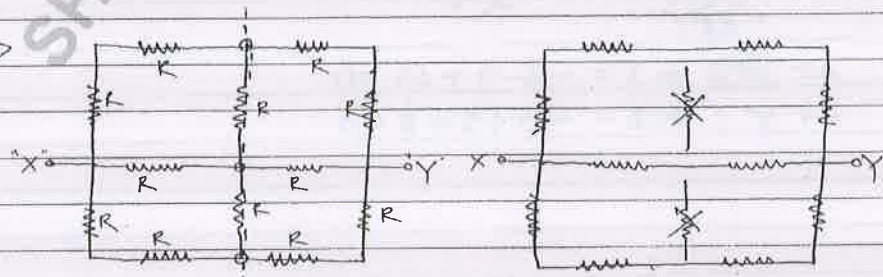
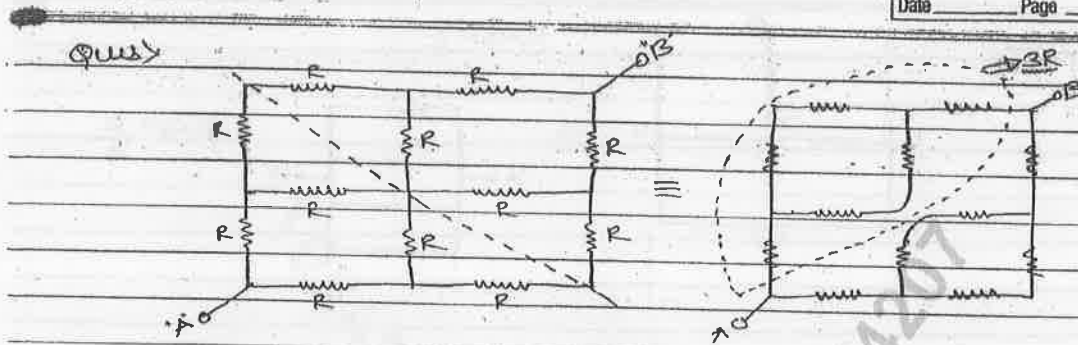
$$R_{XY} = 4R \parallel 2R \parallel 4R = "R"$$



$$R_{AB} = 3R \parallel 3R = 1.5R$$

★ \Rightarrow KIRCHOFF'S LAW :- $\begin{cases} \rightarrow \text{KVL} \\ \rightarrow \text{KCL} \end{cases}$

① First / current / Junction Law (K.C.L) :-

\rightarrow * Based on "charge conservation."

\rightarrow At junction "Algebraic sum" of all current "or" all charges is always zero (0). [At Junctn = $\sum I = 0$]


✓ (i) Incoming current (Towards Junctn) = \ominus ve.

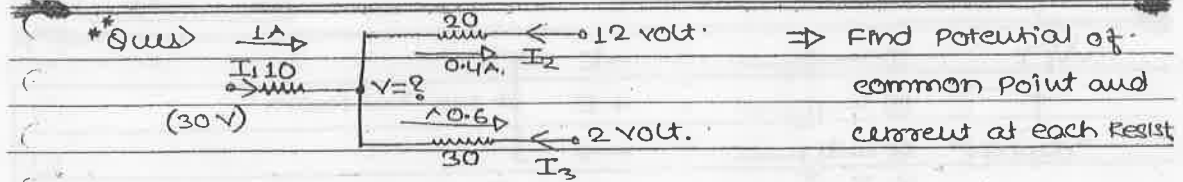(ii) Outgoing current (Away from Junctn) = \oplus ve.



$$\text{At } 'X'; \sum I = -3 - 7 + 10 = 0$$

$$\text{At } 'Y'; \sum I = -10 + 2 + 8 = 0$$



By KCL:-

$$\sum I = 0$$

$$-I_1 - I_2 - I_3 = 0$$

$$I_1 + I_2 + I_3 = 0$$

$$\left(\frac{30-V}{10}\right) + \left(\frac{12-V}{20}\right) + \left(\frac{2-V}{30}\right) = 0$$

$$180 - 6V + 36 - 3V + 4 - 2V = 0$$

$$220 = 11V \Rightarrow V = 20 \text{ Volt.}$$

$$I_1 = \frac{30-V}{10} = \frac{30-20}{10} = 1A \text{ (1A, towards Junction)}$$

$$I_2 = \frac{12-20}{20} = -0.4A \text{ (0.4A, Away from Junction)}$$

$$I_3 = \frac{2-20}{30} = -0.6A \text{ (0.6A, Away from Junction)}$$

(2) second / voltage / Loop Law (KVL):-

(i) Based on "energy conservation".

(ii) "Algebraic sum" of all Potential Differences (P.Ds) is always zero (0) in a close loop.

$$\text{In close loop: } \sum \text{P.D's} = 0$$

\Rightarrow Sign convention:-


\rightarrow (+) to (-) = \ominus ve (se always's final positⁿ)

\leftarrow (-) to (+) = \oplus ve


⇒ "KVL" BETWEEN TWO POINTS:-

Potential of "Initial point" ± (AU PD's) = Potential of Final point.

NEET
Ques >
2010

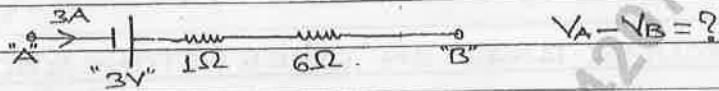


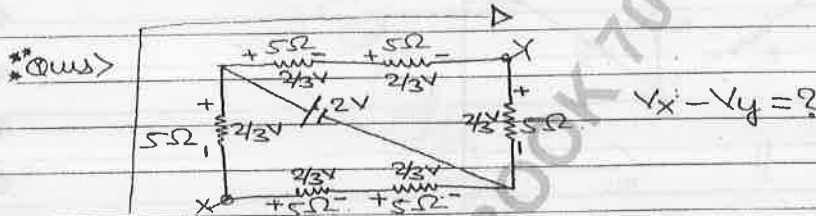Ans > $V_A + 3 - 3 \times 1 - 3 \times 6 = V_B$
 $V_A - V_B = 18 \text{ VOLT}$



soln :- $V_x + \frac{2}{3} - \frac{2}{3} - \frac{2}{3} = V_y$
 $V_x - V_y = \frac{2}{3} = 0.67 \text{ V}$

Ques >

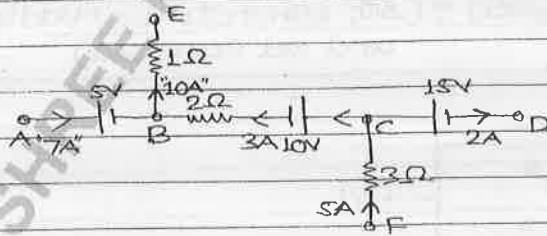


① $V_A - V_B = ?$
 $V_A - 5 + 2 \times 3 + 10 - 15 = V_D$
 $V_A - V_D = 4$

$$(ii) V_E - V_F = ?$$

$$V_E + 10 + 3 \times 2 + 10 + 5 \times 3 = V_F$$

$$V_E - V_F = -41$$

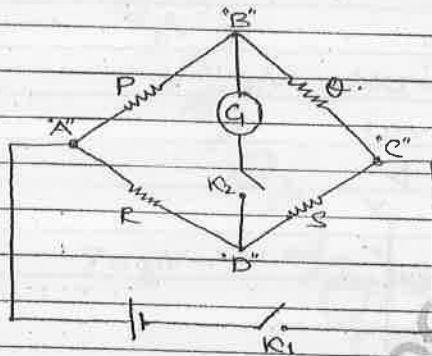★ ⇒ CIRCUITS BASED ON "WHEATSTONE BRIDGE" :-



*** V.I.M.P. ***
 CASE :- (1) ⇒ "BALANCE" BRIDGE :-


$$\text{If; } P = R$$

$$Q = S$$

$$\Rightarrow V_B = V_D$$

$$\Rightarrow I_{\text{MIDDLE}} = 0 \quad \because \text{(So, eliminate the middle arm and get result out)}$$


Ques >

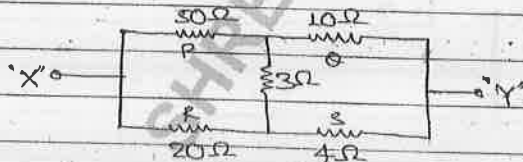

$$\because \frac{50}{10} = \frac{20}{4} \quad \because \text{(Balanced wheatstone bridge)}$$

$$R_{xy} = 60 \parallel 24 = \frac{120}{7}$$

*Ques>

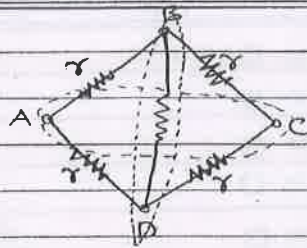

(i) $R_{AC} = ?$


(ii) $R_{BD} = ?$

(i) $R_{AC} =$ "Balance" Wheatstone Bridge

* (ii) $R_{BD} =$ It is "Not-wheatstone bridge" but it is 3-parallel path; so:-

$$R_{BD} = 2r \parallel r \parallel 2r = r$$



Ques>

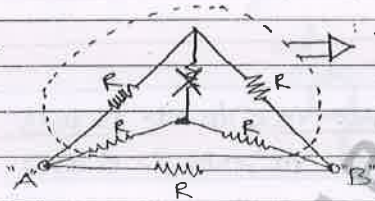

"Balanced" wheatstone bridge
(symmetrical in 2ft chahaga)

$$R_{AB} = 2r \parallel 2r \parallel r = r/2$$


*Ques> all $R = r$

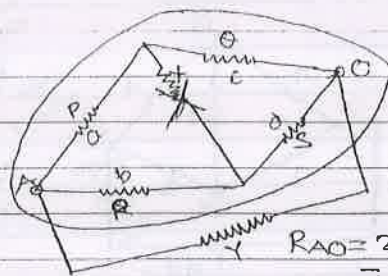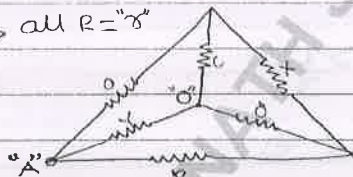

$$R_{AO} = 2r \parallel 2r \parallel r = r/2$$

Reason's: Remove the resistance b/w "A" & "O" and "unfold" the ckt as shown above.

AIMS Ques

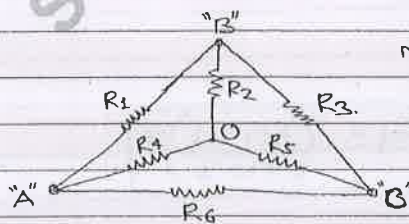

Note: $R_1 = R_2 = R_3 = R_4 = R_5 = R_6$

in which "resistance" current is "0" if Battery is Applied b/w n (1)

Soln: (i) $A \times C \Rightarrow I_{R2} = 0$

(ii) $A \times B \Rightarrow I_{R5} = 0$

(iii) $B \times C \Rightarrow I_{R4} = 0$

(iv) $A \times O \Rightarrow I_{R3} = 0$

(v) $B \times O \Rightarrow I_{R6} = 0$

(vi) $C \times O \Rightarrow I_{R1} = 0$

* Not Imp for Exam
Case: (2) \Rightarrow "UNBALANCED" WHEATSTONE BRIDGE :-


$$g \frac{P}{Q} \neq \frac{R}{S}$$

$$\Rightarrow V_B \neq V_D$$

$$\Rightarrow I_{\text{middle}} \neq 0$$

$$* \begin{cases} \triangleright g \frac{P}{Q} > \frac{R}{S} \Rightarrow V_B < V_D \Rightarrow D \text{ to } B \\ \triangleright g \frac{P}{Q} < \frac{R}{S} \Rightarrow V_B > V_D \Rightarrow B \text{ to } D \end{cases}$$

Ques \rightarrow

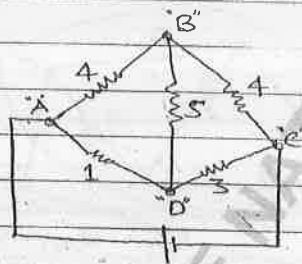


$$\because \frac{4}{4} > \frac{1}{3}$$

$$\because V_B < V_D$$

$$\because I_{\text{middle}} \neq 0 \text{ (D to B)}$$


* \Rightarrow Equivalent Resistance:

(i) KVL

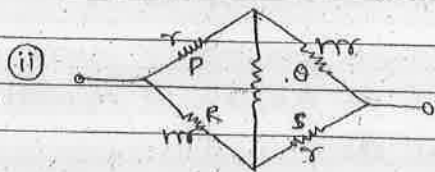

$$R_{eq} = \frac{(3n+1)r}{n+3}$$

Ques >

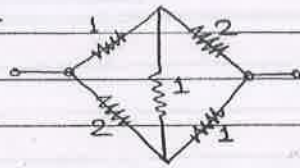

$$\because r=1 \quad \because n=2$$

$$R_{eq} = \frac{(3n+1)r}{n+3} = \frac{7}{5} = 1.4 \Omega$$


⊗ ⇒ SHORTCUT'S :- (For unbalanced wheat stone bridge) :-

→ Eliminate the "Middle Arm" and Get Equivalent Resista. (which is Approx Answer) or than;

① Req. is slightly less than Rapprox.

② Ceq. is slightly more than Capprox.

Ques >

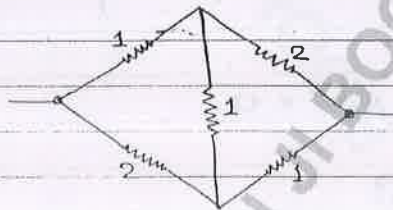

$$R_{approx} = 3 \parallel 3 = 1.5 \Omega$$

Req. is "slightly less" than 1.5
 ≈ 1.4

⊗ ⇒ IMPORTANT POINTS OF WHEATSTONE BRIDGE :-

① In balance condition; Battery Branch and Galvanometer Branch are Interchangeable.


② To avoid the confusion (Due to Induced current), Battery Key is made ONN 1st (First), > than ② key
about difflectn in ②

③ It is most sensitive, if all ④ Resistance are made up of same value. (not same order).

R → Resistance & R → Reduced

Date _____ Page _____

⇒ FOR: CUBE:-

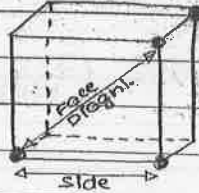

Each resistance = "R"

Each capacitance = "C"

$R_{\text{main diagon. (largest)}} = \frac{5R}{6} = 0.82$ "Impo."

$C_{\text{main Diagon.}} = \frac{6C}{5} = 1.5$ "Not so imp"


$R_{\text{face Diagon. (medium)}} = \frac{3R}{4} = 0.75$

$C_{\text{face Diagon.}} = \frac{4C}{3} = 1.3$

$R_{\text{side (smallest)}} = \frac{7R}{12} = 0.58$

$C_{\text{side}} = \frac{12C}{7} = 1.7$

Ques)

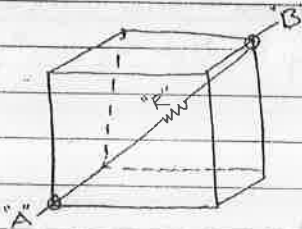

Each side = a

$R_{AB} = ?$


soln = $R_{AB} = \frac{5R}{6}$

$\frac{1}{R_{AB}} = \frac{1}{R} + \frac{6}{5R} = \frac{11}{5R}$



⊗ ⇒ Earthing :-

	V_B	V_A
B A	+5	0
5V	+8	+3
(PD)	-5	-10
	0	-5


P.D = Higher - Lower Potent. Potent.

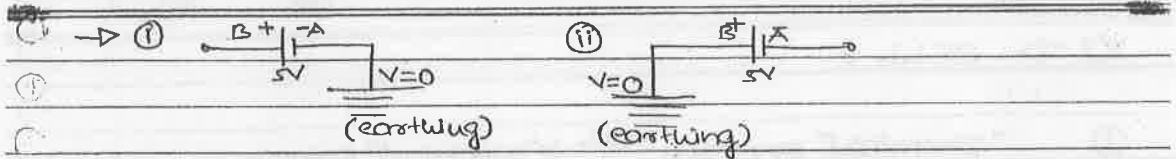

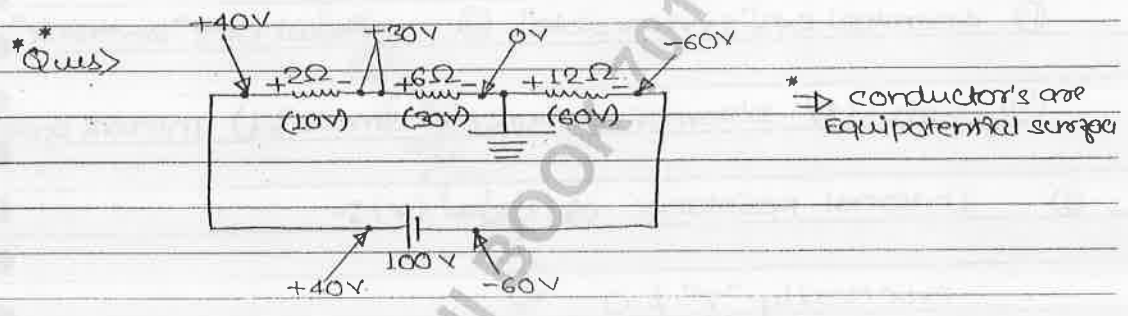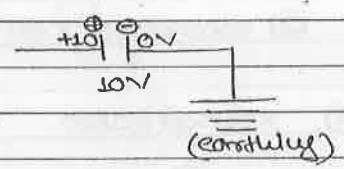$V_A = 0$ (earthing) $V_B = 0$ (earthing).
 $V_B = +5$ $V_A = -5$



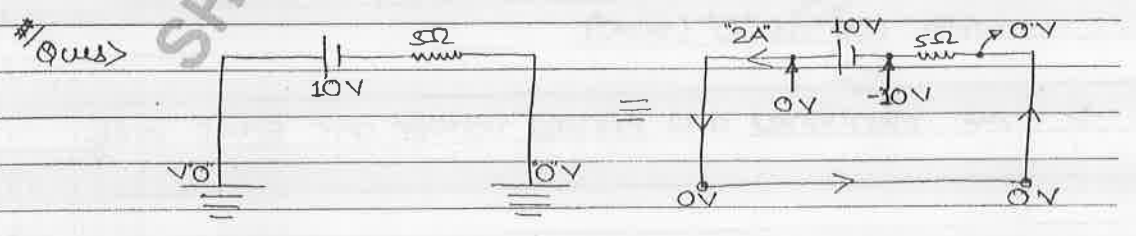soln :- $V_2 : V_6 : V_{12} = 1 : 3 : 6$
 $V_2 = \frac{1}{10} \times 100 = 10V$
 $V_6 = \frac{3}{10} \times 100 = 30V$
 $V_{12} = \frac{6}{10} \times 100 = 60V$



☆ ⇒ CELL :-

(i) "chemical" Energy $\xrightarrow{\text{CELL}}$ "Electrical" Energy.

(ii) cell \rightarrow (2) types :-

(1) Primary cell's

(2) secondary cell's

(i) Not Rechargeable

(i) Rechargeable

(ii) chemical Rxn's "Irreversible"

(ii) chemical Rxn's "Reversible"

(iii) High ($\uparrow\uparrow$) Internal Resistance. (iii) small ($\downarrow\downarrow$) Internal Resistg.

(1) Internal resistance of CELL (γ) :-

Practically " γ " $\neq 0$

Ideal cell " γ " = 0

(2) EMF (E) :-

\rightarrow It is "work done" by cell in Rotating Unit (1) charge in complete "CLOSE LOOP".

\rightarrow It is P.D. between cell Terminal, when current with cell is "0" (zero).

\rightarrow All mentioned and printed voltage are E.M.F only.


* (S) Terminal voltage (V) :-

at is PoD b/w cell Terminal, when current with cell is "Non-zero".

$$V = E - I\gamma \quad \text{: (Discharging) } \leftarrow \text{ (see } \oplus \text{ only)}$$

$$V = E + I\gamma \quad \text{: (charging) } \rightarrow \text{ (see } \oplus \text{ only)}$$

Ques >

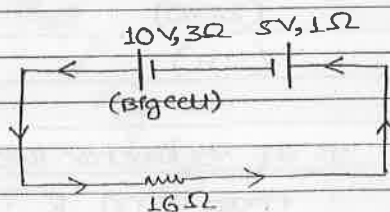

⇒ Find terminal voltage of each cell?

solutn:- $I = \frac{10 - 5}{3 + 16 + 1} = \frac{5}{20} = 0.25 \text{ A}$

10V cell: $V = E - I\gamma$
 $= 10 - 0.25 \times 3$
 $= 9.25 \text{ volt.}$

5V cell: $V = E + I\gamma$
 $= 5 + (0.25) \times (1)$
 $= 5.25 \text{ volt.}$

Ques > A cell (E, γ); Find Terminal voltage (V) of


- (i) cell is "short" circuited.
- (ii) cell is "OPEN" circuited.

Ans > (i) cell short CRT.

∴ $I = E/\gamma$

$V = E - I\gamma \Rightarrow E - \left(\frac{E}{\gamma}\right)\gamma$


$V = 0$

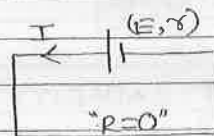

(ii) ∴ $I = 0$

$V = E \oplus I\gamma$

$V = E$

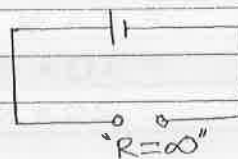

~~Imp~~
 ** \Rightarrow Important Point of Terminal voltage :-

(i) Terminal voltage of cell may be :- more or less or Equal to E.M.F. And even it can be zero.


charging $\Rightarrow V = E + I\gamma$ ($>E$)

discharging $\Rightarrow V = E - I\gamma$ ($<E$)

short CRT $\Rightarrow V = 0$ (zero)

open CRT $\Rightarrow V = E$ ($=E$)

IMPNT
 NIEEE
 Ques \rightarrow
 **

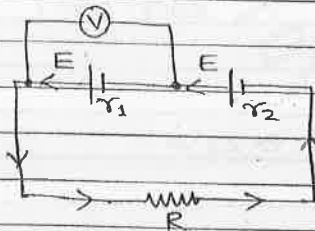

\Rightarrow If voltmeter reading = 0
 than find 'R' ?

$$I = \frac{E + E}{R + r_1 + r_2} = \frac{2E}{R + r_1 + r_2}$$

$$V_1 = E_1 - I_1 r_1$$

$$\because V_1 = 0 \quad 0 = E - \left(\frac{2E}{R + r_1 + r_2} \right) (r_1)$$


$$E = \frac{2E \cdot r_1}{R + r_1 + r_2}$$

$$\boxed{R = r_1 - r_2}$$

(4) "CURRENT CAPACITY" OF CELL (Ah) :-

$$\begin{aligned} \text{EX: } 10 \text{ Ah} &= 1 \text{ A} \times 10 \text{ hours,} \\ &= 2 \text{ A} \times 5 \text{ hours,} \\ &= 5 \text{ A} \times 2 \text{ hours,} \\ &= 10 \text{ A} \times 1 \text{ hours,} \\ &= 20 \text{ A} \times \frac{1}{2} \text{ hours.} \end{aligned}$$

☆ \Rightarrow cell circuit (ckt) :-

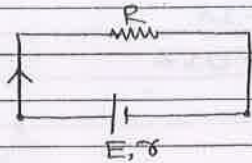

$$(i) I_{ckt} = \frac{E}{R+r}$$

$$(ii) I_{max} = \frac{E}{r} \text{ (when } R=0)$$

\Rightarrow " I_{max} " = maxm current A cell can delivered.

$$(iii) V = E - I r$$

$$(iv) r = ? \quad \because V = E - I r$$

$$= E - \left(\frac{E}{R+r} \right) r$$

$$\boxed{r = \left(\frac{E-V}{V} \right) R}$$

$$(v) P_{load} = ?$$

$$P_{load} = I^2 R$$

$$= \left(\frac{E}{R+r} \right)^2 R$$

(vi) For P_{max} at load :-

$$\frac{dP}{dR} = 0 \Rightarrow \boxed{R=r}$$

$$\boxed{P_{max} = \frac{E^2}{4r}}$$

* Ques > A cell, (E, r)

if load = 1Ω \Rightarrow current = 1A

if load = 3Ω \Rightarrow current = 0.5A

then; find (i) $r = ?$ & $E = ?$


Ans > $I = \frac{E}{R+r}$ $0.5 = \frac{E}{3+r}$ (ii)

$1 = \frac{E}{1+r}$ (i) $E = 2\text{VOLT}$
 $r = 1\Omega$ } \leftarrow

(ii) Find max'm current the cell's can delivered?

$I_{\text{max}} = \frac{E}{r} = 2\text{A}$

* Ques >

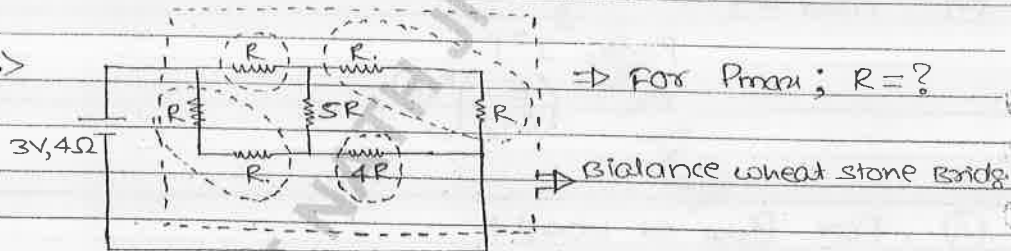

$R_{\text{load}} = 3R \parallel 6R = 2R$


Then for P_{max} :-

$R_{\text{load}} = r_{\text{eq}}$

$2R = 4$

$R = 2\Omega$

Ques →

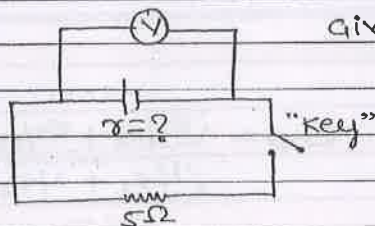Given; If Key OFF $\Rightarrow V = 2.2$ volt.If Key ON $\Rightarrow V = 1.8$ volt. \therefore Find $r = ?$

Ans → Key OFF $\Rightarrow V = 2.2$ volt $\Rightarrow E = 2.2$ volt.
 Key ON $\Rightarrow V = 1.8$ volt $\Rightarrow E = 1.8$ volt.

$$(i) \quad r = \frac{(E - V)R}{V} = \frac{10}{9} \Omega$$

$$(ii) \quad I_{max} = \frac{E}{r} = \frac{2.2}{10/9} = 1.98 \text{ A.}$$


(iii) $R \neq r$ (So; Power at Load is "not Maxm.")★ \Rightarrow GROUPING OF CELLS :-

(1) SERIES :-



$$E_{net} = E_1 + E_2 + E_3 + \dots$$

$$r_{net} = r_1 + r_2 + r_3 + \dots$$

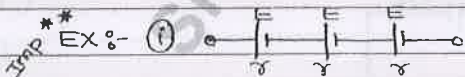

$$E_{net} = E + E + E = 3E$$


$$r_{net} = r + r + r = 3r$$



$$E_{net} = +E + E - E = E$$

$$r_{net} = r + r + r = 3r$$

② PARALLEL :-

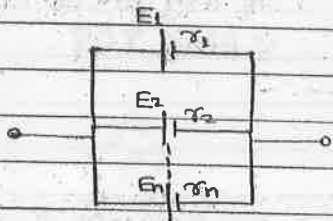


$$E_{net} = \frac{E_1}{r_1} + \frac{E_2}{r_2} + \dots + \frac{E_n}{r_n}$$

$$\frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}$$

$r_{net} = ||$ Resultant of all r_i 's

EX:-

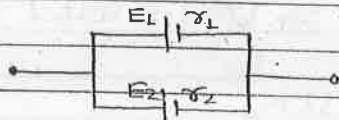


$$E_{net} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$$

$$r_{net} = \frac{r_1 r_2}{r_1 + r_2}$$

* Note:- $E_1 < E_{net} < E_2$ always.

Ques)

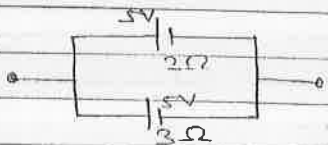


$$E_{net} = \frac{(5)(3) + (5)(2)}{3+2}$$

$$= \frac{15+10}{5} = 5V$$

** \Rightarrow In Parallel grouping of cells having same EMF (E) and of same Polarity then $E_{net} = E$.

Ques)

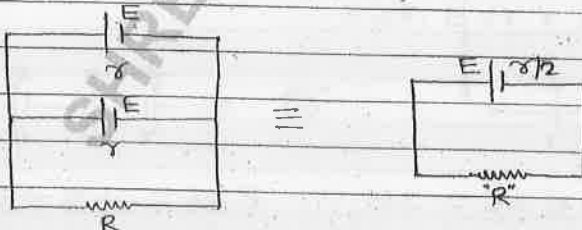


∴ For Pmax :- $R_{eq} = r_{eq}$

$$\boxed{R = \frac{r}{2}}$$

*Ques > (8) identical cells (E, r)

voltmeter reading = ?

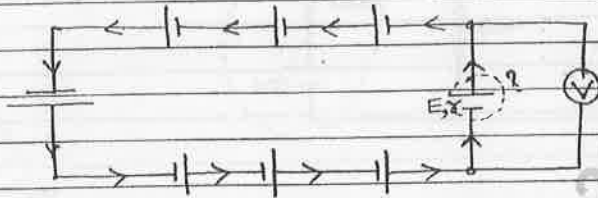

Soln = $I = \frac{8E}{8r} = \frac{E}{r}$


$V = E - Ir$

$= E - \left(\frac{E}{r}\right)r$

of that particular cell, for which we are measuring P.D. or Terminal voltage

$V = 0$


Ques >

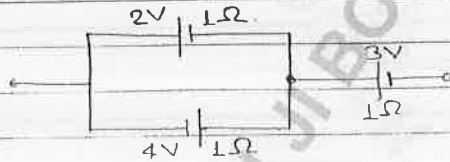


⇒ Find Equivalent cell = ?

Ans > $E_{net} = \frac{(+2)(1) + (-4)(1)}{1+1} = -1V$

$r_{net} = 1 || 1 = \frac{1}{2} \Omega$

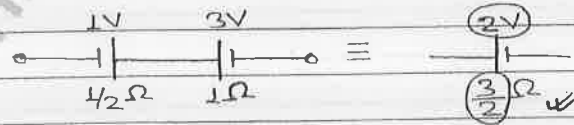


Ques >

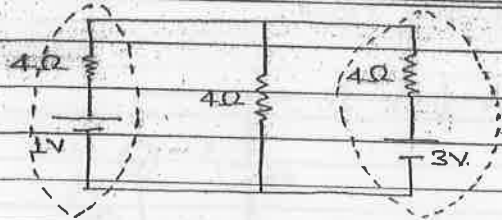


$I_{\text{middle}} = ?$
 4Ω

Ans >

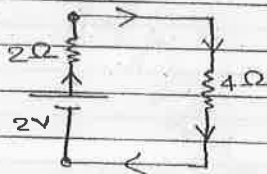


$I = \frac{2}{2+4} = \frac{1}{3} \text{ A}$

Ques >

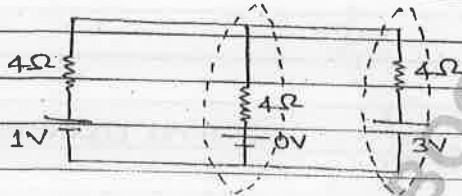

$I_{\text{left}} = ?$
 4Ω

Ans >

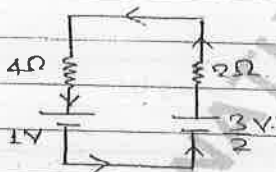

$I = \frac{3/2 - 1}{4+2} = \frac{1}{12} \text{ A}$

SHREE WITHJI BOOK 701471207



★ ⇒ "HEATING" EFFECT OF CURRENT :-

(i) Heat (H) = $I^2 R t = \frac{V^2}{R} \times t = V I t$. Joule * always in Joule
 [∵ t = time]

(ii) 1 cal = 4.2 Joule.

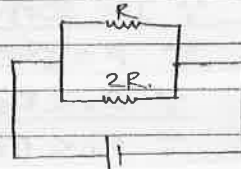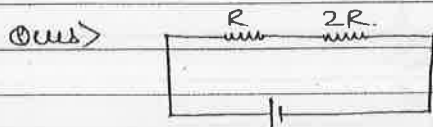
(iii) Electric Power (P) = Ratio of Heat Production.

$P = I^2 R = \frac{V^2}{R} = V I \frac{J}{sec}$ or Watt




soln > ∵ I = same
 $P = I^2 R \propto R$
 $\frac{P_1}{P_2} = \frac{1}{2}$

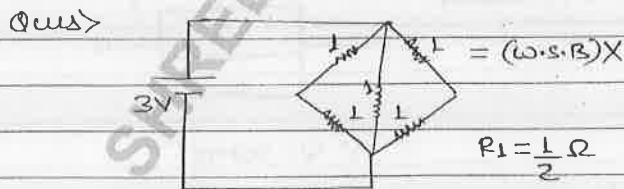
∵ V = same.
 $P = \frac{V^2}{R} \propto \frac{1}{R}$
 $\frac{P_1}{P_2} = \frac{2}{1}$





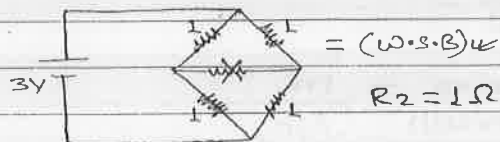
∵ V = same
 ∵ $P = \frac{V^2}{R} \propto \frac{1}{R}$ (B)



∵ $R_3 > R_2 > R_1$
 ∵ $P_3 < P_2 < P_1$

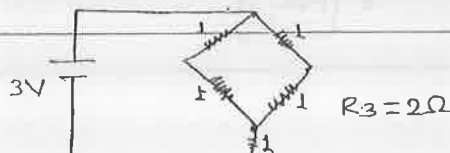

Ques >

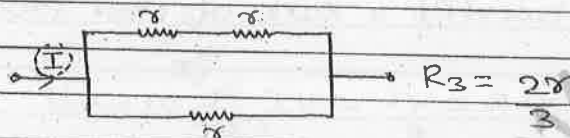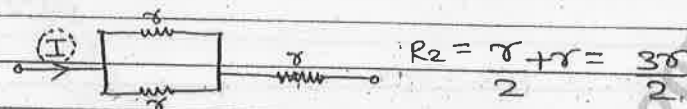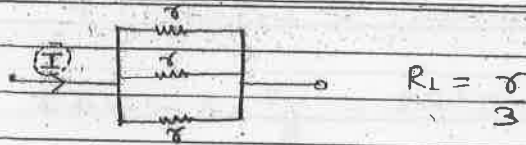

soln > ∴ I = same.

∴ $P = I^2 R \propto R$

∴ $R_1 < R_3 < R_2$

∴ $P_1 < P_3 < P_2$

*Ques > n identical resistance R are connected in series than in parallel, if "same supply voltage" is applied then

$$\frac{\text{Heat (parallel)}}{\text{Heat (series)}} = ?$$

Ans >



∴ $V = \text{same}$



∴ $V = \text{same}$

$$H = \frac{V^2}{R} \times t \propto \frac{1}{R}$$

$$\frac{H(\text{parallel})}{H(\text{series})} = \frac{R(\text{series})}{R(\text{parallel})} = \frac{nR}{R/n}$$

$$= \boxed{n^2 : 1}$$

⇒ * Always keep the Units while solving Question

Date _____ Page _____

$$\otimes \Rightarrow \text{Temp. change} \Rightarrow H = ms \Delta \theta$$

$$\text{Phase change} \Rightarrow H = mL$$

$$S_{\text{water}} = \frac{1 \text{ cal}}{\text{gm} \cdot ^\circ\text{C}}$$

$$L_{\text{ice}} = \frac{80 \text{ cal}}{\text{gm}}$$

$$L_{\text{water}} = \frac{540 \text{ cal}}{\text{gm}}$$

* Ques > A 50Ω of water is inside Ice, of 210 voltage is applied than calculate mass of Ice melted in 1 sec.?

m gm s?

$$\text{Ans} > H = \frac{V^2 t}{R} = mL$$

$$\frac{(210)^2}{50} \times 1 \text{ Joule} = (m \cdot \text{gm}) \left(\frac{80 \text{ cal}}{\text{gm}} \right) \times 4.2$$

$$m = 2.6 \text{ gm}$$

* Ques > A 60Ω of Rod is inside 42 Kg water, of 7A current is Pass than calculate Rise in Temperature of water Per minute?

$$\text{Ans} > H = I^2 R t = m s \Delta \theta$$

$$7^2 \times 60 \times 60 \text{ Joule} = (42 \text{ kg}) \left(\frac{1000 \text{ cal}}{\text{kg} \cdot ^\circ\text{C}} \right) (\Delta \theta) 4.2$$

$$\Delta \theta = 1^\circ\text{C}$$

⊛ ⇒ For "same Heat" by Two different Heaters :-

Heater (1) Resistance = R_1 time = t_1

Heater (2) Resistance = R_2 time = t_2

∴ $V = \text{same}$ (bcz in home = 220V always)

∴ $H = \text{same}$ (given)

$$H = \frac{V^2 t}{R}$$

$$\therefore t \propto R$$

** ⇒ If both used jointly for same Heat :-

$$(i) t_{\text{series}} = t_1 + t_2$$

$$(ii) t_{\text{parallel}} = \frac{t_1 \cdot t_2}{t_1 + t_2}$$

** Ques > For boiling 1 Litre water ; Heater₁ = 3 min.
Heater₂ = 6 min.

Ans > (i) $t \propto R$

$$t_2 > t_1$$

$$R_2 > R_1$$

$$\Rightarrow R_2 = 2R_1$$

(ii) If both used jointly for same Heater :-

$$t_{\text{series}} = 3 + 6 = 9 \text{ min.}$$

$$t_{\text{parallel}} = \frac{3 \times 6}{3 + 6} = 2 \text{ min.}$$

BULB :-

→ Based on Heating Effect of current.

① Rated values (P_R & V_R)

EX:- Bulb (100W, 220V)

$$P_R = 100 \text{ W}$$

$$V_R = 220 \text{ V}$$

(i) If $V_{\text{actual}} = 220 \text{ V} \Rightarrow P_{\text{actual}} = 100 \text{ W} \Rightarrow$ Perfect glow.

(ii) If $V_{\text{actual}} < 220 \text{ V} \Rightarrow P_{\text{actual}} < 100 \text{ W} \Rightarrow$ Less glow.

(iii) If $V_{\text{actual}} > 220 \text{ V} \Rightarrow P_{\text{actual}} > 100 \text{ W} \Rightarrow$ Fused.

② Resistance of Bulb (R_B) :-

(i)

$$R_B = \frac{V_R^2}{P_R}$$

(ii)

$\because V_R = \text{same.}$

$$\therefore R_B \propto \frac{L}{P_R} \quad \text{Always}$$

EX:- ① $R_{400\text{W}} > R_{60\text{W}} > R_{100\text{W}}$

② Bulb ① (200W, 220V) $R_{B1} = ?$
 Bulb ② (500W, 220V) R_{B2}

$$\text{Soln :- } R_B \propto \frac{L}{P_B} \Rightarrow \frac{R_{B1}}{R_{B2}} = \frac{500}{200} = 5:2$$

Ques > Bulb (220V, 100W); Find $R_B = ?$

$$\text{Ans > } R_B = \frac{V_R^2}{P_R} = \frac{(220)^2}{100} = 22 \times 22 \Rightarrow 484 \Omega$$

Q3 Actual Power consumption of Bulb :-

$$P_{\text{actual}} = I_{\text{actual}}^2 R_B = \frac{V_{\text{actual}}^2}{R_B}$$

AIEEE

Ques > Bulb (220V, 100W); $V_{\text{actual}} = 110\text{V}$
 $P_{\text{actual}} = ?$

$$\text{soln > } R_B = \frac{(220)^2}{100} \Omega$$

$$P_{\text{actual}} = \frac{V_{\text{actual}}^2}{R_B} = \frac{(110)^2}{\left[\frac{(220)^2}{100} \right]} = 25\text{W} \quad (\text{Less Bright})$$

* \Rightarrow Brightness $\propto P_{\text{actual}}$

* \Rightarrow Bulb in series AND parallel :-

case: ① :- Bulb in Series :-

① BRIGHTNESS $\propto P_{\text{actual}} (= I^2 R_B) \because I = \text{const.}$

$$\propto R_B$$

$$\propto I$$

$$P_R$$


\rightarrow Bulb of Less Rated Power is more Bright, and vice versa.

$$\textcircled{2} \quad P_{\text{total}} = ?$$

$$\therefore \text{If } V_{R_1} = V_{R_2} = \dots = V_{\text{supply}}$$

$$\frac{1}{P_{\text{total}}} = \frac{1}{P_{R_1}} + \frac{1}{P_{R_2}} + \dots$$

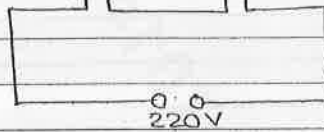*EX:- $\frac{25\text{W}}{220\text{V}}$ (1) $\frac{100\text{W}}{220\text{V}}$ (2) \textcircled{i} Brightness (1) > Brightness (2)



\textcircled{ii} $P_{\text{total}} = ?$

$$\frac{1}{P_{\text{total}}} = \frac{1}{25} + \frac{1}{100} = \frac{1}{20\text{W}}$$

\textcircled{iii} Resistance of bulbs:-

$$R_{B_1} = \frac{(220)^2}{25}$$

$$R_{B_2} = \frac{(220)^2}{100}$$

\textcircled{iv} Ratio of Resistance:-

$$R_B \propto \frac{1}{P} \Rightarrow R_{B_1} : R_{B_2} = 4 : 1$$

\textcircled{v} Voltage across each bulb:-

$$\therefore V \propto R$$

$$\therefore V_1 : V_2 = 4 : 1$$

$$V_1 = \frac{4}{5} \times 220 = 176\text{V}$$

$$V_2 = \frac{1}{5} \times 220 = 44\text{V}$$


$$(vi) P_1 = \frac{V_1^2}{R_{B1}} = \frac{(176)^2}{\left[\frac{(220)^2}{25}\right]} = 16W$$

$$P_2 = \frac{V_2^2}{R_{B2}} = \frac{(44)^2}{\left[\frac{(220)^2}{100}\right]} = 4W$$

$$P_{total} = P_1 + P_2 = (16 + 4)W = 20W$$

NEEE

Ques >

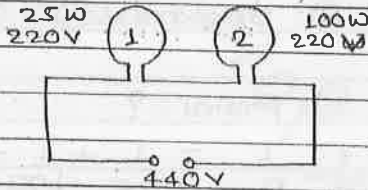

Ans >

$$V \propto R$$

$$V_1 : V_2 = 4 : 1$$

$$V_1 = \frac{4}{5} \times 440 = 352V \Rightarrow \text{Get Fused due to over voltage } (V > 220V)$$

$$V_2 = \frac{1}{5} \times 440 = 88V \Rightarrow \text{It is safe but it will not glow due to open ckt.}$$

[Bulb Fuse]

Case: - (ii) :- Bulb in Parallel :-

$$(1) \text{ * BRIGHTNESS } \propto P_{ACTUAL} \left(= \frac{V^2}{R_B} \right) \because V = \text{const.}$$

$$\propto \frac{1}{R_B}$$

$$\propto P_R$$


→ Bulb of "Less Rated" power is "Less Bright" and VICE VERSA.

② $P_{Total} = ?$

if $V_{R1} = V_{R2} = \dots = V_{Supply}$

$P_{Total} = P_{R1} + P_{R2} + \dots$

Ques >

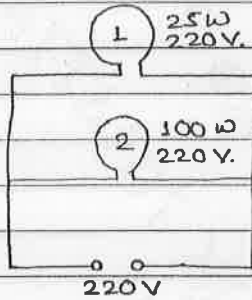


① Brightness of Bulb; ② > ①

② $P_{Total} = ?$


$P_{Total} = 100 + 25 = 125W$

Ques >

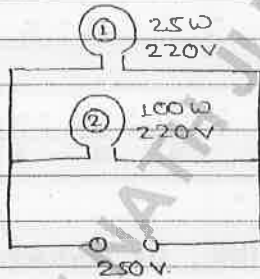

⇒ Both the Bulb get Fused due to excess voltage.

Ques >

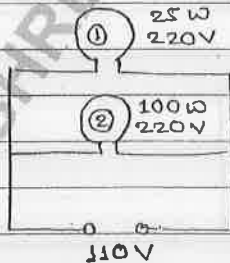

① Brightness of Bulb; ① < ②

② $P_{Total} = ?$


$P_1 = \frac{(110)^2}{\left[\frac{(220)^2}{25}\right]} = 6.25W$

$P_2 = \frac{(110)^2}{\left[\frac{(220)^2}{100}\right]} = 25W$

$P_{Total} = 25 + 6.25 = 31.25W$

Ques > 5 Identical Bulbs ;


Method :- 1

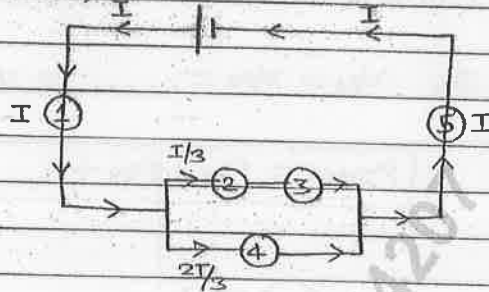

"I" ⇒ 1 = 5 > 4 > 2 = 3


"दासक" ⇒ 1 = 5 > 4 > 2 = 3

Method :- 2

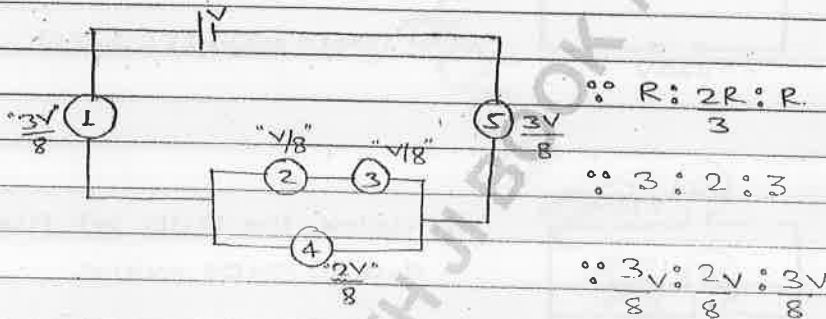

Ques > (B) & (C) are Identical bulbs, if suddenly bulb (C) get Fused than Affect of Brightness on Bulb (A) & Bulb (B) will be ?

Ans >

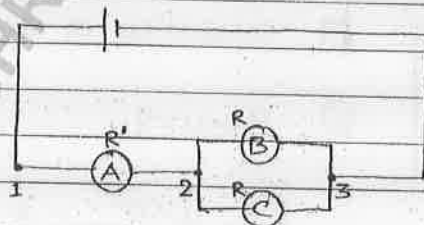

∴ of confused than Do it current method.

Date _____ Page _____


Bulb (C) OK:- $V_{12} : V_{23} = R' : R/2$

Bulb (C) FUSED:- $V_{12} : V_{23} = R' : R$

∴ $V_{23} \uparrow \Rightarrow V_B \uparrow \Rightarrow P_B \uparrow \Rightarrow$ Brightness of (B) \uparrow

∴ $V_{12} \downarrow \Rightarrow V_A \downarrow \Rightarrow P_A \downarrow \Rightarrow$ Brightness of (A) \downarrow

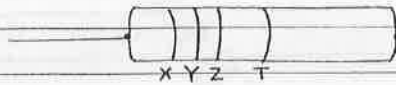☆ \Rightarrow COLOUR CODING OF CARBON RESISTANCE:-



∴ First 3 colour = (Value) ∴ Fourth colour = (Tolerance)

(Black) = B — 0

(Brown) = B — 1

R — 2

O — 3

Y — 4

(Green) = G — 5

(Blue) = B — 6

V — 7

(Gray) = G — 8

W — 9

Golden = $\pm 5\%$

Silver = $\pm 10\%$

No colour = $\pm 20\%$

$$R = xy \times 10^z \Omega \pm T$$

Ques) Red (2) orange (3) blue (6) golden ($\pm 5\%$)

Soln:- $R = 23 \times 10^6 \Omega \pm 5\%$
 $= 23 \text{ M}\Omega \pm 5\%$


Ques> Brown, Black, Blue
(1) (0) 6

soln :- $R = 10 \times 10^6 \Omega \pm 20\%$
 $= 10 \text{ M}\Omega \pm 20\%$

SHREE NATHJI BOOK 7014774207

① METER BRIDGE :-

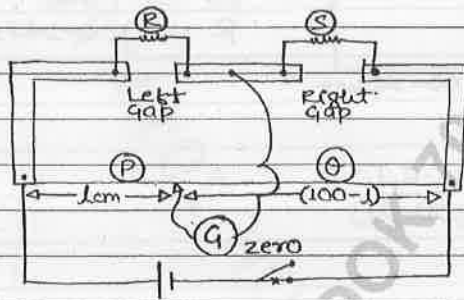- ① Based on wheat-stone Bridge.
- ② Based on zero (0) deflection method.
- ③ Unknown Resistance is measured by comparing with the known Resistance.




⇒ At "Balance" :-

$$\frac{P}{Q} = \frac{R}{S}$$

$$\frac{l}{(100-l)} = \frac{R}{S}$$

∴ $S = \left(\frac{100-l}{l} \right) R$ (Don't use Formula)


MIEEE
Ques >

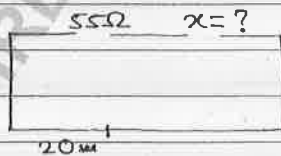


$$\frac{55}{X} = \frac{20}{80}$$

$$X = 220 \Omega$$

Ques >

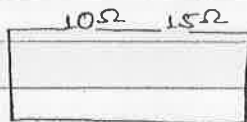


$$l_{\text{balancing}} = 40 \text{ cm}$$

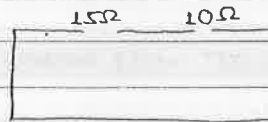


$$l_{\text{balancing}} = 60 \text{ cm}$$

increased by 20 cm.

AIPMT
2015 Ques

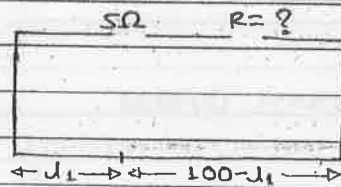
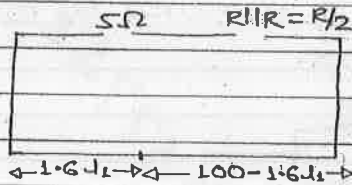
$$\frac{S}{R} = \frac{J_1}{100 - J_1} \quad \text{--- (1)}$$



$$\frac{10}{R} = \frac{1.6J_1}{100 - 1.6J_1} \quad \text{--- (2)}$$

$$\frac{(1)}{(2)} \therefore \frac{1}{2} = \frac{100 - 1.6J_1}{\frac{1.6(100 - J_1)}{0.8}}$$

$$80 - 0.8J_1 = 100 - 1.6J_1$$

$$-0.8J_1 = 100 - 80 - 1.6J_1$$

$$-0.8J_1 = 20 - 1.6J_1$$

$$0.8J_1 = 20$$

$$J_1 = \frac{20}{0.8} = 25 \text{ cm}$$

by eqn -- (1) :-

$$\frac{S}{R} = \frac{J_1}{100 - J_1}$$

$$\frac{5}{R} = \frac{25}{100 - 25}$$


$$\Rightarrow R = 15 \Omega$$

\Rightarrow Draw Back of Volt Meter :-

It does not give accurate reading, because it draw some current from the ckt.

② POTENTIOMETER :-

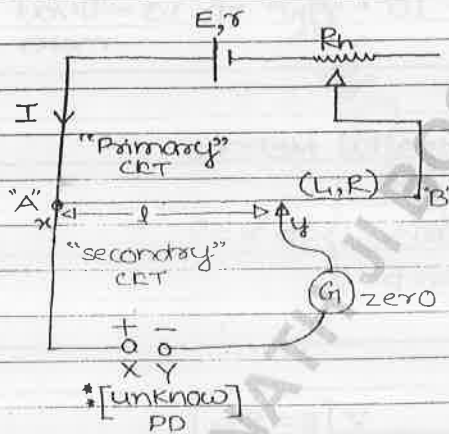- ① Used to measure Potential Difference (P.D)
- ② Based on zero (0) deflection method.
- ③ "Not" Based on wheat-stone bridge.
- ④ It Does not draw current from ckt under measurmn. so, measurement is Acquerate, so Behave as a Ideal Volt Meter.



① Primary Ckt :-

$$I = \frac{E}{R + R_h + r}$$

$$V_{AB} = I \times R \rightarrow \text{wire resistance}$$

⇒ Potential Gradient (x) :-
PD across "unit length" of wire

$$\because L = V_{AB}$$

$$\because 1 = \frac{V_{AB}}{L}$$

$$\therefore \boxed{x = \frac{V_{AB}}{L}}$$

Ques > Primary CRT of Potentiometer; Battery = 2 volt

∴ wire = 10m, 40Ω

Find $x = ?$

∴ Extra Resistance = 780Ω

$$\text{Ans} > I = \frac{2 \text{ volt}}{780 + 40} = \frac{1}{400} \text{ A}$$

$$V_{AB} = I \times R = \frac{1}{400} \times 40 = 0.1 \text{ volt}$$

$$x \approx \frac{V_{AB}}{L} = \frac{0.1}{10\text{m}} \Rightarrow 10^{-2} \text{ V/m} \Rightarrow 10 \text{ millivolt meter}$$

Ques > In Primary CRT of Potential meter:-

$$S = 1 \times 10^{-6}$$

$$A = 1 \text{ cm}^2$$

$$I = 1 \text{ Amp}$$

∴ $x = ?$

$$\text{Ans} > x = \frac{V_{AB}}{L} = \frac{I \times R}{L}$$

$$= \frac{I}{L} \left(\frac{S \cdot L}{A} \right)$$

$$\because \left[R = \frac{S \cdot L}{A} \right]$$

$$= \frac{I \cdot S}{A}$$

$$= \frac{1 \times 10^{-6}}{1 \times 10^{-4}} = 10^{-2} \text{ V/m}$$

$$= 10 \text{ millivolt meter}$$

Ques) Primary CKT of potentiometer :- cell = 2 volt.
wire. (4m, 8Ω)

Find :- $R_h = ?$ $\chi = \frac{1\text{mV}}{\text{cm}}$

Ans) $I = \frac{2}{8 + R_h}$

$$V_{AB} = I \times R \Rightarrow \left(\frac{2}{8 + R_h} \right) \times 8$$

$$\chi = \frac{V_{AB}}{L} \Rightarrow \frac{\left[\frac{16}{8 + R_h} \right]}{4\text{m}}$$

$$\frac{1 \times 10^{-3}}{1 \times 10^{-2}} = \frac{4}{8 + R_h}$$

$$40 = 8 + R_h$$

$$R_h = 32 \Omega$$

(2) secondary CKT :-

Unknown P.D is connected in secondary CKT as show in Figure. And Balancing Length is obtained by Jockey on potentiometer wire.

∴ If Balancing Length = l

∴ Unknown P.D (V) =

$$V = \chi l$$

③ Range :-

$$\text{EX:- } \left. \begin{array}{l} V_{AB} = 10 \text{ volt} \\ L = 10 \text{ m.} \end{array} \right\} \kappa = \frac{1 \text{ V}}{\text{m}}$$

Unknown Balancing Length (l) measured = ($\kappa \cdot l$)

2V $l = 2 \text{ m.}$ $1 \times 2 = 2 \text{ volt.}$

5.5V $l = 5.5 \text{ m.}$ $1 \times 5.5 = 5.5 \text{ volt.}$

10V $l = 10 \text{ m.}$ $1 \times 10 = 10 \text{ volt.}$

10.1V $l = \text{not exist.}$ X

$\therefore \text{ Range} = V_{AB}$

$\text{Range} = \kappa \cdot L$

$\boxed{\text{Range} \propto \kappa}$

④ sensitivity (S) :-

It is Ability to measure "small value" :- $\boxed{S \propto \frac{1}{\kappa}}$

** \Rightarrow Rh (Rheostat) is used in Primary ckt to adjust κ .

so that; (i) $\kappa \uparrow = \text{Range} \uparrow$.


sensitivity \downarrow .

$\kappa \downarrow = \text{Range} \downarrow$.

sensitivity \uparrow .


⑤ Standardisation of Potentiometer :-

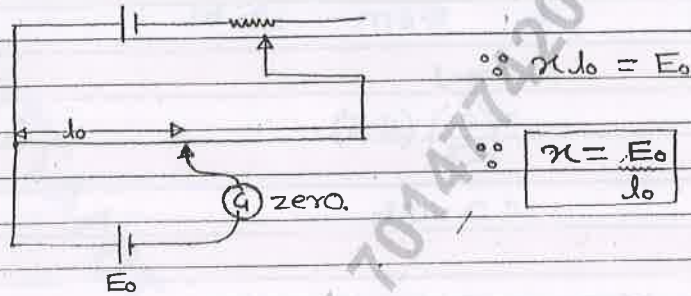It is process to find "Accurate" κ by Balancing a "standard cell" on Potentiometer wire.



☆ \Rightarrow APPLICATION OF POTENTIOMETER :-

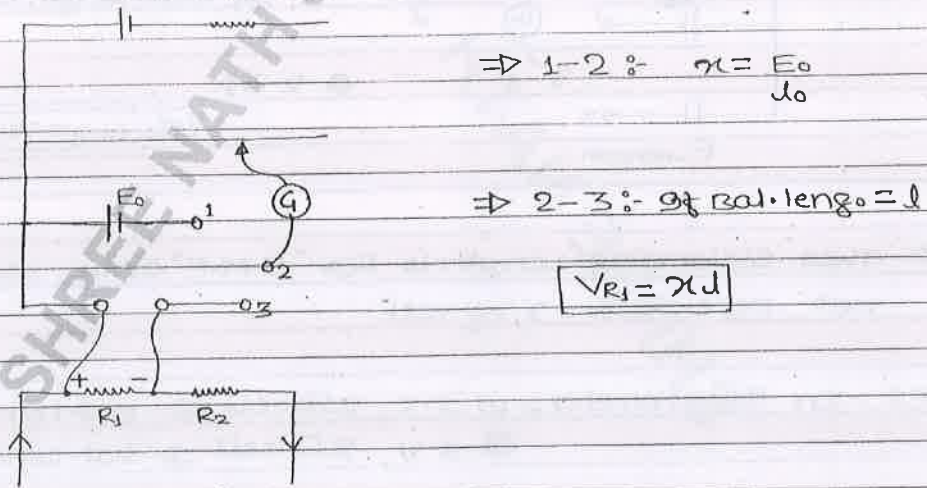① To measure P.D across current carrying resistance :-



Ques > A standard cell of 1.2 volt is balanced at 2.6 m.
An unknown P.D is balanced at 6.5 m, then find its value?


Aus > $\kappa = \frac{E_0}{l_0} = \frac{1.2V}{2.6m} = \frac{6V}{13m}$

$$V = \kappa \cdot l$$

$$= \left(\frac{6}{13}\right) (6.5)$$

$$= 3 \text{ volt}$$

② To measure E.M.F of cell:-

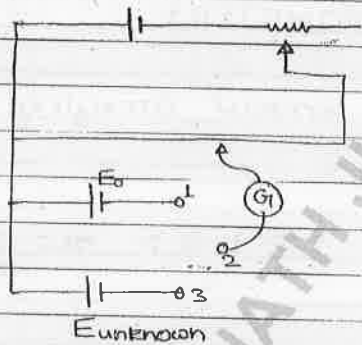

⊗ 1-2 :- $\kappa = \frac{E_0}{l_0}$

if Bal. Length = l

⊗ 2-3 :-

$$E_{\text{unknown}} = \kappa l$$


** → This balancing length is for "E.M.F" only, so does not depend on r of cell.

EX:- In Potentiometer:- (1) 5 V, 2Ω cell → Bal. Len. = 3.2 m

(2) 5 V, 3Ω cell → Bal. Len. = ?

soln:- (2) balancing length = 3.2 (does not depend on " r " of cell.)

③ To compare E.M.F of two cell:-

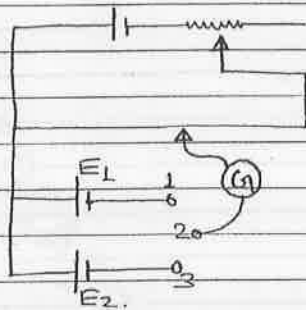


⊗ 1-2 :- $E_1 = \chi J_1$ ----- ①

⊗ 2-3 :- $E_2 = \chi J_2$ ----- ②

E_1	J_1
E_2	J_2

→ Here; standardisation do not Required.

Ques)

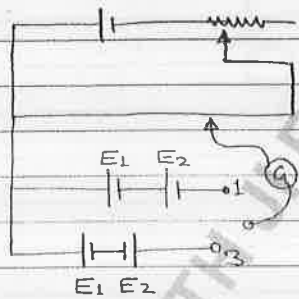

⊗ 1-2 :- $E_1 + E_2 = \chi J_1$

⊗ 2-3 :- $(E_1) - E_2 = \chi J_2$
↳ "Always $> E_2$ "

①	$E_1 + E_2 = J_1$
2	$E_1 - E_2 = J_2$

EXTRA ⊗ ⇒ components & dividendo :-


E_1	$J_1 + J_2$	⇒ Not we use formula.
E_2	$J_1 - J_2$	

Ques) series group of two cell is balanced at 6m, one cell is Reversed then it is balanced at 2m length; than Find $E_1 = ?$
 E_2

Aus \rightarrow $E_1 + E_2 = \kappa(l) \dots \textcircled{1}$
 $E_1 - E_2 = \kappa(l') \dots \textcircled{2}$

$$\frac{E_1}{E_2} = 2:1$$


Ques \rightarrow In Potentiometer:-

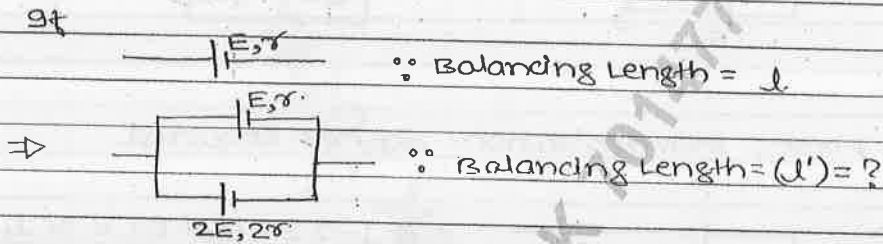

soln \therefore $E = \kappa l \dots \textcircled{1}$
 $\frac{4E}{3} = \kappa l' \dots \textcircled{2}$

$\textcircled{1} \Rightarrow l' = 4l$
 $\textcircled{2} \quad \quad \quad 3 \downarrow$

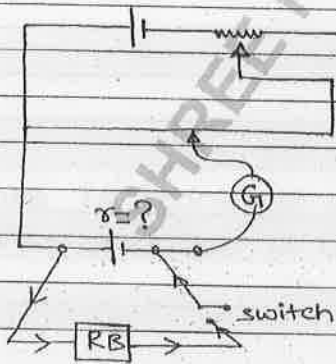$\textcircled{4}$ To Measure Internal Resistance (r) of cell :-



\textcircled{i} switch OFF:- $E = \kappa(l_1)$
OFF

\textcircled{ii} switch ON:- $V = \kappa(l_2)$
ON

$\therefore r = \left(\frac{E-V}{V} \right) R$

$r = \left(\frac{l_1 - l_2}{l_2} \right) (R, B) \rightarrow$ use as formula.

\rightarrow Here; standardisation is not required.

Qus-44; pg=211.

AIPT 2014
 Ques) $l_1 = 52 \text{ cm}$ of $R = 4 \Omega$ then; $r = ?$
 $l_2 = 40 \text{ cm}.$


Soln:- $r = \left(\frac{l_1 - l_2}{l_2} \right) R \Rightarrow \left(\frac{52 - 40}{40} \right) \times 4 \Rightarrow 1.2 \Omega$

AIPT 2014
 Ques) $l_1 = 3 \text{ m}.$ of $R = 9.5 \Omega$ then; $r = ?$
 $l_2 = 2.85 \text{ m}.$

Soln:- $r = \frac{0.15^3 \times 9.5}{2.85 \times 10^2} = 0.5 \Omega$

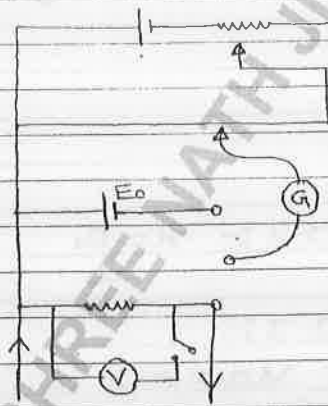5) calibration of \odot :-

\Rightarrow It is used to find Error in voltmeter.



* 1-2 :- $\alpha = \frac{E_0}{I_0}$

* 2-3 :- $V = \alpha I$

Let \odot reading = V'

(i) Error :- $= V' - V$

(ii) Relative error :- $= \frac{V' - V}{V}$

"Error" = असतु व भ्रम (always.)

(iii) % Error :- $= \frac{V' - V}{V} \times 100$

Ques) A standard cell of 1.1 volt is balanced at 44m, an unknown P.D is balanced at 1.9m, and voltmeter reading is 0.5V. Then calculate % Error in voltmeter?


$$\text{Ans) } \kappa = \frac{E_0}{l_0} = \frac{1.1 \text{ V}}{44 \text{ m}} = \frac{1 \text{ V}}{4 \text{ m}}$$

$$V = \kappa \cdot l \Rightarrow \frac{1}{4} \times 1.9 = 0.475 \text{ volt.}$$

$$\text{Reading} = 0.5 \text{ volt.}$$

$$\begin{aligned} \% \text{ Error} &= \frac{0.5 - 0.475}{0.475} \times 100 \\ &= \frac{0.5 - 0.475}{0.475} \times 100 \Rightarrow +5.2\% \end{aligned}$$

6) calibration of (A) :-

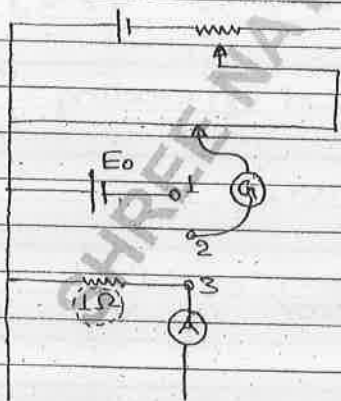

$$\text{1-2 :- } \kappa = \frac{E_0}{l_0}$$

$$\text{2-3 :-}$$

$$V_{IR} = \kappa \cdot l$$

$$(IR)_{IR} = \kappa \cdot l$$

$$I(l) = \kappa \cdot l$$

$$I = \kappa \cdot l$$


∴ Let (A) reading = I'

$$\% \text{ error} = \frac{I' - I}{I} \times 100$$

③ MOVING COIL GALVANOMETER (M.C.G.) :-

* (i) Based on magnetic Effect of current.

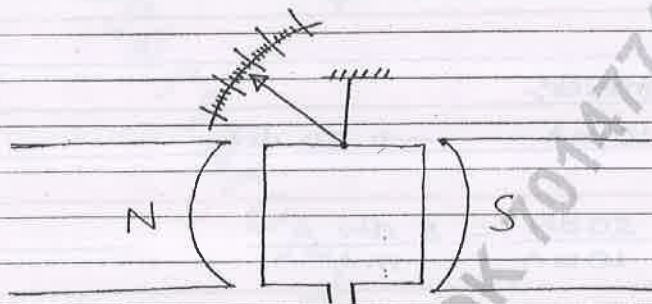(ii) Used to measure *small current and used to Detect current in the circuit.



at ϕ

$$\tau_{\text{deflecting}} = \tau_{\text{restoring}}$$

$$NIAB \sin 90^\circ = K\phi$$

$$\phi = \left(\frac{NAB}{K} \right) I \Rightarrow \phi \propto I$$

Here;

K :- (Torsional constant) \Rightarrow Restoring Torque for ^{UNIT} deflection
rad. ~~current~~

⊗ \Rightarrow CURRENT SENSITIVITY :- (CS) :-

$$\because I \text{ --- } \phi$$

$$I \text{ --- } \frac{\phi}{I}$$

$$CS = \frac{\phi}{I} = \frac{NAB}{K}$$

⊗ ⇒ VOLTAGE SENSITIVITY (V_s) :-

$$V_s = \frac{\phi}{I}$$

⊗ ⇒ Figure of Merit :- $\frac{1}{CS} = \frac{I}{\phi}$

EX: In galvanometer:-

10 mA → 50 div.

(i) $CS = \frac{\phi}{I} = \frac{50 \text{ div}}{10 \text{ mA}} = 5 \frac{\text{div}}{\text{mA}}$

(ii) Figure of Merit = $\frac{I}{\phi} = \frac{10 \text{ mA}}{50 \text{ div}} = \frac{1 \text{ mA}}{5 \text{ div}}$

⊗ SYMBOL :-



I_g ⇒ Full deflection current.

V_g ⇒ Full deflection voltage.

R_g ⇒ Resistance of galvanometer.

⇒ ∴ $V_g = I_g \cdot R_g$

* ⇒ It behaves like Ammeter of " I_g " Range And;
Voltmeter of " V_g " Range

Ques) MOVING COIL (M) has 100 Divⁿ and $C_s = 5 \text{ div}$
 and $V_s = 10 \text{ div}$, than Find R_g ?
 mA


Ans) $C_s = 5 \text{ div} \Rightarrow I_g = 20 \text{ mA}$
 mA

$V_s = 10 \text{ div} \Rightarrow V_g = 10 \text{ mA}$
 mA

$\therefore R_g = \frac{V_g}{I_g} = \frac{10 \text{ mA}}{20 \text{ mA}} = 0.5 \Omega$

④ SHUNTING:-

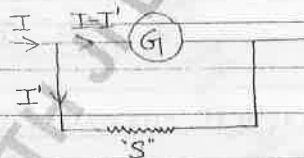"shunting" is apply "small" Resistance in "Parallel"
 to galvanometer



Due to shunting some part of current is diverted through shunt; so deflection & sensitivity (C_s) both decreases.

$$S = \frac{\phi_2 R_g}{\phi_1 - \phi_2} \quad \therefore \phi_1 = \text{Deflect}^n \text{ before shunt}$$

$$\phi_1 - \phi_2 \quad \therefore \phi_2 = \text{Deflect}^n \text{ after shunting}$$

Ques) $R_g = 50 \Omega$, calculate shunt for changing Deflectⁿ
 80 div. to 20 divⁿ?


Ans) $S = \frac{\phi_2 R_g}{\phi_1 - \phi_2} \Rightarrow \frac{20 \times 50}{80 - 20} = 100 \Rightarrow \frac{50}{3} \Omega$

(S) AMMETER:-

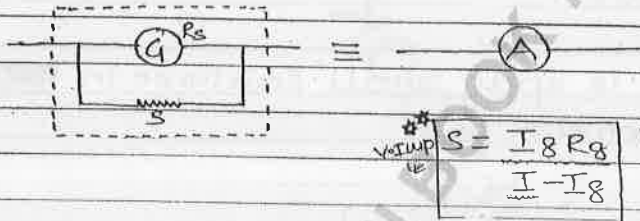- (i) used to measure current.
- (ii) "Always" connected in series.
- (iii) It's resistance is small.
- (iv) Resistance of Ideal Ammeter is zero (0).

⇒ (G) CONVERSION → (A) "or" (A) UPGRADING → (A) "or" (V) CONVERSION → (A) :-

→ "small" shunt is connected across galvanometer



Ques > $R_g = 13\Omega$, Full deflection current (I_g) = 100 Amp,
calculate Required shunt for making Ammeter of 750A.

Ans >
$$S = \frac{13 \times 100}{750 - 100} = \frac{1300}{650} = 2\Omega$$

AIEEE

Ques > Range of Ammeter is 1A, and its Resistance is 90Ω ,
calculate shunt for making it range 10A?

soln >
$$S = \frac{1 \times 90}{10 - 1} = 10\Omega$$

* If $S \downarrow \Rightarrow$ Range of (A) \uparrow [From formula]

* $R_A = S \parallel R_g \Rightarrow \boxed{R_A = \frac{S \cdot R_g}{S + R_g}} < R_g$
(smaller than smallest)


⑥ VOLTMETER :-

(i) Always connected in series parallel. to a ckt.

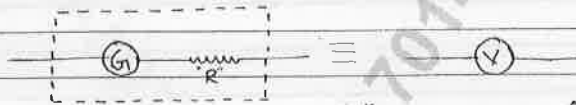(ii) Its resistance is High (Ideally $= \infty$).

* \Rightarrow $G \xrightarrow{\text{CONVERSION}} \text{V}$ "or" $\text{V} \xrightarrow{\text{UPGRADATION}} \text{V}$ "or" $\text{A} \xrightarrow{\text{CONVERSION}} \text{V} \therefore$

"Series" Resistance is connected in series of Galvanometer.



Here:

* V = Require Range
of voltmeter.

$$R = \frac{V}{I_g} - R_g \quad \begin{array}{l} \text{*} \\ \text{*} \end{array} \quad \begin{array}{l} \text{V Imp} \\ \text{for Exam.} \end{array}$$

Ques $\rightarrow R_g = 10 \Omega$, Find diff. leastⁿ current (I_g) = $1 \mu\text{A}$, then calculate series resistance for making voltmeter of 1V Range?

soln :- $R = \frac{1}{1 \times 10^{-3}} - 10 = 990 \Omega$.

* $R_{\text{series}} \uparrow = \text{Range of } \text{V} \uparrow$

* $R_{\text{V}} = R_g + R$

\therefore * $R_{\text{V}} > R_{\text{A}} > R_{\text{G}}$

Date _____ Page _____


SHREE NATH JI BOOK 7014774207

★ ⇒ DI-electric strength of Medium :-

→ It is Maximum Electric Field after which insulation of DI-electric medium gets punched.

For; Air (dielectric const.) = 3×10^6

Ques > Is it possible to hold 1C charge on metal sphere of 1cm Radius ?

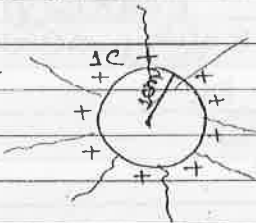Ans >  $E_{\text{surface}} = \frac{kQ}{r^2} = \frac{9 \times 10^9 \times 1}{(1 \times 10^{-2})^2} = 9 \times 10^{13}$

→ Breakdown of surrounding air takes place due to this high Electric Field, so charge leakage takes place.

★ ⇒ CAPACITANCE OF CONDUCTOR :- (C) :-

(i) It represents charge holding capacity of conductor.

(ii) In conductor; $Q \propto V$
 $Q \propto V$


⇒ scalar Quantity.

$Q = CV$
$e = \frac{Q}{V}$

Unit - $\begin{cases} \text{SI MKS :- } \frac{\text{Coulomb}}{\text{Volt}} \text{ (F)} \\ \text{DEGS :- st. F} \end{cases}$

$1F = 9 \times 10^{11} \text{ st. F}$

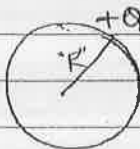(i) capacitance of spherical conductor :-



If +Q is given:-

$V = \frac{kQ}{R} \Rightarrow \therefore V = \frac{Q}{4\pi\epsilon_0 R}$

$Q = 4\pi\epsilon_0 R V \Rightarrow \boxed{C_{\text{sphere}} = 4\pi\epsilon_0 \epsilon_r R} \quad \boxed{C_{\text{sph.}} \propto R}$

$\therefore C_{\text{big}} = n^{1/3} C_{\text{small}}$

"C" does not depends on:
(i) $\frac{Q}{V}$

"C" depends on:-
(i) size
(ii) surrounding medm. (ϵ_r)


② Capacitance of Earth:-

(i) Theoretically:- By considering a earth, a conducting sphere


of $R = 6400 \text{ km}$. $\therefore C_{\text{earth}} = 4\pi\epsilon_0 (6400 \text{ km}) \Rightarrow C_{\text{earth}} = 711.4 \text{ F}$

(ii) Practically:- Earth can accept unlimited charge; $C_{\text{earth}} = \infty$

EX: (i)

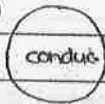

(ii)

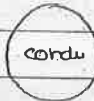

(iii)




Capacitance = C

capacitance = ∞ ($V=0$) $C = 4\pi\epsilon_0 R$

Note:- capacitance of any earthed conductor is always ∞ (infinite).


* Ques >

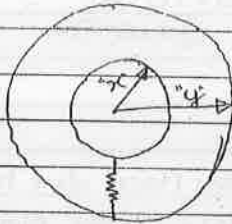

$$C = 4\pi\epsilon_0 R$$

\therefore All charge will come on outer surface (\because conductor)

* Ques >

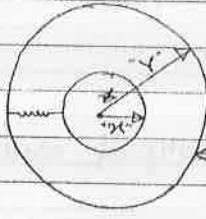

$$C = \infty$$

\therefore Earthed

★ \Rightarrow POTENTIAL ENERGY OF CHARGED CONDUCTOR (U):-

It is External work done during charging of conductor which is "stored" in the form of Potential Energy.

$$** U = \frac{1}{2} CV^2 = \frac{1}{2} QV = \frac{Q^2}{2C}$$

⊗ Energy spent by Battery :-

$$\because E = M \cdot F = V$$

$$\text{Unit charge} \text{ --- } \text{work} = V$$

$$Q \text{ charge} \text{ --- } \text{work} = QV$$

⊗ $W_{\text{battery}} = \Delta U + \text{Heat}$

$$QV = \left(\frac{1}{2} QV - 0 \right) + \text{Heat}$$

$$\boxed{\text{Heat} = \frac{1}{2} QV} \rightarrow \text{only while charging of conduct}$$

Ques) For a conductor :-

$$Q \text{ charge} = Q \Rightarrow P \cdot E = U$$

$$Q \text{ charge} = \frac{Q}{2} \Rightarrow P \cdot E = ?$$

Soln :- $\because C = \text{constant}$

$$U = \frac{Q^2}{2C} \propto Q^2$$

$$U' = U/4$$

APMT

Ques) For charging a conductor, from "5V" to "10V", work done is "W", then calculate work done to increasing its potential "5V" further?

$$\text{soln :- } 5V \rightarrow 10V ; W = W$$

$$10V \rightarrow 15V ; W' = ?$$

$$5V :- U_5 = \frac{1}{2} C (5)^2 \quad 15V :- U_{15} = \frac{1}{2} C (15)^2$$

$$10V :- U_{10} = \frac{1}{2} C (10)^2$$

$$\because W_{\text{ext}} = \Delta U$$

$$W = U_{10} - U_5$$

$$W = \frac{1}{2} C (10)^2 - \frac{1}{2} C (5)^2$$

$$\textcircled{1} W = \frac{75 C}{2} \dots \textcircled{1}$$

$$W' = U_5 - U_{10}$$


$$= \frac{1}{2} C (5)^2 - \frac{1}{2} C (10)^2$$

$$\textcircled{2} W' = \frac{12.5 C}{2} \dots \textcircled{2}$$


$$\frac{\textcircled{1}}{\textcircled{2}} \therefore W' = \frac{5}{3} W$$

★ \Rightarrow RE-DISTRIBUTION OF CHARGES:-

\rightarrow

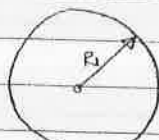

Q_1, C_1, V_1

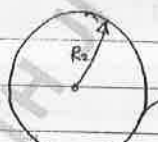


Q_2, C_2, V_2

Q_1', C_1, V_1'



Q_2', C_2, V_2'

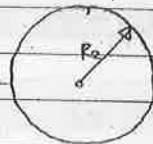

$$\textcircled{1} C_{\text{SYSTEM}} = C_1 + C_2$$

$$\textcircled{2} \text{ Charge distribut}^n \Rightarrow Q = CV \quad \because V = \text{same after connect}^n$$

$$\because Q \propto C \propto R^2$$

③ common potential :-

$$Q_1 + Q_2 = Q_1' + Q_2'$$

$$C_1 V_1 + C_2 V_2 = C_1 V_c + C_2 V_c$$

$$V_{\text{common}} = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$

$$V_{\text{common}} = \frac{Q_1 + Q_2}{C_1 + C_2}$$

$$V_{\text{common}} = \frac{Q_{\text{SYSTEM}}}{C_{\text{SYSTEM}}}$$

④ Energy loss (ΔU):

$$U_{\text{before}} = \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2$$

$$U_{\text{after}} = \frac{1}{2} C_1 V^2 + \frac{1}{2} C_2 V^2$$

$$\therefore U_{\text{before}} > U_{\text{after}}$$

→ ** some Energy is lost in the form of "Heat", so

$$\therefore U_{\text{before}} > U_{\text{after}}$$


$$\Delta U = U_{\text{before}} - U_{\text{after}}$$

$$\Delta U = \frac{C_1 C_2 (V_1 - V_2)^2}{2(C_1 + C_2)}$$

Ques > Two conductor of each capacitance "C", one is charged upto 'V' and another is Neutral. If both are connected; find charge loss?

$$\text{soln: } \Delta U = \frac{exc}{2(C+0)} (V-0)^2 \Rightarrow \frac{1 \text{ eV}^2}{4}$$

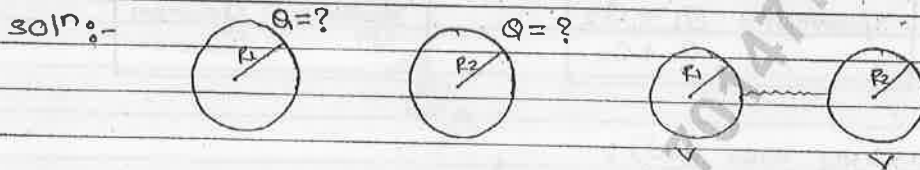**
Ques > Two metal sphere of radius R_1 & R_2 have same charges, and if these are connected with each other than common potential become "V", Find initial charge of each sphere?



Ist Method :- $V_{\text{common}} = \frac{Q_1 + Q_2}{C_1 + C_2}$

$$V = \frac{Q + Q}{4\pi\epsilon_0 R_1 + 4\pi\epsilon_0 R_2}$$

$$V = \frac{2Q}{4\pi\epsilon_0 (R_1 + R_2)}$$

$$V = \frac{2KQ}{R_1 + R_2}$$

$$Q = \frac{V (R_1 + R_2)}{2K}$$

IInd Method :- $Q_{\text{total}} = Q + Q = 2Q$

$$Q_1' : Q_2' = R_1 : R_2$$

$$Q_1' = \frac{R_1}{R_1 + R_2} \cdot 2Q$$


$$V_1' = \frac{KQ_1}{R_1} = \frac{K \left(\frac{R_1 + 20}{R_1 + R_2} \right)}{R_1} = V$$

$$\therefore Q = \frac{V(R_1 + R_2)}{2K}$$

⇒ CAPACITOR:-

★ ⇒ CONCEPT OF CAPACITOR:-

Case: I ⇒

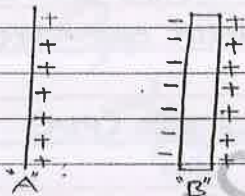

Potential of Plate A :-


$$\therefore V_A' = V_A - V_B^- + V_B^+$$

$$\therefore |V_B^-| > |V_B^+| \quad \because \text{Bez distance of } \ominus \text{ve is less than distance of } \oplus \text{ve.}$$

$$\therefore V_A' < V_A$$

$$\therefore C = \frac{Q}{V} \xrightarrow{\text{(same)}} \Rightarrow C \uparrow$$

Case: II ⇒

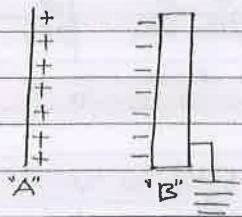

$$V_A'' = V_A - V_B^-$$

$$\therefore V_A'' < V_A$$

$$\therefore C = \frac{Q}{V} \xrightarrow{\text{(const)}} \Rightarrow C \uparrow \uparrow$$


$$\Rightarrow C \uparrow \uparrow$$

⇒ whether "Neutral" or "oppositely" charge conductor is place at already charged conductor, then; its charge remains constant and Potential increases significantly (असत)

⇒ CAPACITOR :-

⇒ It is combination of two or more electrically separated "conductor" having "same" magnitude and "opposite nature" charges at Facing layer and Potential of conductor are Different.


① PARALLEL PLATE CAPACITOR (PPC) :-

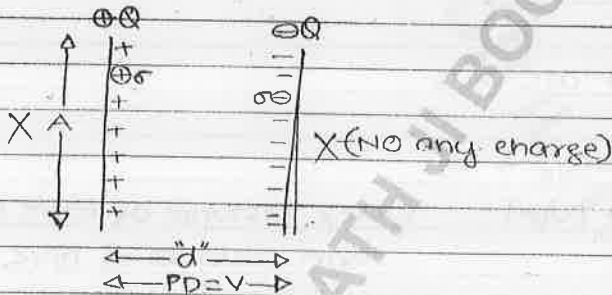

① Electric Field (E) :-

$$E_{\text{outside}} = 0$$
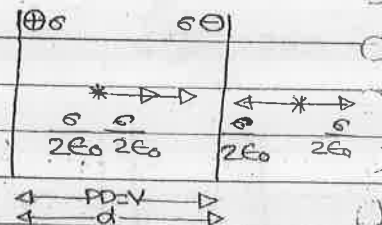
$$E_{\text{inside}} = \frac{\sigma}{\epsilon_0 \epsilon_r} = \frac{V}{d}$$



$$\therefore E = \left| \frac{dv}{ds} \right| = \frac{V}{d}$$

② Potential Energy (U) :-

$$U = \frac{1}{2} CV^2 = \frac{1}{2} QV = \frac{Q^2}{2C}$$

** → This Energy is stored in the form of "Electric Field" b/w the plates.

③ Energy Density (u) or Electrostatic Pressure :-

→ Energy stored in unit volume.

$$* u = \frac{\text{Energy}}{\text{Volume}} = \frac{1}{2} CV^2 / A.d.$$

$$* u = \frac{1}{2} \epsilon_0 E^2 = \frac{\sigma^2}{2\epsilon_0} \quad \because E = \frac{\sigma}{\epsilon_0}$$

AIPMT Ques > Dimension of $\frac{1}{2} \epsilon_0 E^2 = ?$

$$\text{soln :-} \quad \frac{\text{Energy}}{\text{Volume}} = \frac{ML^2T^{-2}}{L^3} \Rightarrow M^1L^{-1}T^{-2}$$

AIPMT Ques > Total stored Energy :-

$$\text{soln :-} \quad = u \times \text{volume} \\ = \left(\frac{1}{2} \epsilon_0 E^2 \right) A.d$$



Force b/w plates :-

$$\therefore u = \frac{\text{Energy}}{\text{Volume}} = \frac{\text{Force} \times \text{Distance}}{\text{Area} \times \text{Distance}}$$

$$= \text{Electrostatic Pressure.}$$

\therefore Force on each plate :-

$$= u \times \text{Area.} \checkmark$$

$$= \left(\frac{\sigma^2}{2\epsilon_0} \right) \times \text{Area} \checkmark$$

AI PMT

2015 Ques >


Force = $u \times \text{Area.}$

$$= \left(\frac{\frac{1}{2} CV^2}{Ad} \right) \times \text{Area}$$

$$= \frac{CV^2}{2d}$$

(5) capacitance (C)

(i)

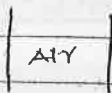

$$C_{\text{air}} = \frac{\epsilon_0 A}{d}$$

(ii)



$$C_{\text{med}} = \frac{\epsilon_0 \epsilon_r A}{d}$$

$$C_{\text{med}} = \epsilon_r C_{\text{air}}$$


$$\therefore \epsilon_r > 1 \text{ (always)}$$

$$C_{\text{med}} > C_{\text{air}}$$


$$(iii) \text{ } \epsilon_0 C_{air} = C_{med}$$

$$\frac{\epsilon_0 A}{d_{air}} = \frac{\epsilon_0 \epsilon_r A}{d_{med}}$$

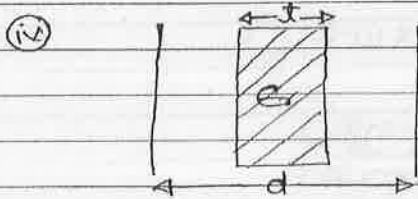
$$\therefore \boxed{d_{air} = \frac{d_{med}}{\epsilon_r}}$$



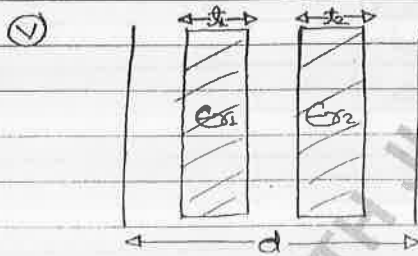
$$C = \frac{\epsilon_0 A}{(d-t) + \frac{t}{\epsilon_r}}$$


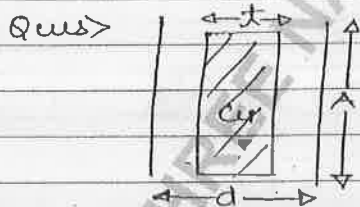
$$C = \frac{\epsilon_0 A}{(d-t_1-t_2) + \left(\frac{t_1}{\epsilon_{r1}} + \frac{t_2}{\epsilon_{r2}}\right)}$$


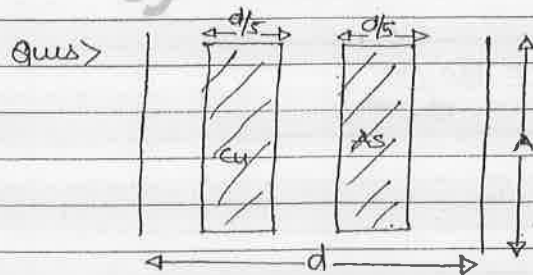
$$C = \frac{\epsilon_0 A}{(d-t) + \frac{t}{\infty}} = \frac{\epsilon_0 A}{(d-t)}$$



$$C = \frac{\epsilon_0 A}{\left(d - \frac{d}{s} - \frac{d}{s}\right) + \left(\frac{d/s}{\infty} + \frac{d/s}{\infty}\right)}$$

*Ques> capacitance of ppc (diameter of plate = 3cm)
is equal to capacitance of metal sphere (dia = 200 cm)
Find separation b/w plates?

soln :- $C_{ppc} = C_{sphere}$

$$\frac{\epsilon_0 (\pi r^2)}{d} = \epsilon_0 4\pi R$$

$$d = \frac{r^2}{4R} = \frac{3^2 \times 10^{-4}}{4 \times 200 \times 10^{-2}}$$


$$= 0.15$$

$$= (3 \times 10^{-2})^2$$

$$4 \times 100 \times 10^{-2}$$

$$= 2.25 \times 10^{-4}$$

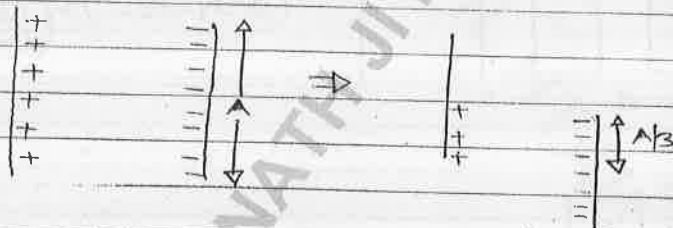*Ques> $A \Rightarrow$ common area of plates.




$$capa. = C = \frac{\epsilon_0 (A)}{d}$$

$$capa. = C' = \frac{\epsilon_0 (A/3)}{d}$$

$$= C/3$$

Ques>

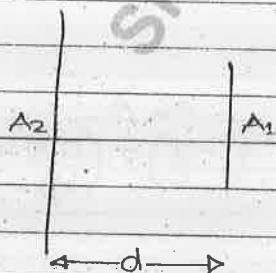

$$C' = \frac{\epsilon_0 A_1}{d}$$

Ques >		Given:- $C = \frac{\epsilon_0 A}{d}$
	Attr.	
	PPC	

NEEE
 (i) If a "thin" metal foil is placed inside ppc as shown




$$C' = \frac{\epsilon_0 A}{(d-0) + \frac{0}{\infty}}$$

$$C' = \frac{\epsilon_0 A}{d} = C$$

$$C' = C \checkmark$$

$C' \Rightarrow$ "slightly more" than C ✓

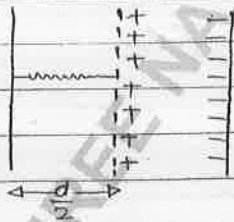
(ii) If foil is placed at mid and connected with one plate :-



$$d' = d/2$$

$$C' = 2C \checkmark$$

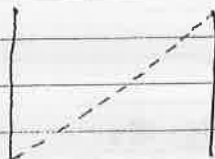*(iii) If foil touches both the plates :-




$\because P.D (V) = 0 \because$ [conductors are equipotential surface]

$$\because C = \frac{Q}{V} = \frac{Q}{0} = \infty$$


Ques > Two metal plates placed parallel, one given charges +5 and -5 C. If P.D = V, then capacitance = ?

Soln :-

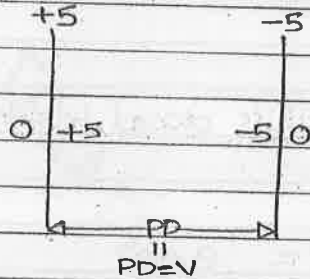

$$C = \frac{Q}{V} = \frac{5}{5} = 1$$

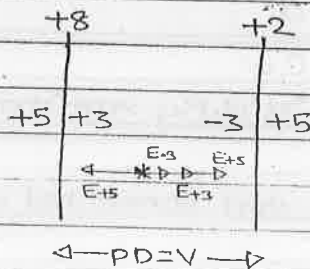
Ques > 2 Metal plates; charges +8 C and +2 C. If P.D = V, then capacitance = ?



$$C = \frac{Q}{V} = \frac{3}{5} = 0.6$$

III #
Ques >
W

Two Metal Plates; charge = Q_1 & Q_2


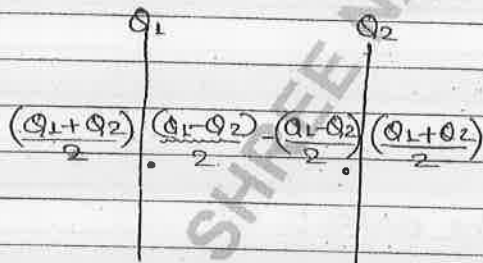


If Cap. = 'C' \Rightarrow P.D = ?

Soln :- $Q = CV$

$$P.D(V) = \frac{Q}{C} = \frac{\left(\frac{Q_1 - Q_2}{2}\right)}{C} = \frac{Q_1 - Q_2}{2C}$$

VARIATION IN CHARGED PPC :-

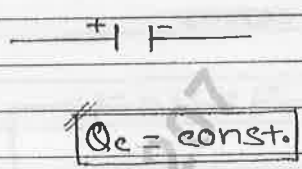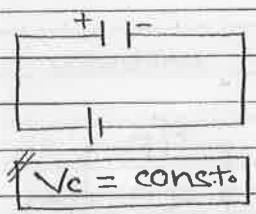

(i) case: (I) :- IF Battery is connected [Vc = const.]

VARIATN	$C = \frac{\epsilon_0 \epsilon_r A}{d}$	$V_c = \text{const.}$	$Q = \frac{CV}{Q \times C}$	$E = \frac{V}{d}$	$U = \frac{1}{2} CV^2$	$U \propto C$
(i) $\epsilon_r \uparrow$	\uparrow	$\leftarrow \text{cons.} \rightarrow$	\uparrow	$\leftarrow \rightarrow$	\uparrow	\uparrow
(ii) $A \uparrow$	\uparrow	$\leftarrow \rightarrow$	\uparrow	$\leftarrow \rightarrow$	\uparrow	\uparrow
(iii) $d \uparrow$	\downarrow	$\leftarrow \rightarrow$	\downarrow	\downarrow	\downarrow	\downarrow


(ii) case: II :- If Battery is disconnected [Qc = const.]

VARIATN	$C = \frac{\epsilon_0 \epsilon_r A}{d}$	$Q_c = \text{const.}$	$V = \frac{Q}{C} \propto \frac{1}{C}$	$E = \frac{Q}{A \epsilon_0 \epsilon_r}$	$U = \frac{Q^2}{2C}$	$U \propto \frac{1}{C}$
(i) $\epsilon_r \uparrow$	\uparrow	$\leftarrow \text{cons.} \rightarrow$	\downarrow	\downarrow	\downarrow	\downarrow
(ii) $A \uparrow$	\uparrow	$\leftarrow \rightarrow$	\downarrow	\downarrow	\downarrow	\downarrow
(iii) $d \uparrow$	\downarrow	$\leftarrow \rightarrow$	\uparrow	$\leftarrow \rightarrow$	\uparrow	\uparrow


**** Note :- If Nothing is given than consider battery is disconnected.**

★ ⇒ GROUPING OF CAPACITOR :-

SERIES

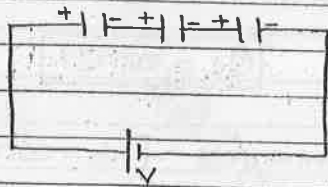

PARALLEL

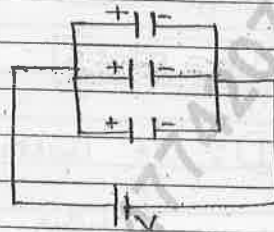

(i) ∴ $Q = \text{same}$

(i) ∴ $V = \text{same}$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

(ii) $C_{eq} = C_1 + C_2 + C_3$

(ii) $C_{eq} = \frac{C_1 \cdot C_2}{C_1 + C_2}$

charge density:-

$$Q = CV$$


(iii) ∴ $Q \propto C$

voltage density:-

$$Q = CV$$

(iii) ∴ $V \propto \frac{1}{C}$

Ques >

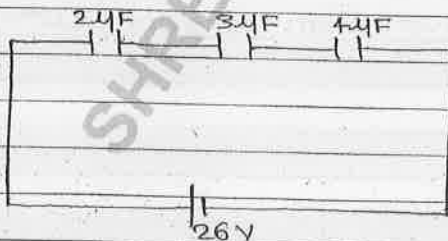

Find:-

① voltage in each 'C'.

② $Q_{3\mu F} = ?$

③ $U_{2\mu F} = ?$

④ $E_{4\mu F} = ?$ ($d = 3\text{mm}$)

Ans > (i) $\because V \propto \frac{1}{C}$

$$V_2 : V_3 : V_4 = \left(\frac{1}{2} : \frac{1}{3} : \frac{1}{4} \right) \times 12 = 6 : 4 : 3$$

$$V_2 = \frac{6}{13} \times 26 = 12 \text{ V}$$

$$V_3 = \frac{4}{13} \times 26 = 8 \text{ V}$$

$$V_4 = \frac{3}{13} \times 26 = 6 \text{ V}$$

(ii) $Q_{3\mu\text{F}} = ?$

$$\begin{aligned} Q &= CV \\ &= (3 \times 10^{-6}) (8) \\ &= 24 \mu\text{C} \end{aligned}$$


(iii) $U_{2\mu\text{F}} = ?$

$$\begin{aligned} U &= \frac{1}{2} CV^2 \\ &= \frac{1}{2} (2 \times 10^{-6}) (12)^2 \end{aligned}$$

(iv) $E_{4\mu\text{F}} = ?$ if $d = 3 \text{ mm}$.


$$E = \frac{V}{d} = \frac{6}{3 \times 10^{-3}} = 2 \times 10^3 = 2 \text{ kV/m}$$

Ques >

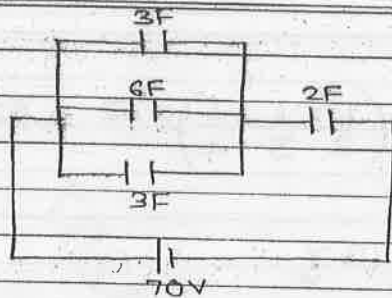

∴ Voltage across each capacitor?

Soln :-

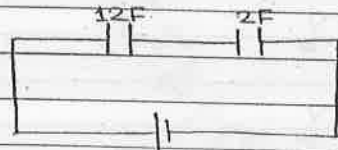


$$V_{12} : V_2 = \left(\frac{1}{12} : \frac{1}{2} \right) \times 12$$

$$= 1 : 6$$

$$V_{12} = \frac{1}{7} \times 70 = 10V$$


$$V_2 = \frac{6}{7} \times 70 = 60V$$

Ques >

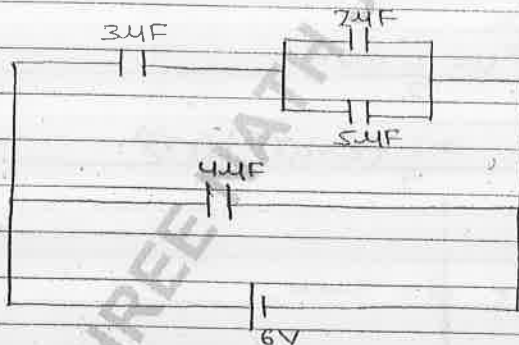

∴ Voltage across each capacitor?

Soln:

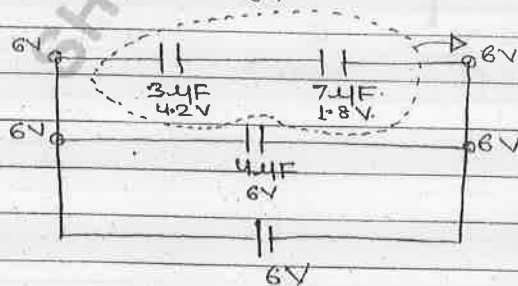


$$V_3 : V_7 = \left(\frac{1}{3} : \frac{1}{7} \right) \times 21$$

$$= 7 : 3$$

$$V_3 = \frac{7}{10} \times 6 = 4.2V$$

$$V_7 = \frac{3}{10} \times 6 = 1.8V$$

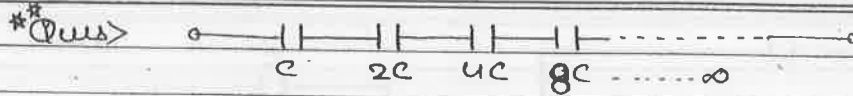


calculate $C_{eq} = ?$

$$\begin{aligned} \text{soln:- } \frac{1}{C_{eq}} &= \frac{1}{C} + \frac{1}{2C} + \frac{1}{4C} + \frac{1}{8C} + \dots \infty \\ &= \frac{1}{C} \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \dots \infty \right) \end{aligned}$$

$$\begin{aligned} \frac{1}{C_{eq}} &= \frac{1}{C} \left[\frac{1}{1 - \frac{1}{2}} \right] \\ &= \frac{2}{C} \end{aligned}$$

$$\boxed{C_{eq} = C/2}$$

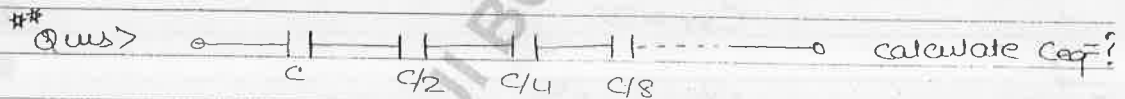

$$\begin{aligned} \text{soln:- } \frac{1}{C_{eq}} &= \left[\frac{1}{C} + \frac{2}{C} + \frac{4}{C} + \frac{8}{C} + \dots \infty \right] \\ &= \frac{1}{C} (1 + 2 + 4 + 8 + \dots \infty) \\ &= \frac{\infty}{C} = \infty \end{aligned}$$

$$\therefore S_p = \frac{a}{1}$$

$$\boxed{C_{eq} = \frac{1}{\infty} = 0}$$

$$\therefore S_0 = \frac{a}{1} \left. \begin{array}{l} \text{EXTRA} \\ \text{POINT.} \end{array} \right\}$$


$$\therefore [S_0 = \infty; \text{if } (r > 1)]$$

should must less than one. ($\therefore < 1$)

∴ charge 'd' current move from High Potential to Low Potential,

Date _____ Page _____

Ques >

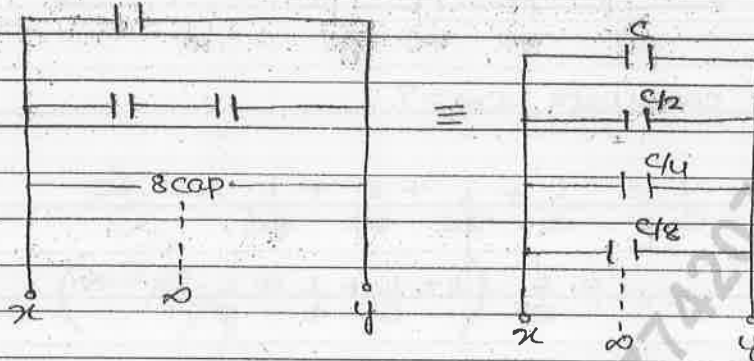

Soln :-


$$C_{xy} = ?$$

$$C_{xy} = C + \frac{C}{2} + \frac{C}{4} + \frac{C}{8} + \dots \infty$$

$$= C \cdot \frac{1}{1 - 1/2}$$

$$C_{xy} = 2C$$

Ques >

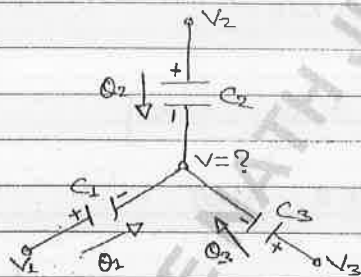

∴ Find Potential of common point.?

Soln :- KCL, $\sum Q = 0$


$$-Q_1 - Q_2 + Q_3 = 0$$

$$Q_1 + Q_2 + Q_3 = 0$$

$$C_1(V_1 - V) + C_2(V_2 - V) + C_3(V_3 - V) = 0$$

$$V = \frac{C_1 V_1 + C_2 V_2 + C_3 V_3}{C_1 + C_2 + C_3} \quad \text{W}$$

Ques)

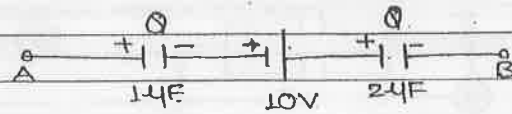Given:- $V_A - V_B = 5V$ $\Rightarrow V_{1\mu F} = ?$

Soln:- By KVL:-

Ist method:-

$$V_A - \frac{Q}{1 \times 10^{-6}} + 10 - \frac{Q}{2 \times 10^{-6}} = V_B$$



$$(V_A - V_B) + 10 = \frac{3Q}{2} \times 10^6$$

$$5 + 10 = \frac{3Q}{2} \times 10^6$$

$$Q = 10 \mu F$$

IInd method:-

Circuit

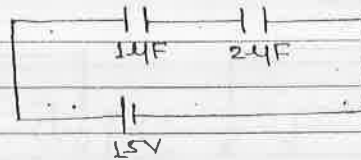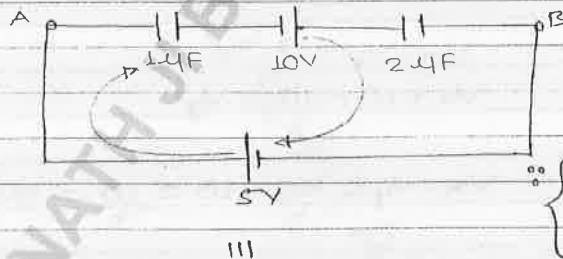


$$V_1 : V_2 = 2 : 1$$

$$\therefore V_1 = \frac{2}{3} \times 15 = 10V$$


$$\therefore V_2 = \frac{1}{3} \times 15 = 5V$$

Ques >

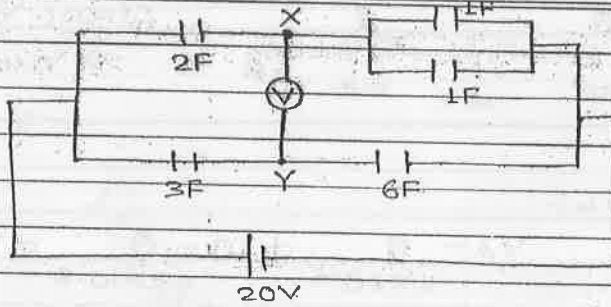

✓ Reading = ?

Soln :-

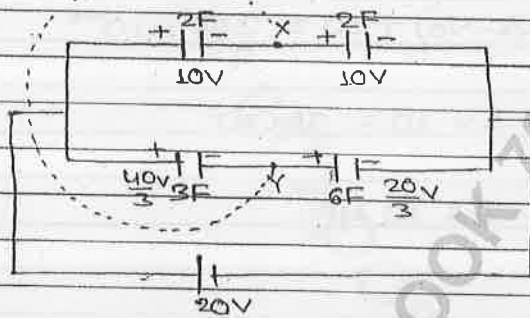


$$V_x - V_y = ?$$

$$V_x + 10 - \frac{40}{3} = V_y$$


$$V_x - V_y = \frac{40}{3} - 10 = \frac{10}{3} = 3.33V$$

Ques >

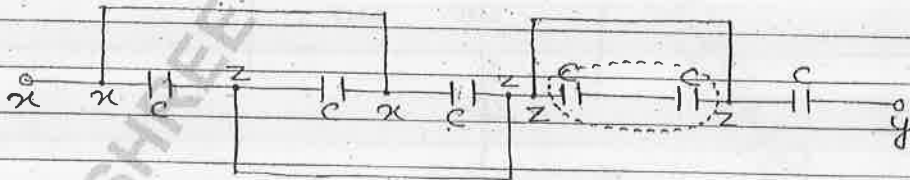


$C_{xy} = ?$

Soln :-

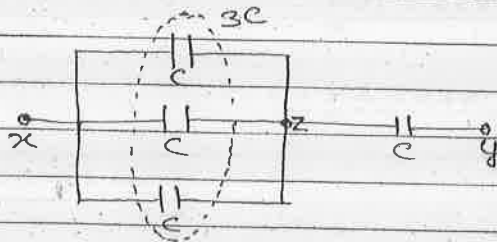


$$C_{xy} = \frac{3C}{4}$$

Ques >

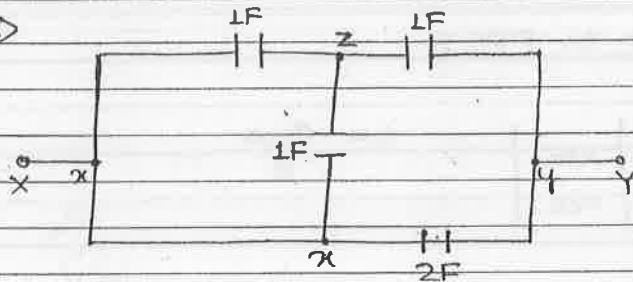


$C_{XY} = ?$

Soln

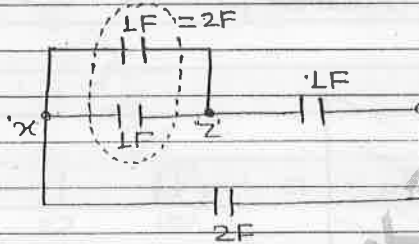


$$C_{XY} = \frac{2+2}{3} = \frac{8}{3}$$

Ques >

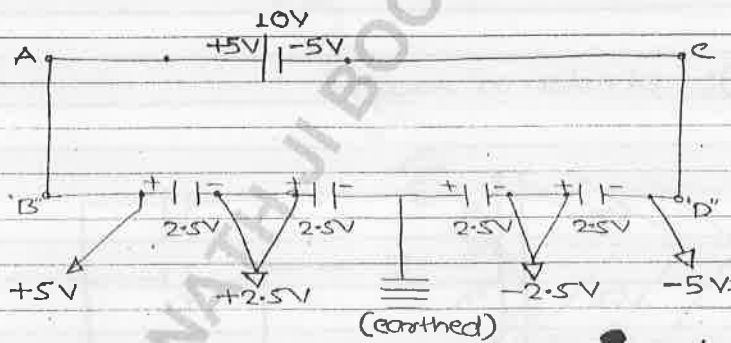

Ques > $\frac{4}{3}C$

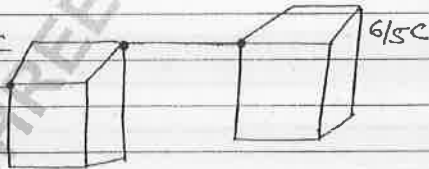

Soln :-
$$L = \frac{3}{4C} + \frac{5}{6C} = \frac{9+10}{12C}$$


$$C_{eq} = \frac{12C}{19}$$

☆ ⇒ Partition in PPC :-


Given :-

Area	C = $\frac{\epsilon_0 A}{d}$
Per	


① case: (I) :- Divsh in distance :-

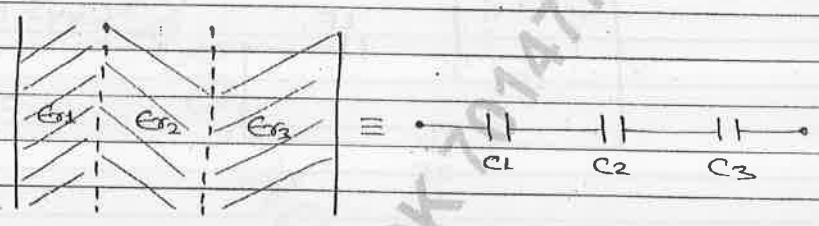

② case: (II) :- Division in Area :-

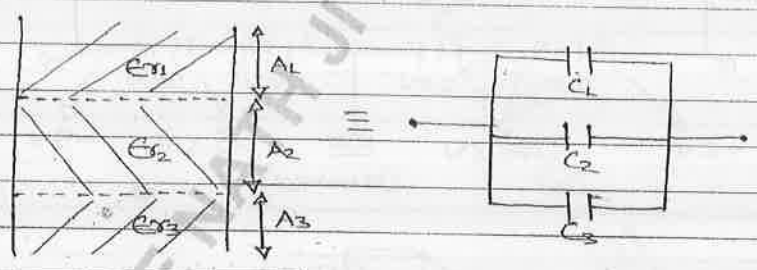

Ques)

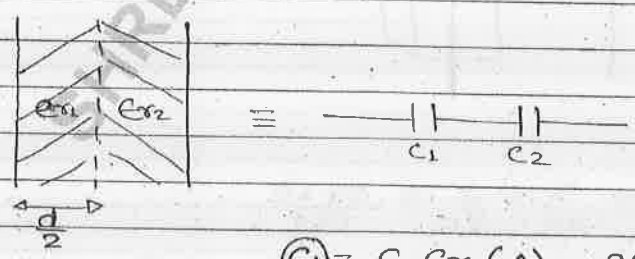


Ceq = ?

$$C_1 = \frac{\epsilon_0 \epsilon_{r1} (A)}{d/2} = 2\epsilon_{r1} \left(\frac{\epsilon_0 A}{d} \right) = 2\epsilon_{r1} C$$

$$C_2 = \frac{\epsilon_0 \epsilon_{r2} (A)}{d/2} = 2\epsilon_{r2} C$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \left(\frac{2 \epsilon r_1 \epsilon r_2}{\epsilon r_1 + \epsilon r_2} \right) \times C$$
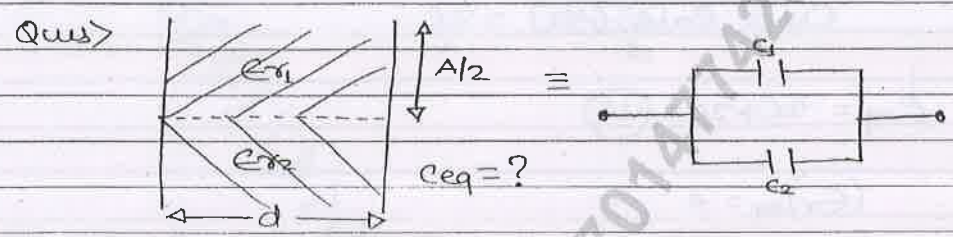
$$(\epsilon_r)_{eq} = \frac{2 \epsilon r_1 \epsilon r_2}{\epsilon r_1 + \epsilon r_2} \quad \because \text{(Harmonic Mean of } \epsilon r_1 \text{ \& } \epsilon r_2 \text{)}$$




som:- $C_1 = \frac{\epsilon_0 \epsilon r_1 (A/2)}{d} \Rightarrow \frac{\epsilon r_1 C}{2}$

$$C_2 = \frac{\epsilon_0 \epsilon r_2 (A/2)}{d} \Rightarrow \frac{\epsilon r_2 C}{2}$$

$$C_{eq} = C_1 + C_2 = \left(\frac{\epsilon r_1 + \epsilon r_2}{2} \right) \times C$$
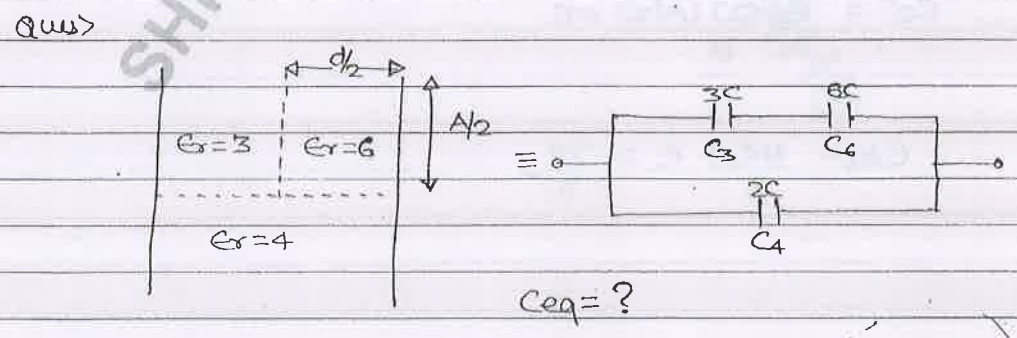
$$(\epsilon_r)_{eq} = \frac{\epsilon r_1 + \epsilon r_2}{2} \quad \because \text{Arithmetic Mean of } \epsilon r_1 \text{ \& } \epsilon r_2$$



$$\text{soln: } C_3 = \frac{\epsilon_0(3)(A/2)}{d/2} = 3C.$$


$$C_6 = \frac{\epsilon_0(6)(A/2)}{d/2} = 6C.$$

$$C_4 = \frac{\epsilon_0(4)(A/2)}{d} = 2C$$

$$C_{eq} = 2C + 2C = 4C$$

$$(\epsilon_r)_{eq} = 4$$

IT
2015 Qus

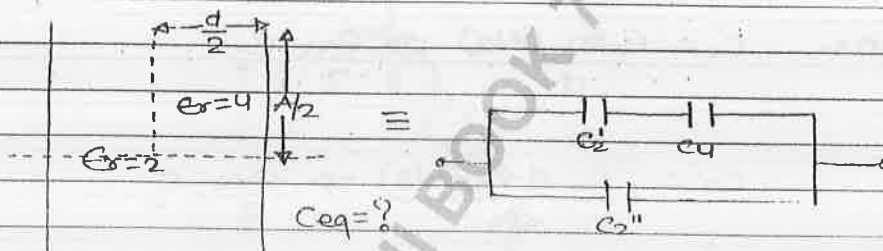


$$\text{soln: } C_4 = \frac{\epsilon_0(4)(A/2)}{d/2} = 4C$$

$$C_2' = \frac{\epsilon_0(2)(A/2)}{d/2} = 2C$$

$$C_2'' = \frac{\epsilon_0(2)(A/2)}{d} = C$$
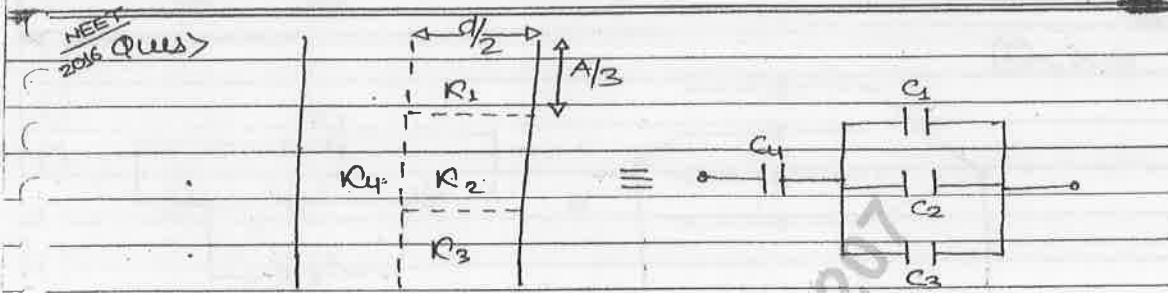
$$C_{eq} = \frac{4C}{3} + C = \frac{7C}{3}$$




★ ⇒ MULTIPLATE CAPACITOR :-

→ Given Plate Arrangement is converted into CRT, Using *Polar Potential Method.

step: ① "Nomerling" of Plates is Done. conductor's connected with each other consider as single conductor.

step: ② For making capacitor; plates should be consicntly and their potential should be different.


EX: - ①

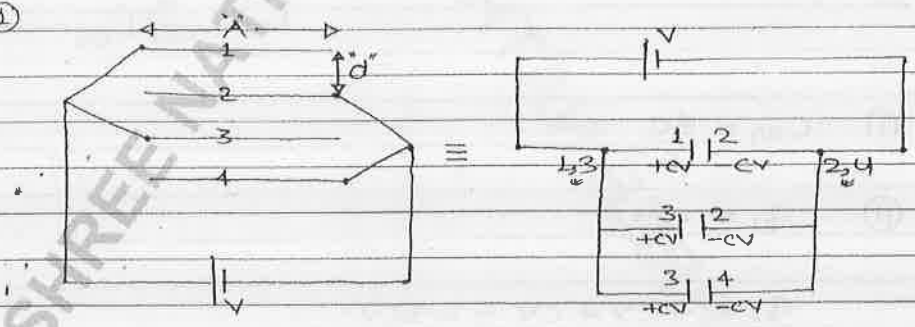

① $C_{eq} = 3C = 3 \left(\frac{\epsilon_0 A}{d} \right)$

② $q_1 = +CV$ $q_3 = +CV + CV = +2CV.$
 $q_2 = -CV - CV = -2CV.$ $q_4 = -CV.$


EX: (2)

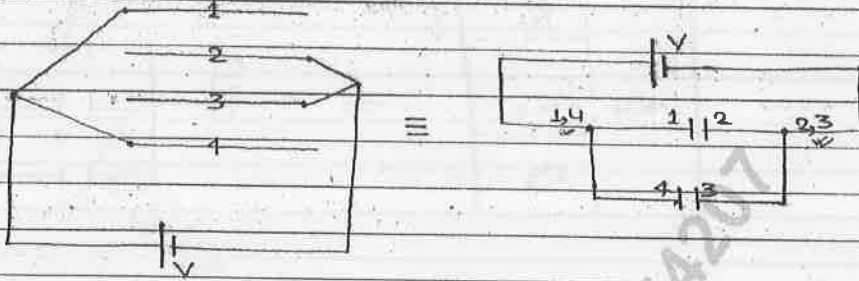

(i) $C_{eq} = 2C$

(ii) $q_1 = +CV$ $q_2 = -CV$
 $q_3 = -CV$ $q_4 = +CV$

EX: (3)

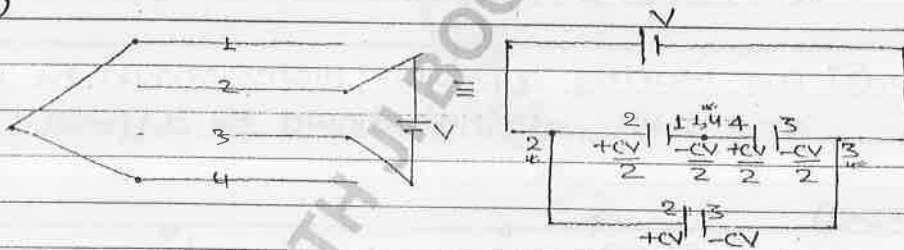

(i) $C_{eq} = \frac{3C}{2}$

(ii) $q_1 = \frac{-CV}{2}$

$$q_2 = \frac{+CV}{2} + \frac{+CV}{2} = \frac{+3CV}{2}$$

$$q_3 = \frac{-CV}{2} - \frac{CV}{2} = \frac{-3CV}{2}$$

$$q_4 = \frac{+CV}{2}$$

*** Terminal point सब से दूर बनाइये।


** \Rightarrow If "Alternate Plates" are connected, then Maxm capacitor's " $n-1$ " are formed in "Parallel Groupings."

so;

AIEEE

$$C_{\text{Max}} = (n-1)C$$


Ques >

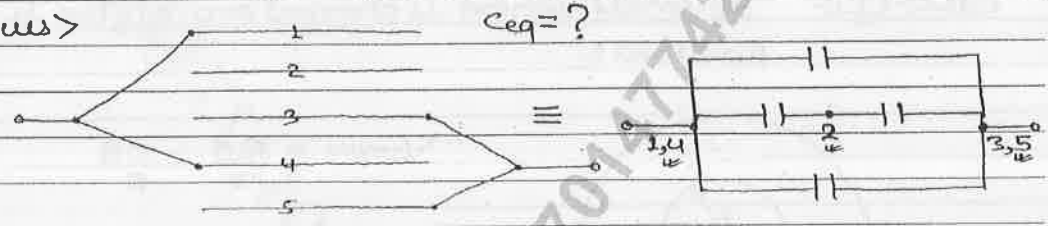

soln :-

$C_{eq} = 2.5$

Ques >

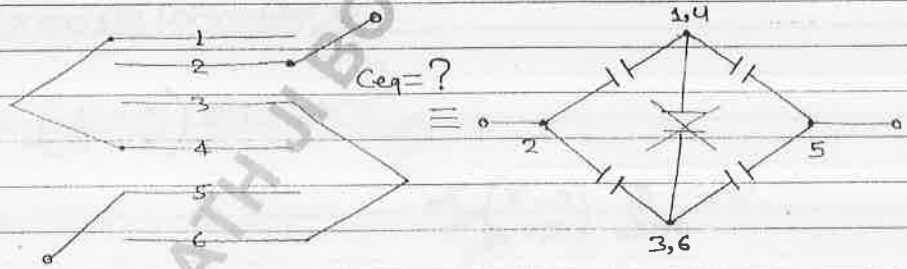

\rightarrow Balanced wheat stone Brid.


soln :-

$C_{eq} = C_w$

☆ ⇒ SPHERICAL CAPACITOR:-

It has TWO (2) concentric metallic shell,
where one is charged and another is earthed.

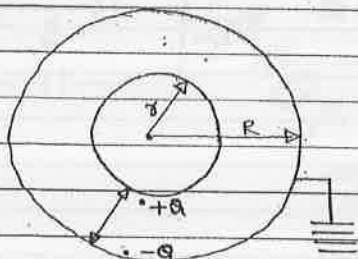case: (I):- of "small" sphere is charged and "Big" one is
earthed:-



$$V_{\text{small}} = \frac{kQ}{r} - \frac{kQ}{R}$$

$$V_{\text{big}} = \text{zero } (0)$$

∴ Potential Difference (P.D):-

$$V = kQ \left(\frac{1}{r} - \frac{1}{R} \right)$$

$$V = \frac{Q}{4\pi\epsilon_0} \left(\frac{R-r}{Rr} \right)$$

$$\frac{Q}{V} = \frac{4\pi\epsilon_0 Rr}{R-r}$$

$$\text{*IMP.} \quad C_I = \frac{4\pi\epsilon_0 \epsilon_r Rr}{R-r}$$

Ques) If; $r = \text{fix}$ And $R \uparrow \Rightarrow C = ?$

soln:- $C = \frac{4\pi\epsilon_0 \epsilon_r r}{1 - \frac{r}{R}} \therefore \text{[by dividing by (R)]} \Rightarrow C \downarrow$

Ques > If $r = \text{fix}$; And $R \downarrow \Rightarrow C = ?$

soln :- $C \Rightarrow \uparrow$.


* Ques > If $r = \text{fix}$; And $R = \infty \Rightarrow C' = ?$

soln :- $C' = 4\pi\epsilon_0\epsilon_r \frac{r}{1 - \frac{r}{\infty}}$

$$C' = 4\pi\epsilon_0\epsilon_r \cdot r$$

** \Rightarrow "SINGLE CONDUCTOR" is also a capacitor, considering that its another conductor is at "Infinity."

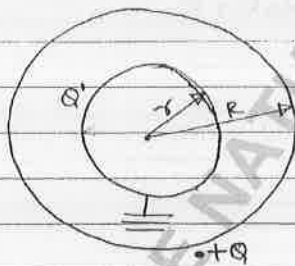Case: (II) :- If "BIG SPHERE" is charged & "small sphere" is Earthed :-



\Rightarrow As small sphere is earthed, some charge " Q' " is transferred to small sphere from Earth, for making its potential zero

$$\because V_{\text{small}} = 0$$

$$\frac{kQ'}{r} + \frac{kQ}{R} = 0$$

$$Q' = -\frac{r}{R} Q$$

$$\because V_{\text{small}} = 0$$

$$V_{\text{big}} = \frac{kQ}{R} + \frac{kQ'}{R}$$

\because PD :-

$$V = \frac{kQ}{R} + \frac{kQ'}{R}$$

PTO...

$$\therefore V = \frac{RQ}{R} + \frac{RQ}{R}$$

$$= \frac{RQ}{R} + \frac{R}{R} \left(\frac{-\gamma Q}{R} \right)$$

$$= \frac{RQ}{R} \left(\frac{1-\gamma}{R} \right)$$


$$V = \frac{Q}{4\pi\epsilon_0 R} \left(\frac{R-\gamma}{R} \right)$$

$$\frac{Q}{V} = \frac{4\pi\epsilon_0 R^2}{R-\gamma}$$

$$C_{II} = \frac{4\pi\epsilon_0 \epsilon_r R^2}{R-\gamma}$$

$$C_{II} = \frac{4\pi\epsilon_0 \epsilon_r R \gamma + 4\pi\epsilon_0 \epsilon_r R}{R-\gamma}$$

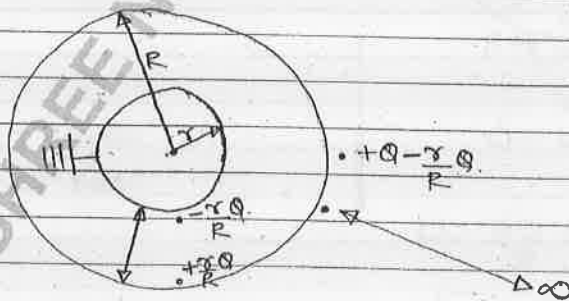
$$C_{II} = C_I + 4\pi\epsilon_0 \epsilon_r R$$



Ques > Spherical conductor of Radius " r "; capacitance = C
i.e.: $4\pi\epsilon_0\epsilon_r R$.

if it is surrounded by metal sphere of Radius " R "; where $\frac{R}{r} = n$; then capacitance?


soln.

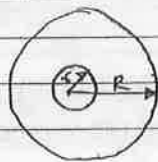

$$C' = 4\pi\epsilon_0\epsilon_r \frac{rR}{R-r} = C \frac{1 - \frac{r}{R}}{1 - \frac{r}{R}}$$

$$= \frac{C}{n - n + 1} \Rightarrow \frac{nC}{n}$$

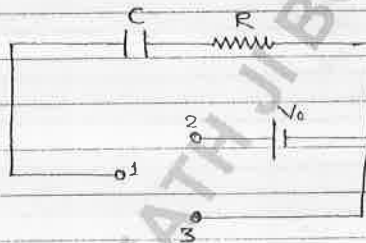**~~XX~~ ⇒ "CHARGING" AND "DISCHARGING" OF CAPACITOR:-



① case:-(I):- "CHARGING" (1-2)

At; $t=0$	$t \uparrow$	$t = \infty$ {full charge}	} Max ^m
$V_c = 0$	$V_c = \uparrow$	$V_c = V_0$	
$Q_c = 0$	$Q_c = \uparrow$	$Q_c = CV_0$	
$U_c = 0$	$U_c = \uparrow$	$U_c = \frac{1}{2} CV_0^2$	
$I_{ckt} = \frac{V_0}{R}$ (Max.)	$I_{ckt} = \downarrow$	$I_{ckt} = 0$ (Min.)	

→ KVL:-

$$V_c = V_0 \left(1 - e^{-t/RC}\right) \quad \therefore \uparrow$$

$$I_{ckt} = I_{max} e^{-t/RC} \quad \text{(Decay)} \quad \therefore \downarrow$$

⊛ ⇒ Point's to Remember :-

$$e^0 = 1$$

$$e^{\infty} = \infty$$

$$e = 2.73$$

$$e^{-\infty} = 0$$

$$\frac{1}{e} = 0.37$$

$$\log_e x = 2.303 \log_{10} x$$

$$\log_{10} 2 = 0.3010$$

$$\log_e 2 = 2.303 \log_{10} 2$$

$$\log_{10} 3 = 0.477$$

$$= 2.303 \times 0.3010$$


$$= 0.693$$

$$\log_{10} 5 = 0.699$$


$$\log_{1/x} x = 1$$

⇒ GRAPH :-

(i) I_{ext} v/s t :-

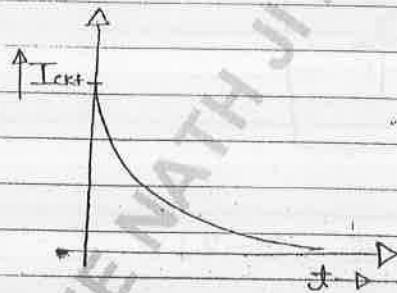

(ii) V_c v/s t :-

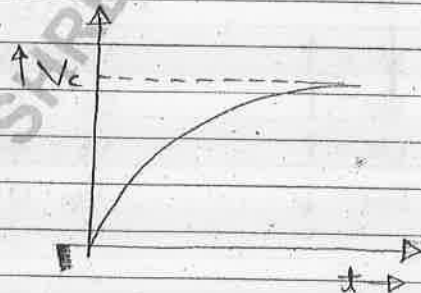

⊗ → Time constant (τ):-

$$\tau = RC \quad \text{∴ [63% charging]}$$

* I_{max}
** →

$$t = \tau \quad 63\%$$

$$t = 3\tau \quad 95\%$$

$$t = 5\tau \quad 99.9\%$$

→ $R \uparrow \Rightarrow \text{timing.} \uparrow$

$R \downarrow \Rightarrow \text{timing.} \downarrow$

② case: (II) ∴ "DISCHARGING" (1-3) ∴-

At; $t=0$

$$V_c = V_0$$

$$Q_c = eV_0$$

$$U_c = \frac{1}{2} eV_0^2$$

$$*I_{c(t)} = \frac{V_0}{R}$$

$t \uparrow$

$$V_c \downarrow$$

$$Q_c \downarrow$$

$$U_c \downarrow$$

$$I_{c(t)} \downarrow$$

$t = \infty$ [Fully discharge]

$$V_c = 0$$

$$Q_c = 0$$



$$U_c = 0$$

$$I_{c(t)} = 0$$

$$\rightarrow V_c = V_0 e^{-t/RC}$$

$$I_{c(t)} = I_{\text{max}} e^{-t/RC}$$

-disap: intensity

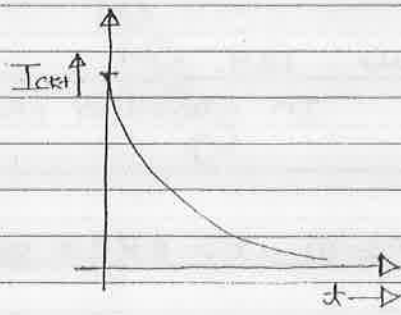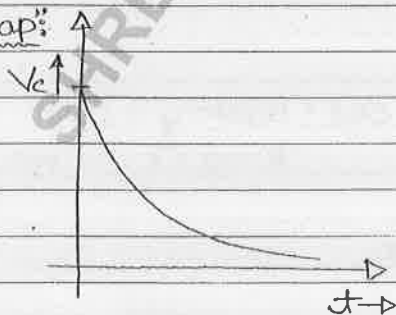

⊗ ⇒ Time constant (τ)

$$\tau = RC \quad \% (63\% \text{ Discharge})$$

$$t = \tau \quad 63\%$$

$$t = 3\tau \quad 95\%$$

$$t = 5\tau \quad 99.3\%$$

⊗ ⇒ $R \uparrow = \text{Timing} \uparrow$

⊗ ⇒ * "Total stored Energy" of capacitor is conserved converted into Heat of Resistance.

SO Heat;

$$\text{Heat} = \frac{1}{2} CV_0^2$$

** Heat is Independent of Resistance.

⊗ ⇒ $t = 0$; Uncharged capacitor = short ckt.
*($I = \text{Max}$)

$t = \infty$; Fully charged capc. = open ckt.
*($I = 0$)

Ques) 12V.

In capacitor charging ckt; Battery = 12V

$$R = 2 \Omega \quad C = 100 \mu F$$

soln :- (i) $\tau = RC = 200 \mu \text{ sec.}$

$$(ii) I_{\text{max}} = \frac{V_0}{R} = \frac{12}{2} = 6A.$$

(ii) I_{ckt} at $t = 400 \mu\text{sec}$.

$$\begin{aligned} I_{ckt} &= \frac{V_0}{R} e^{-t/RC} \\ &= \frac{12}{2} e^{-\frac{400 \times 10^{-6}}{200 \times 10^{-6}}} \\ &= 6 e^{-2} \\ &= \frac{6}{e^2} \end{aligned}$$

(iv) 99% charging :-

$$V_c = V_0 (1 - e^{-t/RC})$$

$$0.99 V_0 = V_0 (1 - e^{-t/RC})$$

$$0.99 - 1 = -e^{-t/RC}$$

$$-0.01 = -e^{-t/RC}$$

$$\frac{1}{100} = e^{-t/RC}$$

$$100 = e^{t/RC}$$

$$\log_e 100 = \frac{t}{RC}$$

$$t = RC \log_e 100$$

$$t = 2RC \log_e 10$$

$$= 2 \times 2 \times 100 \times 10^{-6} (2.303 \times \log_{10} 10)$$


$$= 921.2 \mu\text{sec}$$

** Note :- 63% charge = τ = time $\therefore [\tau = RC]$

95% charging = 3τ = time

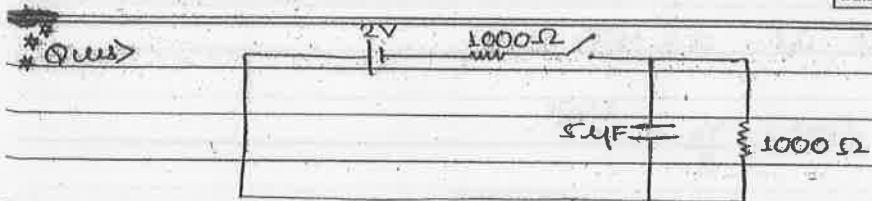99.3% charging = 5τ = time


so; For 99% charging time will be slightly less than "5 τ ".




Find capacitor current at:-

- (i) $t = 0$
- (ii) $t = \infty$

soln:- (i) $t = 0$;

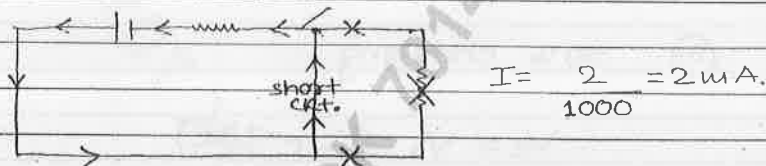

(ii) $t = \infty$;

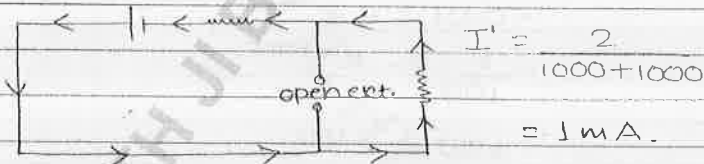

Ques → After Full charging; capacitor is discharge than;
 giv; $R = 10 \text{ k}\Omega$ $C = 0.1 \mu\text{F}$

soln:- (i) $\tau = R \cdot C$

$$= (10 \times 10^3) (0.1 \times 10^{-6})$$

$$= 1 \text{ second. } \therefore [\text{In } 1 \text{ second; } 63\% \text{ Discharge}]$$

(ii) $V_c = V_0 e^{-t/\tau}$

$$\frac{V_0}{2} = V_0 e^{-t/\tau}$$

$$2 = e^{t/RC}$$

$$\log_e 2 = t/RC$$

$$t = RC \log_e 2$$


$$= (10 \times 10^6) (0.1 \times 10^{-6}) (0.693)$$

$$= 0.693 \text{ sec.}$$

(iii) Time taken for 80% Discharge :-

$$V_c = V_0 e^{-t/RC}$$

$$0.2 V_0 = V_0 e^{-t/RC}$$

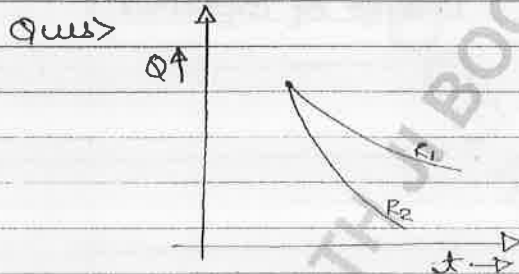


∴ time (2) < time (1)

∴ $R_2 < R_1$

☆ ⇒ R-C CIRCUIT (CRT) :-

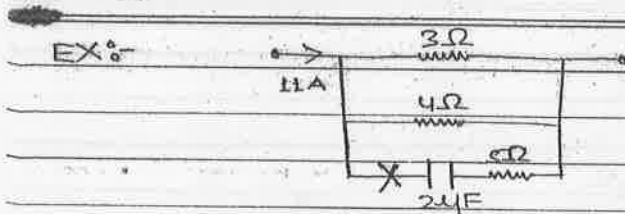In "stable condition" or "steady state condition", capacitor's are fully charged, so current in the capacitive branch is "zero".




soln:- $I_{3\Omega} = 0$

$I_3 : I_4 = 4 : 3$

$I_3 = \frac{4}{7} \times 11 = \frac{44}{7} \text{ A}$

$I_4 = \frac{3}{7} \times 11 = \frac{33}{7} \text{ A}$

*Ques>

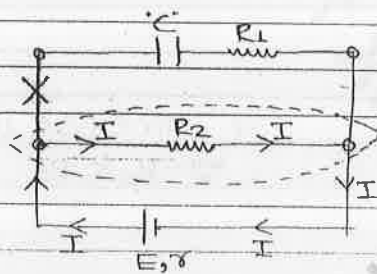

In stable condition, Find charge of capacitor?

soln:- $I = \frac{E}{R_2 + \gamma}$

$V_{R_2} = I \times R_2$
 $= \frac{R_2}{R_2 + \gamma} E$


$\therefore V_{R_2} = V_c + V_{R_1}$

$\therefore V_{R_1} = \overset{\text{Current}}{\text{constant}} \times R_1$
 $= 0 \times R_1$
 $= 0$

$$\begin{aligned} \therefore V_c &= V_{R_2} \\ V_c &= \frac{R_2}{R_2 + r} E \end{aligned}$$

$$Q = C V_c = \frac{R_2}{R_2 + r} C E$$

$$= \frac{C E}{\frac{R_2 + r}{R_2}}$$

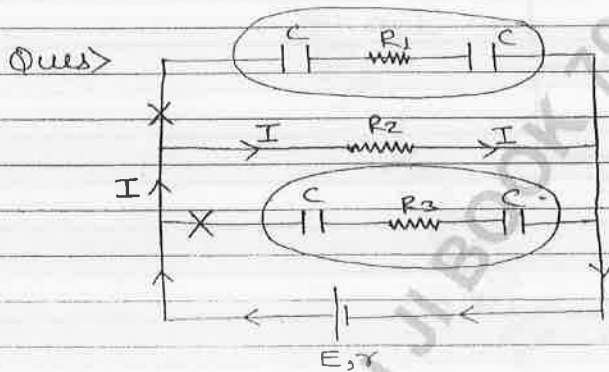

soln :- $\therefore I = \frac{E}{R_2 + r}$

$$\begin{aligned} \therefore V_{R_2} &= I \times R_2 \\ &= \frac{R_2}{R_2 + r} E \end{aligned}$$

$$\therefore V_{R_2} = V_c + V_{R_1} + V_c$$

$$\therefore V_{R_2} = V_c + V_{R_3} + V_c$$


$$\therefore V_{R_1} = V_{R_3} = 0 \quad (\therefore \text{current} = 0)$$

$$\because V_R = V_R + V_{R1}$$

$$\text{Each } V_C = \frac{V_{R2}}{2} = \frac{R_2}{R_2 + R} \cdot \frac{E}{2}$$

$$\because Q = CV_C = \frac{R_2}{R_2 + R} \cdot CE$$

AIEEE
Ques)

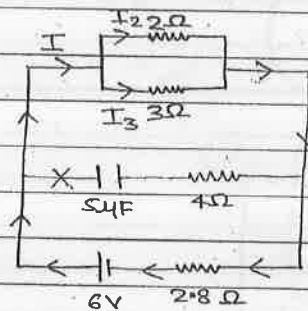



$$I_{2\Omega} = ?$$

Soln :- $I = \frac{6}{1.2 + 2.8} = 1.5 \text{ A}$


$$I_2 : I_3 = 3 : 2$$

$$I_2 = \frac{3}{5} \times 1.5 = 0.9 \text{ A}$$

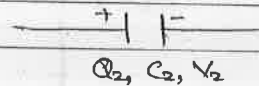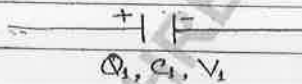★ \Rightarrow TO CONNECT CHARGED PPE'S :-





① series :-

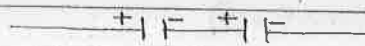


\Rightarrow "NO close loop," so NO charge


flow; so NO any change

in detail of ppe.

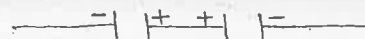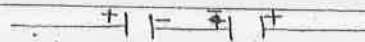

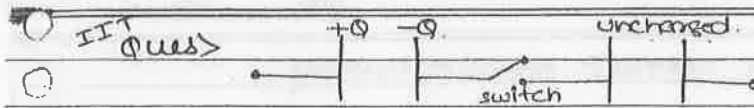

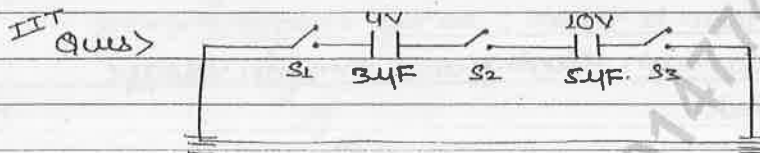soln:- If switch is made ON then;
No close loop so; No charge flow; so
uncharged capacitor will remain unchanged.



soln:- If any "one" or "two" switches are made ON,
then no close loop, so no charge flow so;
No change in detail of p.c.

② Parallel:-

① case:- ①:- To connect some polarity ends:-



close loop is there; so due to potential difference
** charge sharing takes place to make common voltage.


$$V_c = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$

$$\Delta U = \frac{C_1 C_2 (V_1 - V_2)^2}{2(C_1 + C_2)}$$

→ If "Nothing is given", then consider it of "same Polarity".

Date _____ Page _____

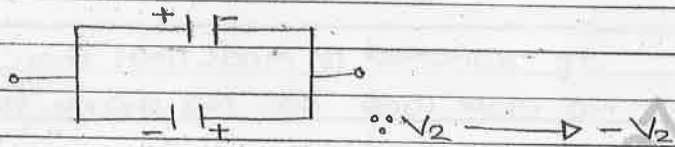② case: (II) :- TO connect opposite Polarity



A close loop is there; so by charge sharing finally common Polarity and common voltage are developed.

$$V_{\text{common}} = \frac{C_1 V_1 - C_2 V_2}{C_1 + C_2}$$

$$\Delta U = \frac{C_1 C_2 (V_1 \oplus V_2)^2}{2(C_1 \oplus C_2)}$$

*Ques capacitor; $\begin{array}{c} C, V \\ | | \end{array}$

capacitor; $\begin{array}{c} C, \text{Neutral} \\ | | \end{array}$

if these are connected in parallel then :-

soln: (i) $V_{\text{common}} = \frac{C V + C(0)}{C+C} = \frac{V}{2}$

(ii) charge of each capacitor :-

$$Q_1 = C_1 V_1 = C \times \left(\frac{V}{2}\right) = \frac{CV}{2}$$


$$Q_2 = C_2 V_2 = C \times \left(\frac{V}{2}\right) = \frac{CV}{2}$$

$$(iii) \Delta U = \frac{C_1 C_2 (V_1 + V_2)^2}{2(C_1 + C_2)} \quad \because (\text{same polarity})$$

$$= \frac{C \cdot C (V - 0)^2}{2(C + C)}$$

$$= \frac{1}{4} CV^2$$

NEET
2016
Ques >

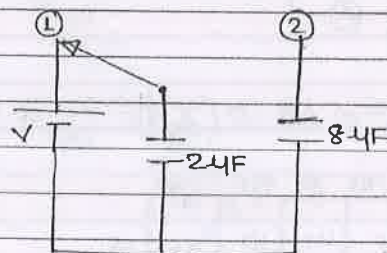

\Rightarrow If Liver is shifted to posn (2) than % loss in stored energy ?

soln: Initial:


$$U = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 24 (V)^2 = 12V^2$$

$$\Delta U = \frac{2 \times 8}{2(2+8)} (V-0)^2 = \frac{8}{10} V^2$$

$$\therefore \% \text{ Loss} = \frac{\Delta U}{U} \times 100$$

$$= \frac{(8/10)V^2}{12V^2} \times 100 = 80\%$$

EX: 1 Q; 81 >

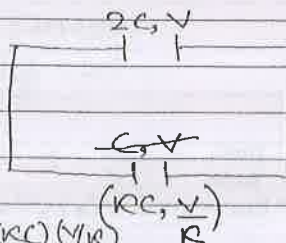

$$\because Q = CV$$

$$V \propto \frac{1}{C}$$

soln :-

$$V_{\text{com}} = \frac{(20)(V) + (kC)(V/R)}{2C + kC}$$

$$= \frac{3V}{k+2}$$


"CURRENT EXERCISE:-"

Date _____ Page _____

EX:- (1):-


(27) $\frac{6}{\frac{1}{3} + R} = 4$
 $\frac{6}{\frac{1}{3} + R} = \frac{4R}{3} + 4R \Rightarrow \frac{4R}{3} = 4 \Rightarrow R = 7$

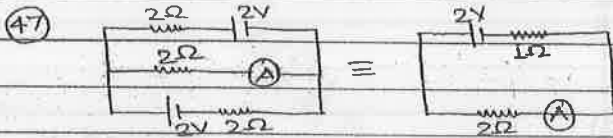(36) $\frac{r}{n} = x \Rightarrow r = nx$
 $R_{series} = nr \Rightarrow R_{series} = n(n \cdot x) = n^2 x$




EX:- (2):-

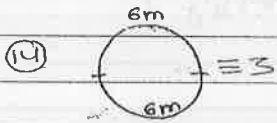(2) $H = I^2 R t = ms \Delta \theta \Rightarrow I^2 \propto \Delta \theta \Rightarrow \left(\frac{I}{2I}\right)^2 = \frac{3C}{\Delta \theta} \Rightarrow \Delta \theta = 12^\circ C$




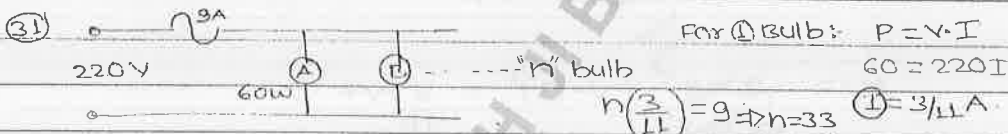(28) $20 \text{ cell } 20 \times 1.8 = 36V$
 $20 \times 1.8 = 36V$
 $220V$
 $R = ? \Rightarrow I = \frac{220 - 36}{2 + R} = 15 \Rightarrow R = 10.27 \Omega$





(46) $H_{40} = H_{100}$
 $H_4 : H_6 = 2:3$

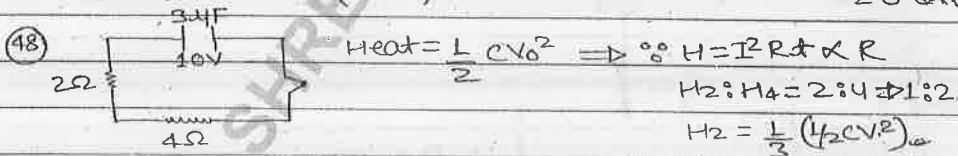(51) $(\frac{E}{40+r})^2 40 \cdot t = (\frac{E}{100+r})^2 100 \cdot t$
 $I = q \cdot f \Rightarrow 2 \times 10^{-2} \times f = 0.6 A$



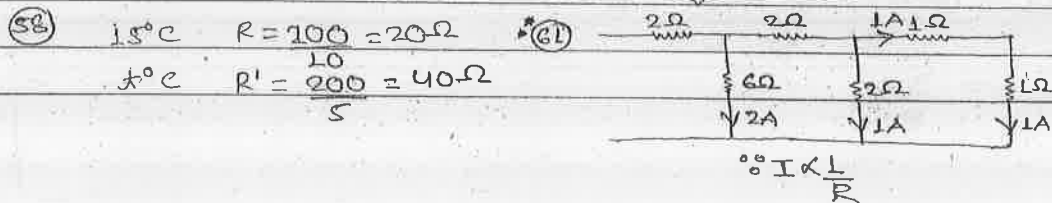(55) $R_{oc} = ?$ $R_{oA4} = ?$
 $R_{oc} + R_{oA4} = 30$ --- (i)
 $R_1 \times 1 + R_2 \times 2 = 0 \Rightarrow R_{oc} = 80/3$ $R_{oA4} = 10/3$
 $\frac{R_{oc}}{R_{oA4}} = \frac{R_{oA1}}{R_{oc}} = 8$ --- (ii)



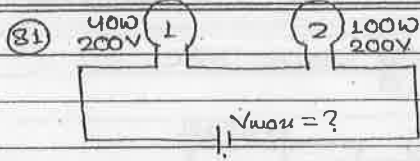

$V_1 : V_2 = 5 : 2$

$V_1 = \frac{5}{7} V_{max} = 200 \Rightarrow V_{max} = 280V$
 $V_2 = \frac{2}{7} V_{max} = 200 \Rightarrow V_{max} = 700V$



37) $V_d = \frac{I}{n e A}$ $1 \text{ cm}^3 \equiv 9 \text{ gm} \equiv N_A \times 9$
 $\rightarrow 1 \text{ m}^3 = \frac{N_A}{63} \times 9 \times 10^6$

39) $V = E - IR$

☆ \Rightarrow EX:- 3(A) :-


6) $\alpha = \frac{V_{AB}}{L} = \frac{IS}{A}$

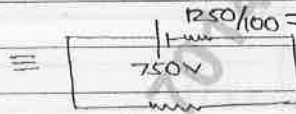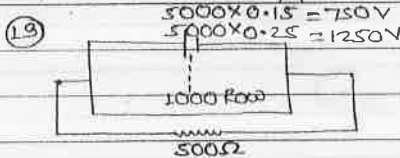14) electrostat $\Rightarrow \Delta R + \Delta V = 0 \Rightarrow \Delta R = -\Delta V$




$I = \frac{750}{500 + 1250} = 1.5A$

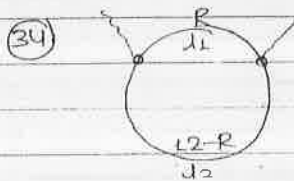15) $\% \eta = \frac{(V \times I \times t)_{\text{output}}}{(V \times I \times t)_{\text{input}}} \times 100 \Rightarrow \frac{15 \times 14 \times 5}{15 \times 8 \times 10} \times 100 = 87.5\%$



$R \frac{(2-R)}{R + (2-R)} = \frac{8}{3}$

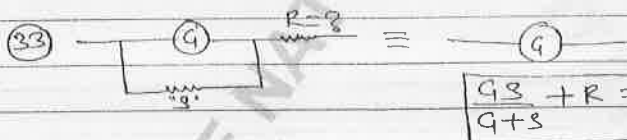$\therefore R = 4 \Omega$
 $\therefore R = 8 \Omega$
 $\therefore \frac{R_1}{R_2} = \frac{1}{2} = \frac{1}{2}$



$\frac{9S + R}{9 + S} = 9 \Rightarrow R = \frac{9^2}{9 + S}$

39) $V = IR$


1st; $R = 0 \Rightarrow V = 0$

$V = \frac{E}{R + r} R$


2nd; $R = \uparrow \Rightarrow V = \uparrow$

$V = \frac{E}{1 + \frac{r}{R}}$

3rd; $R = \infty \Rightarrow V = E$

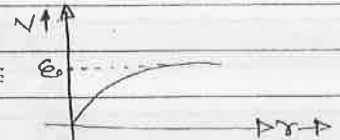

45)

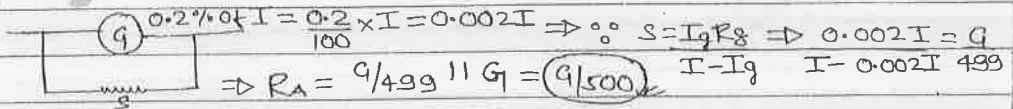


$0.2\% \text{ of } I = \frac{0.2}{100} \times I = 0.002I \Rightarrow S = I_g R_g \Rightarrow 0.002I = 9$
 $\Rightarrow R_A = \frac{9}{499} \parallel 9 = \frac{9}{500}$ $I - I_g$ $I - 0.002I$ 499

EX: 3'B:


(6) $E_1 = J_1 \Rightarrow E_2 = J_2$ $4 \cdot 8 = 40 \Rightarrow V = 7.2$
 $E_2 = J_2$ $E_2 J_2$ $V 60$

(14) Use Potent potential method.

(25)

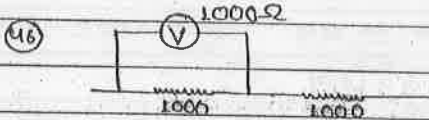

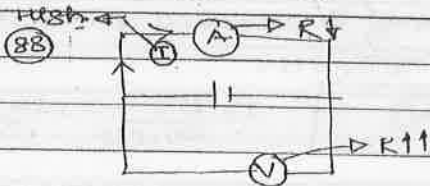(47) $R = 8 \cdot 1^2 \propto l \Rightarrow R = 1 : 2$ $\therefore V \propto d \times g \Rightarrow$ Bouancy
 $V \propto 1$ $V \propto 2$
 $V = 2 : 1$



SHREE NATHJI BOOK 701477207

EX: (1):

(29)

(31) $E = \frac{V}{D} = \frac{300V}{1 \times 10^{-3}} = 3 \times 10^5 \text{ N/C}$

(33)

(36) $Q = CV \Rightarrow \frac{1 \times 10^{-6}}{3 \times 10^2} = C$

$C = \frac{1 \times 10^{-8}}{3} \Rightarrow$

work done by battery = $2 \left(\frac{1}{2} CV^2 \right)$

$W = \left(\frac{1}{3} \right) \times 10^{-8} \times 9 \times 10^4 = 3 \times 10^{-4}$

(37) $\frac{\text{Work by Battery}}{\text{Energy stored}} = \frac{\frac{1}{2} CV^2 + \frac{1}{2} CV^2}{\frac{1}{2} CV^2} \Rightarrow$
Heat

$\Rightarrow 2:1$

(53) हर हमेशा एक EIND से CAPACITOR BRANCH छोट करते जाओगे!

(70) Capacitor is divided by area (1/2):

$= \frac{5 \mu\text{F}}{2} = \frac{\epsilon_0 A}{2d} + \frac{K \epsilon_0 A}{2d} \Rightarrow 10.4 \mu\text{F} = 2.5 \mu\text{F} + K \times 2.5 \mu\text{F}$

"OR"

$\frac{A_1 V}{K} \Rightarrow \frac{A_2}{2} \Rightarrow C/2 \Rightarrow 1.25$

$\Rightarrow 1.25 + 1.25 \epsilon_r = 5$

$\epsilon_r = 3$

(73) $C = \frac{4 \pi \epsilon_0 R \gamma}{R - \gamma}$

$(R - \gamma) = 1 \text{ mm. (given)}$

$1 \times 10^{-6} \times \frac{1}{9 \times 10^9} \times \frac{R}{1 \times 10^{-3}} \Rightarrow R(R - 1 \text{ mm}) = 9 \text{ (Neglect 1 mm)}$

$R^2 = 9 \Rightarrow R = (3 \text{ m})$

(77) $Q = CV \Rightarrow \frac{dQ}{dt} = C \frac{dV}{dt} \Rightarrow 100 \times 10^{-6} = 500 \left(\frac{10}{dt} \right) \Rightarrow dt = 50 \text{ s}$

EX: (2):

(3) $U = \frac{1}{2} CV^2 \Rightarrow U \propto C \Rightarrow C \rightarrow U \text{ of } (U) \text{ of } KC \text{ (Cap) than; } U = KU_0$
∵ (V = const)

(10) $250 = \frac{C_1(300) + C_2(100)}{C_1 + C_2}$

(10)

$$(28) \quad U = \frac{1}{2} \left(\frac{\epsilon_0 A}{d} \right) V_0^2 \Rightarrow \theta = \text{const.}$$

$$d' = 3d \Rightarrow C' = \frac{C}{3}$$

$$U' = 3U$$

$$= \frac{3}{2} \left(\frac{\epsilon_0 A}{d} \right) V_0^2$$

$$(29) \quad U_{\text{before}} = \frac{1}{2} C_1 V_0^2$$

$$U_{\text{after}} = \frac{1}{2} C_1 (V_{\text{com}})^2 + \frac{1}{2} C_2 (V_{\text{com}})^2$$

$$V_{\text{common}} = \frac{C_1 V_0}{(C_1 + C_2)} \Rightarrow = \frac{1}{2} (V_{\text{com}})^2 (C_1 + C_2)$$

$$\Rightarrow \frac{1}{2} \times (C_1 V_0)^2 \frac{(C_1 + C_2)}{(C_1 + C_2)^2}$$

$$U_{\text{before}} = \frac{1}{2} \frac{C_1 V_0^2}{(C_1 + C_2)} \Rightarrow \frac{(C_1 + C_2)}{C_1^2} \Rightarrow \frac{(C_1 + C_2)}{C_1}$$

$$(31) \quad \begin{array}{l} 1 \text{ sec} :- 50V \rightarrow 40V \\ 2 \text{ sec} :- 50V \rightarrow V_c \end{array} \quad (ii) \quad V_c = V_0 e^{-t/RC}$$

$$40 = 50 e^{-1/RC} \dots (1)$$

$$(31) \quad (i) \quad 1 \text{ sec} :- V_c = 40 = \left(\frac{4}{5} \right) \text{ part} \quad V_c = 50 e^{-2/RC} \dots (2)$$

$$= 50 \left(\frac{4}{5} \right) = 32 \text{ Volt from (1)}$$

$$U = \frac{1}{2} C \left(\frac{V_c}{2} \right) \Rightarrow \frac{16}{25.4}$$

\therefore both Ans. correct

$$(39) \quad K \theta = \frac{V}{r} \Rightarrow \text{same} \Rightarrow C_1 = \frac{\epsilon_0 A}{d} \quad C_2 = \frac{\epsilon_0 A}{\left(\frac{d-d}{2} \right) + \frac{d}{2\epsilon_r}} = \frac{2\epsilon_0 A}{d \left(1 + \frac{1}{\epsilon_r} \right)}$$

$$C_3 = \frac{2\epsilon_0 A (\epsilon_r - 1)}{d} \quad C_1 < C_2 < C_3$$

$$(41) \quad \text{capacitor} = 1 \mu F; \quad V_{\text{max}} = 500V$$

3A-13

$$\text{design} \quad 3 \mu F; \quad V_{\text{max}} = 2000V$$

$$n \left[\frac{1}{2} (1) (500)^2 \right] = \frac{1}{2} (3) (2000)^2$$


$$n = 48$$

EX:- 3A:-

(18) $P = I^2 R \Rightarrow I V$ ($I = \frac{dq}{dt}$) $\Rightarrow P = \frac{Q}{t} \times V = \frac{12 \times 10^{-2} \times 3000}{2 \times 10^{-3}}$

$\therefore Q = 40 \times 10^6 \times 3 \times 10^3 \Rightarrow 12 \times 10^2 \Rightarrow P = 18 \times 10^4 = 180 \text{ kW}$

(19) 1st P-R:-

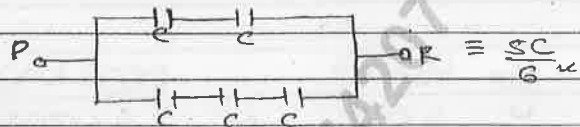

$\therefore P-R = \frac{5C}{6} = 4 = \frac{2}{3}$
 $P-Q = \frac{5C}{4} = 6 = \frac{3}{2}$

(23) see copy of Electrostat.

(11) $C = \frac{\epsilon_0 A}{d} \Rightarrow A = \frac{3 \times 5 \times 10^{-3}}{8.8 \times 10^{-12}}$


EX:- 3'B:-

(10) $\frac{2nC \times 2C}{2RC + 2C} = \frac{2eC \cdot R}{2e(R+1)}$


(17) $C = \frac{4\pi\epsilon_0 \epsilon_r R^2}{(R-r)} \Rightarrow C = \frac{4\pi\epsilon_0 \epsilon_r R^2}{R(R-r)}$

$C \Rightarrow \frac{1 \times 10^{-9} \times 6 \times 3}{9} \Rightarrow 2 \times 10^{-9} \text{ F}$

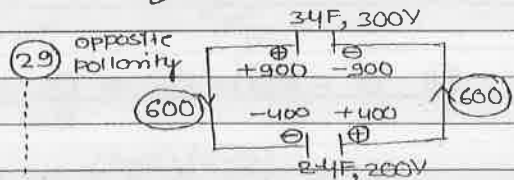
(30) $\epsilon = \frac{\epsilon_0 \epsilon_r (W \times L)}{d} = ?$



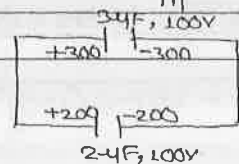$V_{\text{common}} = \frac{900 - 400}{2 + 3} = 100 \text{ V}$



(31) पिंटे से झोला करा

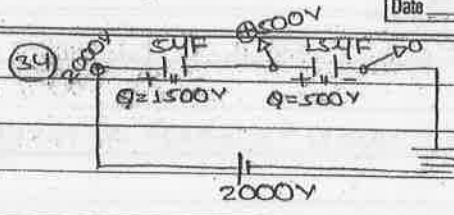

(50) $U = \frac{1}{2} R x^2$ $\because (R = k/x)$
 $U = \frac{1}{2} C V^2 \Rightarrow \frac{1}{2} \times 5000 \times 0.2 = \frac{1}{2} \times 10 \times 10^{-6} \times 10^8 = 1000 = 1$

(61) Energy (u): $\frac{1}{2} \epsilon_0 E^2 = \frac{Q^2}{2 \epsilon_0 A} \Rightarrow \frac{Q^2}{2 \epsilon_0 A} \Rightarrow \frac{Q^2}{2 \epsilon_0 A^2}$
 change density = q/A

(66/74) $\left(\frac{1}{2} C V^2\right) \times 2 \Rightarrow \because C' = C [d \rightarrow \text{doubled}] \Rightarrow \frac{1}{2} \left(\frac{C \times V^2}{2}\right) \times 2$
 \downarrow const.
 $\because \Delta V = \text{const};$ Because work is done by battery ($V = \text{const}$)

Str: $d' = 2d \Rightarrow C' = \frac{C}{2} \Rightarrow U = \frac{Q^2}{2C} \propto \frac{1}{C}$ (Battery Discon)

$[U_1 = \frac{1}{2} C V^2] = U_2 = 2U_1 \Rightarrow 2 \left(\frac{1}{2} C V^2\right)$

$W = \Delta U \Rightarrow U_2 - U_1 \Rightarrow \frac{1}{2} C V^2$

(79) $C_1 = \frac{\epsilon_0 R (A/3)}{d} \Rightarrow \frac{R}{3} \frac{\epsilon_0 A}{d}$
 $C_2 = \frac{\epsilon_0 (1) (2A/3)}{d} = \frac{2}{3} \left(\frac{\epsilon_0 A}{d}\right)$

$E = V = E_1 = E_2$

$C = C_1 + C_2 \Rightarrow C = \left(\frac{R+2}{3}\right) \left(\frac{\epsilon_0 A}{d}\right)$

(ii) $Q = C V \propto C \Rightarrow \frac{Q_1}{C_1} = \frac{Q_2}{C_2} = \frac{R}{2}$

$C = \frac{\left(\frac{R+2}{3}\right) \left(\frac{\epsilon_0 A}{d}\right)}{\frac{R}{3} \left(\frac{\epsilon_0 A}{d}\right)} \Rightarrow \frac{R+2}{R}$ (80) $E = \frac{6}{6 \epsilon_0 R}$

(81) $\frac{dQ^2}{dC} = E$ $Q_2 = C_2 V_2' = 2 \left(\frac{CE}{C+3}\right) \Rightarrow Q_2 = 2E \Rightarrow C \uparrow \Rightarrow Q_2 \uparrow$

$\frac{dQ^2}{dC} = 2E(1) \left(1 + \frac{3}{C}\right)^{-2} \times \frac{-3}{C^2} \Rightarrow \frac{6E}{C^2 \left(1 + \frac{3}{C}\right)^2} \Rightarrow \text{solpe} = \frac{6E}{(C+3)^2} \Rightarrow C \uparrow = \text{slope} \downarrow$

SHREE NATH JI BOOK 7014774207

Date _____ Page _____

SHREE NATH JI BOOK 7014774207

SHREE NATH JI BOOK 7014774207

SHREE NATHJI BOOK 7014774207